



Kirchhoff's laws and Wheatstone bridge

CLASS-XII

SUBJECT : PHYSICS
CHAPTER NUMBER: 03
CHAPTER NAME : CURRENT ELECTRICITY

CHANGING YOUR TOMORROW


Website: www.odmegroup.org
Email: info@odmps.org

Toll Free: **1800 120 2316**
Sishu Vihar, Infocity Road, Patia, Bhubaneswar- 751024

KIRCHHOFF'S LAWS:

I Law or Current Law or Junction Rule:

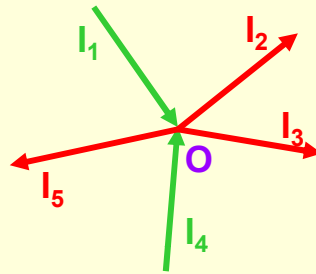The algebraic sum of electric currents at a junction in any electrical network is always zero.



$$I_1 - I_2 - I_3 + I_4 - I_5 = 0$$

Sign Conventions:

1. The incoming currents towards the junction are taken positive.
2. The outgoing currents away from the junction are taken negative.


Note: The charges cannot accumulate at a junction. The number of charges that arrive at a junction in a given time must leave in the same time in accordance with conservation of charges.

Numerical

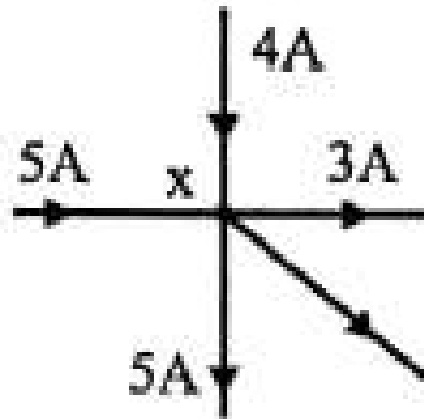Question: In the given figure what is the current through the arm shown


Solution :

$$\text{Unknown current} = 5A + 4A - 5A - 3A = 1A$$



II Law or Voltage Law or Loop Rule:

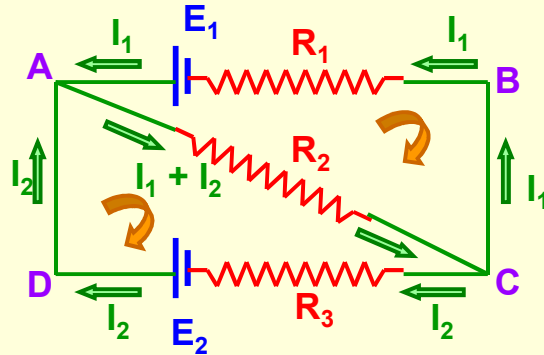The algebraic sum of all the potential drops and emf's along any closed path in an electrical network is always zero.



Loop ABCA:

$$-E_1 = -I_1.R_1 - (I_1 + I_2).R_2$$

Loop ACDA:

$$E_2 = (I_1 + I_2).R_2 + I_2.R_3$$


Sign Conventions:

1. The emf is taken **negative** when we traverse from **positive to negative** terminal of the cell through the electrolyte.
2. The emf is taken **positive** when we traverse from **negative to positive** terminal of the cell through the electrolyte.

Note: The path can be traversed in clockwise or anticlockwise direction of the loop.

Numerical

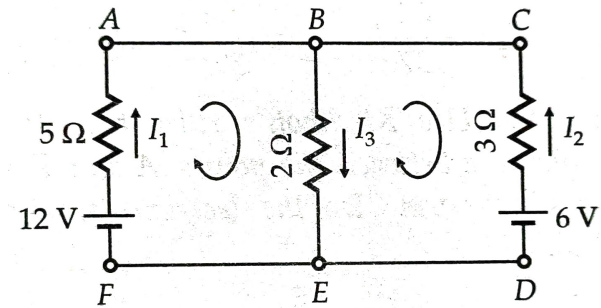Question: Using Kirchhoff's laws obtain the values of I_1 , I_2 and I_3 , as in the given figure.



Numerical

Question: Using Kirchhoff's laws obtain the values of I_1, I_2 and I_3 , as in the given figure.

Solution: In the figure using KCL; $I_3 = I_1 + I_2 \dots (i)$

Using KVL in the loop ABEFA;


$$5I_1 + 2I_3 = 12 \Rightarrow 5I_1 + 2(I_1 + I_2) = 12 \Rightarrow 7I_1 + 2I_2 = 12 \dots (ii)$$

In the loop BCDEB;

$$3I_2 + 2I_3 = 6 \Rightarrow 3I_2 + 2(I_1 + I_2) = 6 \Rightarrow 2I_1 + 5I_2 = 6 \dots (iii)$$


On solving equations (ii) and (iii) we have $I_1 = \frac{48}{31} A$ and $I_2 = \frac{18}{31} A$

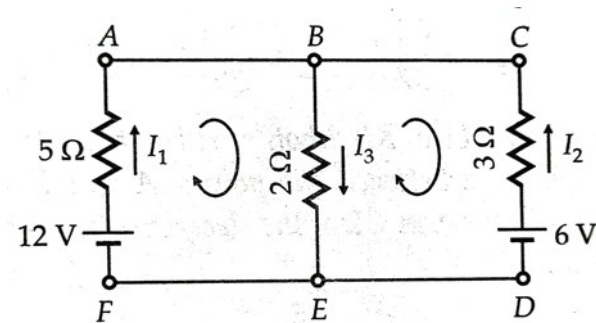Using the values in equation (i) we have ; $I_3 = I_1 + I_2 = \frac{48}{31} A + \frac{18}{31} A = \frac{66}{31} A$



Numerical

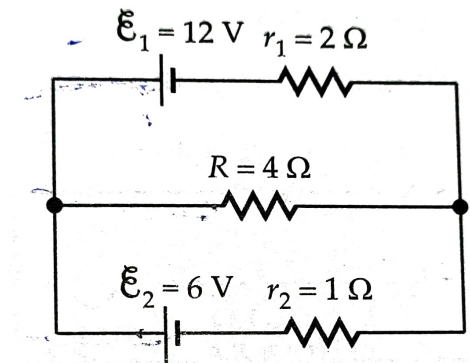Question: Using Kirchhoff's laws obtain the potential difference across each cell and also find the rate of energy dissipation in R.



Numerical

Question: Using Kirchhoff's laws obtain the potential difference across each cell and also find the rate of energy dissipation in R.

Solution :

Using KCL current is distributed and shown in the figure.

Using KVL in the loop ABCDA ;

$$4(I_1 + I_2) + 2I_1 = 12 \Rightarrow 6I_1 + 4I_2 = 12 \Rightarrow 3I_1 + 2I_2 = 6 \dots (i)$$


Using KVL in the loop CDEFC; $4(I_1 + I_2) + 1 \cdot I_2 = 6 \Rightarrow 4I_1 + 5I_2 = 6$

Solving equations (i) and (ii) we get

$$I_1 = \frac{18}{7} A \text{ and } I_2 = -\frac{6}{7} A \quad \text{i.e. } \frac{6}{7} A \text{ from E to F.}$$


$$\therefore V_{AB} = E_1 - I_1 r_1 = 12 - \frac{18}{7} \times 2 = \frac{48}{7} V = V_{EF}$$
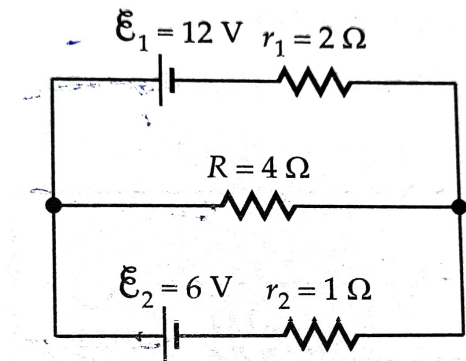
$$\therefore P_{4\Omega} = (I_1 + I_2)^2 \times 4\Omega = \left(\frac{12}{7} A\right)^2 \times 4\Omega = \frac{576}{49} W$$



Numerical

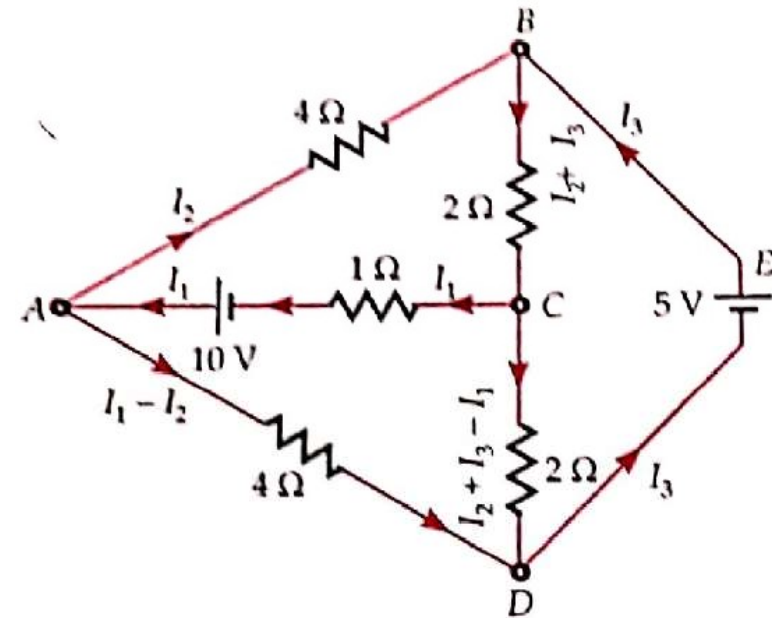Question:- Determine the current in each branch of the network shown in the figure.



Numerical

Question:- Determine the current in each branch of the network shown in the figure.

Solution :

The current distribution is shown by using KCL.


Using KVL, in the loop ABCA, $4I_2 + 2(I_2 + I_3) + 1(I_1) = 10$

$$\Rightarrow I_1 + 6I_2 + 2I_3 = 10 \quad \text{.....(i)}$$

In the loop ADCA, $1(I_1) - 2(I_2 + I_3 - I_1) + 4(I_1 - I_2) = 10$

$$\Rightarrow 7I_1 - 6I_2 - 2I_3 = 10 \quad \text{.....(ii)}$$

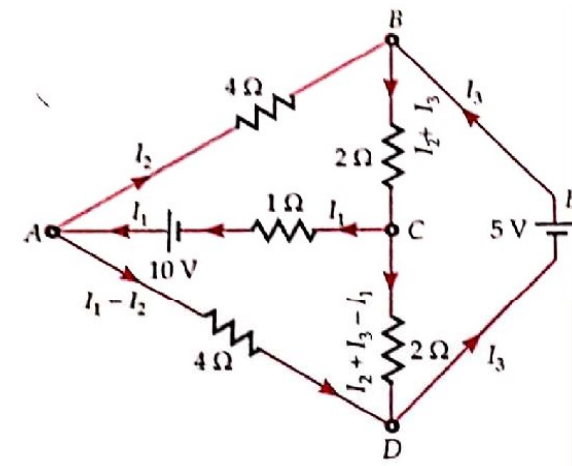In the loop BCDB, $2(I_2 + I_3) + 2(I_2 + I_3 - I_1) = 5 \Rightarrow -2I_1 + 4I_2 + 4I_3 = 5 \quad \text{.....(iii)}$



Numerical

Solution :

Now adding equations (i) and (ii) we get, $8I_1 = 20 \Rightarrow I_1 = \frac{20}{8}A = \frac{5}{2}A$ (iv)

Now equation (i) $\times 2 \Rightarrow 2I_1 + 12I_2 + 4I_3 = 20$ equation (iii) $\Rightarrow -2I_1 + 4I_2 + 4I_3 = 5$

Subtracting the two we have ; $4I_1 + 8I_2 = 15 \Rightarrow 4 \times \frac{5}{2} + 8I_2 = 15 \Rightarrow I_2 = \frac{5}{8}A$


Using values of I_1 and I_2 in equation (i) we get, $I_3 = \frac{15}{8}A$

Now for each arm; $CA = I_1 = 5/2A$; $AB = I_2 = 5/8A$; $DEB = I_3 = 15/8A$

$AD = I_1 - I_2 = 5/2 - 5/8 = 15/8A$; $BC = I_2 + I_3 = 5/8 + 15/8 = 5/2A$; $CD = I_2 + I_3 - I_1 = 0$


HOME ASSIGNMENT

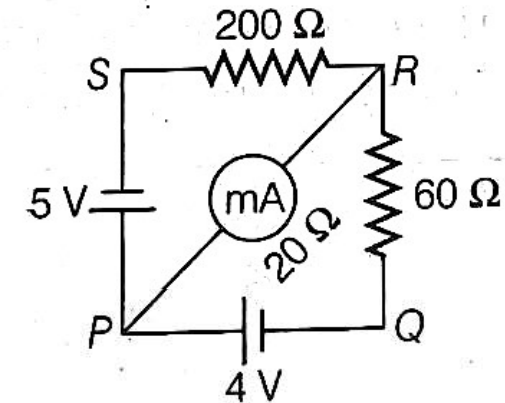1. The network PQRS, shown in the circuit diagram, has the batteries of 4 V and 5 V and negligible internal resistance. A milliammeter of 20Ω resistance is connected between P and R. Calculate the reading in the milliammeter.



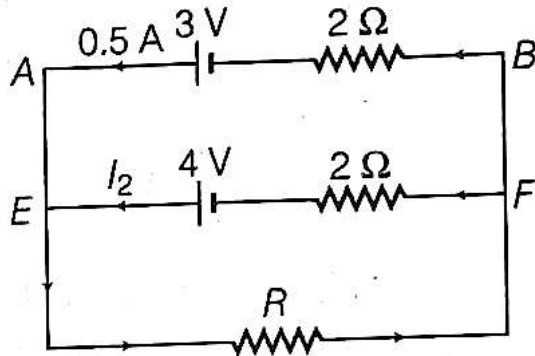2. Using Kirchhoff's rules in the given circuit, determine

- the current I_2 in the arm EF
- the voltage drop across the unknown resistor R



THANKING YOU
ODM EDUCATIONAL GROUP

