

Chapter- 12

ELECTRICITY**WORKSHEET**

1. Out of 60 W and 40 W lamps, which one has a higher electrical resistance when in use? (1 MARK)
2. What is the function of a galvanometer in a circuit? (1 MARK)
3. Why are the coils of electric toasters made of an alloy rather than a pure metal? (1 MARK)
4. A piece of wire of resistance $20\ \Omega$ is drawn out so that its length is increased to twice its original length. Calculate the resistance of the wire in the new situation. (1 MARK)
5. The values of current (I) flowing through a given resistor of resistance (R), for the corresponding values of potential difference (V) across the resistor are as given below : (3 MARKS)

Plot a graph between current (I) and potential difference (V) and determine the resistance (R) of the resistor.

V in volts	0.5	1.0	1.5	2.0	2.5	3.0	3.5	4.0
I in amperes	0.1	0.2	0.3	0.4	0.5	0.6	0.7	0.8

6. While studying the dependence of potential difference (V) across a resistor on the current (I) passing through it, in order to determine the resistance of the resistor, a student took 5 readings for different values of current and plotted a graph between V and I. (3 MARKS)
He got a straight line graph passing through the origin. What does the straight line signify? Write the method of determining resistance of the resistor using this graph.

