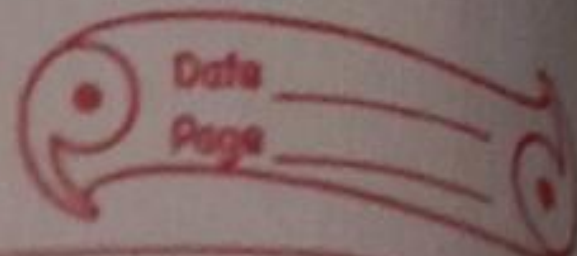


Chapter - 3

Current Electricity



1. $E = 12 \text{ V}$

$$r = 0.4 \Omega$$

Maximum current drawn from the battery = I

According to Ohm's law,

$$E = Ir$$

$$I = \frac{E}{r}$$

$$= \frac{12}{0.4} = 30 \text{ A}$$

The maximum current drawn from the given battery is 30A.

2.

$$E = 10 \text{ V}$$

$$r = 3 \Omega$$

$$I = 0.5 \text{ A}$$

Resistance of the resistor = R

The relation for current using Ohm's law is,

$$I = \frac{E}{R+r}$$

$$R+r = \frac{E}{I}$$

$$= \frac{10}{0.5} = 20 \Omega$$

$$\therefore R = 20 - 3 = 17 \Omega$$

Terminal voltage of the resistor = V

According to Ohm's law,

$$V = IR$$

$$= 0.5 \times 17$$

$$= 8.5 \text{ V.}$$

3(a) Three resistors of resistances 1Ω , 2Ω and 3Ω are combined in series. Total resistance of the combination is given by the algebraic sum of individual resistances.

Total resistance $1 + 2 + 3 = 6 \Omega$

(b) Current flowing through the circuit = I

$$E = 12 \text{ V}$$

$$R = 6 \Omega$$

The relation for current using Ohm's law is

$$I = \frac{E}{R}$$

$$= \frac{12}{6} = 2 \text{ A}$$

Potential drop across 1Ω resistor = V_1

From Ohm's law, the value of V_1 can be obtained

$$\text{as } V_1 = 2 \times 1 = 2 \text{ V} \dots \text{i}$$

Potential drop across 2Ω resistor = V_2

Again, from Ohm's law, the value of V_2 can be

$$\text{obtained as } V_2 = 2 \times 2 = 4 \text{ V} \dots \text{ii}$$

$$3 \Omega \text{ resistor} = V_3$$

$$V_3 = 2 \times 3 = 6 \text{ V} \dots \text{iii}$$

Therefore, the potential drop across 1Ω , 2Ω and

3Ω resistors are 2 V , 4 V and 6 V ~~respe.~~

respectively.

4 (a) There are three resistors of resistances,

$$R_1 = 2 \Omega \quad R_2 = 4 \Omega \quad \text{and} \quad R_3 = 5 \Omega$$

They are connected in parallel. Hence, total

resistance (R) of the combination is given by,

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$= \frac{1}{2} + \frac{1}{4} + \frac{1}{5} = \frac{10 + 5 + 4}{20} = \frac{19}{20}$$

$$\therefore R = \frac{20}{19} \Omega$$

Therefore, total resistance of the combination

$$\text{is } \frac{20}{19} \Omega.$$

(b) $V = 20\text{ V}$
 current (I_1) flowing through resistor R_1 is given by

$$I_1 = \frac{V}{R_1}$$

$$= \frac{20}{2} = 10\text{ A}$$

current (I_2) flowing through resistor R_2 is given by

$$I_2 = \frac{V}{R_2}$$

$$= \frac{20}{4} = 5\text{ A}$$

current (I_3) flowing through resistor R_3 is given by

$$I_3 = \frac{V}{R_3}$$

$$= \frac{20}{5} = 4\text{ A}$$

Total current, $I + I_1 + I_2 + I_3 = 10 + 5 + 4 = 19\text{ A}$
 Therefore, the current through each resistor is 10 A , 5 A and 4 A respectively and the total current is 19 A .

5. $T = 27^\circ\text{C}$
 $T, R = 100\ \Omega$

Let T is the increased temperature of the filament.

Resistance of the heating element at T_1 , $R_1 = 117\ \Omega$
 Temperature co-efficient of the material of the filament,

$$\alpha = 1.70 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}$$

α is given by the relation,

$$\alpha = \frac{R_1 - R}{R(T_1 - T)}$$

$$T_1 - T = \frac{R_1 - R}{R\alpha}$$

$$T_1 - 27 = \frac{117 - 100}{100(1.70 \times 10^{-4})}$$

$$T_3 - 27 = 1000$$

Therefore, at 1027°C , the resistance of the element is $117\ \Omega$.

6. $I = 15\ \text{m}$

$$a = 6.0 \times 10^{-7}\ \text{m}^2$$

$$R = 5.0\ \Omega$$

Resistivity of the material of the wire = ρ

$$R = \rho \frac{l}{A}$$

$$\rho = \frac{RA}{l}$$

$$= \frac{5 \times 6 \times 10^{-7}}{15} = 2 \times 10^{-7}\ \Omega\text{m}$$

7. $T_1 = 27.5^{\circ}\text{C}$

$$T_1, R_1 = 2.1\ \Omega$$

$$2. T_2 = 100^{\circ}\text{C}$$

$$T_2, R_2 = 2.7\ \Omega$$

Temperature coefficient of silver = α

$$\alpha = \frac{R_2 - R_1}{R_1 (T_2 - T_1)}$$

$$= \frac{2.7 - 2.1}{2.1 (100 - 27.5)} = 0.0039^{\circ}\text{C}^{-1}$$

8. $V = 230\ \text{V}$

$$I_1 = 3.2\ \text{A}$$

R_1 , which is given by the relation,

$$R_1 = \frac{V}{I}$$

$$= \frac{230}{3.2} = 71.87\ \Omega$$

~~$R_2 = \frac{230}{2.8}$~~ $I_2 = 2.8\ \text{A}$

R_2 , which is given as,

$$R = \frac{230}{2.8} = 82.14\ \Omega$$

$$\alpha = 1.70 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}$$

$$T_1 = 27.0^\circ\text{C}$$


T_2 can be obtained by the relation for α

$$\Delta R = \frac{R_2 - R_1}{R_1 (T_2 - T_1)}$$

$$T_2 - 27^\circ\text{C} = \frac{82.14 - 71.87}{71.87 \times 1.7 \times 10^{-4}} = 840.5$$

$$T_2 = 840.5 + 27 = 867.5^\circ\text{C}$$

9.

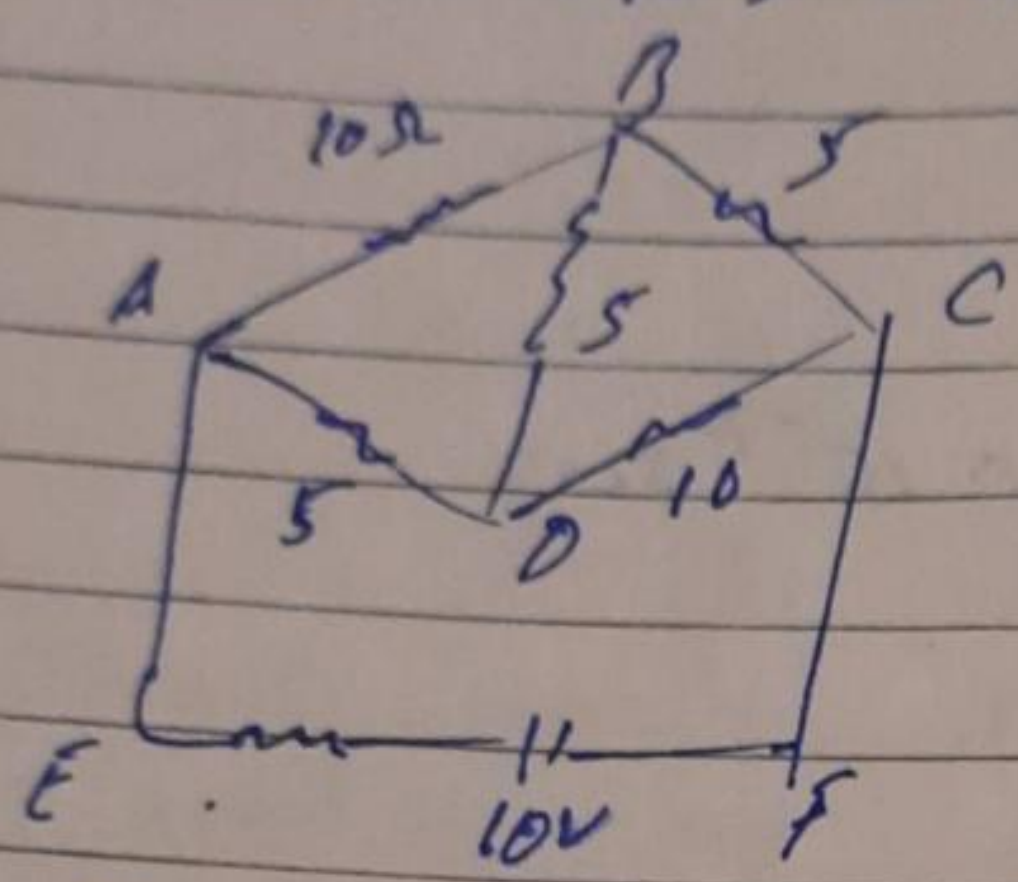

For the closed circuit ABDA, potential is zero

$$5(I_2 - I_4) - 10(I_3 + I_4) = 0$$

$$10I_2 + 5I_4 + 5I_3 = 0$$

$$2I_2 + I_4 + I_3 = 0$$

$$I_3 = 2I_2 + I_4 \quad \dots (1)$$

For the closed circuit BCDB, potential is zero i.e.,

$$5(I_2 - I_4) - 10(I_3 + I_4) - 5I_4 = 0$$

$$5I_2 + 5I_4 - 10I_3 - 10I_4 - 5I_4 = 0$$

$$5I_2 - 10I_3 - 20I_4 = 0$$

$$I_2 = 2I_3 + 4I_4 \quad \dots (2)$$

For the closed circuit ABCFEA, potential is zero i.e.,

$$-10 + 10(I_1) + 10(I_2) + 5(I_2 - I_4) = 0$$

$$10 = 15I_2 + 10I_1 - 5I_4$$

$$3I_2 + 2I_1 - I_4 = 2 \quad \dots (3)$$

$$I_3 = 2(2I_3 + 4I_4) + I_4$$

$$I_3 = 4I_3 + 8I_4 + I_4$$

$$-3I_3 = 9I_4$$

$$-3I_4 = +I_3 \quad \dots \dots (4)$$

$$I_3 = 2I_2 + I_4$$

$$-4\frac{1}{4} = 2I_2$$

$$I_2 = 2I_4 \quad \dots \dots (5)$$

$$I_1 = I_3 + I_2 \quad \dots \dots (6)$$

$$3I_2 = 2(I_3 + I_2) - I_4 = 2$$

$$5I_2 + 2I_3 - I_4 = 2 \quad \dots \dots (7)$$

Putting equations (4) and (5) in equation (7), we obtain

$$5(-2I_4) + 2(-3I_4) - I_4 = 2$$

$$-10I_4 - 6I_4 - I_4 = 2$$

$$17I_4 = 2$$

$$I_4 = \frac{-2}{17} \text{ A}$$

Equation (4) reduces to

$$I_3 = -3(I_4)$$

$$= -3 \left[\frac{-2}{17} \right] = \frac{6}{17} \text{ A}$$

$$I_2 = -2(I_4)$$

$$= -2 \left[\frac{-2}{17} \right] = \frac{4}{17} \text{ A}$$

$$I_2 - I_4 = \frac{4}{17} - \left[\frac{-2}{17} \right] = \frac{6}{17} \text{ A}$$

$$I_3 + I_4 = \frac{6}{17} + \left[\frac{-2}{17} \right] = \frac{4}{17} \text{ A}$$

$$I_1 = I_3 + I_2$$

$$= \frac{6}{17} + \frac{4}{17} = \frac{10}{17} \text{ A}$$

current in branch = $\frac{4}{17} \text{ A}$

in branch CD = $-\frac{4}{17} \text{ A}$

in branch AD = $\frac{6}{17} \text{ A}$

in branch BD = $\left[\frac{-2}{17} \right] \text{ A}$

Total current = $\frac{4}{17} + \frac{-4}{17} + \frac{6}{17} + \frac{-2}{17} = \frac{10}{17} \text{ A}$

10

(a) $A, l_1 = 39.5 \text{ cm}$

$Y = 12.5 \Omega$

Condition for the balance is given as,

$$\frac{X}{Y} = \frac{100 - l_1}{l_1}$$

$$X = \frac{100 - 39.5}{39.5} \times 12.5 = 8.9 \Omega$$

(b) If X and Y are interchanged, then l_1 and $100 - l_1$ get interchanged. The balance point of the bridge will be $100 - l_1$ from A . $100 - l_1 = 100 - 39.5 = 60.5 \text{ cm}$.

(c) When the galvanometer and cell are interchanged at the balance point of the bridge, the galvanometer will show no deflection. Hence, no current would flow through the galvanometer.

11. $\mathcal{E} = 8.0 \text{ V}$

$r = 0.5 \Omega$

$V = 120 \text{ V}$

$R = 15.5 \Omega$

Effective voltage in the circuit = V_1

$$V_1 = V - \mathcal{E}$$

$$V_1 = 120 - 8 = 112 \text{ V}$$

Current flowing in the circuit = I , which is given by the relation,

R is connected to the storage battery in series. Hence, it can be written as

$$I = \frac{V_1}{R + r}$$

$$= \frac{122}{15.5 + 0.5} = \frac{112}{16} = 7A$$

$$iR = 7 \times 15.5 = 108.5V$$

Voltage across resistor R given by the product, $iR = 7 \times 15.5 = 108.5V$

DC supply voltage = Terminal voltage of battery + voltage drop across R

$$\text{Terminal voltage of battery} = 120 - 108.5 = 11.5V$$

A series resistor in a charging circuit limits the current drawn from the external source. The current will be extremely high in its absence. This is very dangerous.

12. $E_1 = 1.25V$

$$I_1 = 35 \text{ cm}$$

$$E_2 =$$

$$I_2 = 63 \text{ cm}$$

The balance condition is given by the relation,

$$\frac{E_1}{E_2} = \frac{I_1}{I_2}$$

$$E_2 = E_1 \times \frac{I_2}{I_1}$$

$$1.25 = \frac{63}{35} = 2.25V$$

13. $n = 8.5 \times 10^{28} \text{ m}^{-3}$

$$L = 3.0 \text{ m}$$

$$A = 2.0 \times 10^{-6} \text{ m}^2$$

$$I = 3.0 \text{ A}$$

$$i = nAeV_d$$

where,

$$e = \text{Electric charge} = 1.6 \times 10^{-19} \text{ C}$$

$$V_d = \text{Drift velocity} = \frac{\text{Length of the wire (L)}}{\text{Time taken to cover (t)}}$$

$$I = nAe \frac{1}{t}$$
$$t = \frac{nAeL}{I}$$
$$= \frac{3.85 \times 10^{28} \times 2 \times 10^{-6} \times 1.6 \times 10^{-19}}{3.0}$$
$$= 2.7 \times 10^4 \text{ s}$$