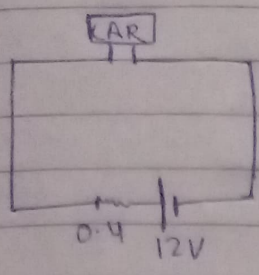


Current electricity - (NCERT)

Q1



Current will be maximum when external resistance will be zero


$$I = \frac{E}{r+R}$$

$$= \frac{E}{r} \quad R=0$$

$$= \frac{12}{0.4}$$

$$= \underline{\underline{30A}}$$

3.2)

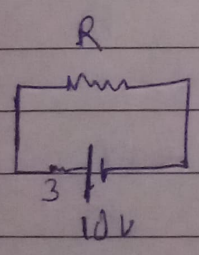

$I = 0.5A$

$$I = \frac{E}{R+r}$$

$$0.5 = \frac{10V}{3+R}$$


$$1.5 + 0.5R = 10V$$

$$0.5R = 8.5V$$

$$R = \frac{8.5}{0.5} = \underline{\underline{17\Omega}}$$


$$\begin{aligned} \text{Terminal Voltage} &= \mathcal{E} - I r \\ &= 10 - 0.5 \times 3 \\ &= 10 - 1.5 \\ &= \underline{8.5V} \end{aligned}$$

3.3

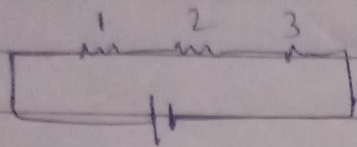

(a)
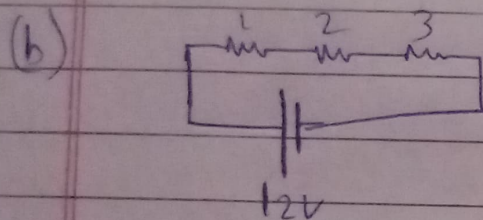
$$\begin{aligned} R &= 1 + 2 + 3 \\ &= \underline{6\Omega} \end{aligned}$$




$$I = \frac{V}{R} = \frac{12}{6} = \underline{2A}$$

$$\begin{aligned} V_1 &= IR_1 \\ &= 2 \times 1 \\ &= \underline{2V} \end{aligned}$$

$$\begin{aligned} V_2 &= IR_2 \\ &= 2 \times 2 \\ &= \underline{4V} \end{aligned}$$
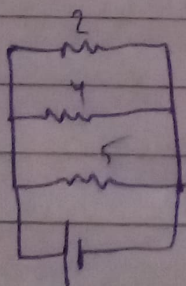
$$\begin{aligned} V_3 &= IR_3 \\ &= 2 \times 3 \\ &= \underline{6V} \end{aligned}$$



$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$= \frac{1}{\frac{1}{2} + \frac{1}{4} + \frac{1}{5}}$$

$$\frac{1}{R_{eq}} = \frac{10 + 5 + 4}{20}$$

$$\frac{1}{R_{eq}} = \frac{19}{20}$$

$$R_{eq} = \frac{20}{19} \Omega$$

(b) $E_{mf}(E) = 20 V$

$$V = IR$$

$$I = \frac{V}{R}$$

$$= \frac{20}{\frac{20}{19}}$$

Total = 19 A
Current

$$I_1 = \frac{V_1}{R_1}$$

$$= \frac{20}{2}$$

$$= \underline{10 A}$$

$$I_2 = \frac{V}{R_2} = \frac{20}{4} = \underline{5 A}$$

$$I_3 = \frac{V}{R_3} = \frac{20}{5} = \underline{4 A}$$

3.5

$$R_2 = R_1 [1 + \alpha(T_2 - T_1)]$$

$$R_1 = 27\% \text{ } 100 \Omega \quad T_1 = 27.0^\circ\text{C}$$

$$R_2 = 117 \Omega \quad T_2 = x^\circ\text{C}$$

$$\alpha = 1.70 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}$$

$$R_2 = R_1 [1 + \alpha(T_2 - T_1)]$$

$$\frac{R_2}{R_1} = 1 + 1.70 \times 10^{-4} (x - 27)$$

27
117
189
27
4.5

$$\frac{117}{100} = 1 + 1.70 \times 10^{-4} (x - 27)$$

$$1.17 = 1 + 1.70 \times 10^{-4} (x - 27)$$

$$1.70 \times 10^{-4} (x - 27) = 0.17$$

$$1.17 - 1 = 1.70 \times 10^{-4} (x - 27)$$

$$0.17 = 1.70 \times 10^{-4} (x - 27)$$

$$x - 27 = \frac{0.17}{1.70 \times 10^{-4}}$$

$$x = 1027^\circ\text{C}$$

3.6) Wire length = 15 m

Uniform cross-section of $6.0 \times 10^{-7} \text{ m}^2$

$$A = 6.0 \times 10^{-7} \text{ m}^2$$

$$R = 5 \Omega$$

$$R = \frac{\rho l}{A}$$

$$5 = \frac{\rho \cdot 15}{6.0 \times 10^{-7}}$$

$$\rho = \frac{5 \times 6.0 \times 10^{-7}}{15}$$
$$= 2 \times 10^{-7} \Omega \cdot m$$

~~3.7~~

$$R_1 = 2.1 \Omega$$
$$T_1 = 27.5^\circ C$$

$$R_2 = 2.7 \Omega$$
$$T_2 = 100^\circ C$$

$$R_2 = R_1 [1 + \alpha (T_2 - T_1)]$$

$$\frac{R_2}{R_1} = 1 + \alpha (T_2 - T_1)$$

$$\frac{R_2}{R_1} - 1 = \alpha (T_2 - T_1)$$

$$\frac{2.7}{2.1} - 1 = \alpha (100 - 27.5)$$

$$\frac{2}{7} = \alpha (72.5)$$

$$\alpha = \frac{2}{7 \times 72.5}$$


$$= 0.0039^\circ C^{-1}$$

3.8 ~~3.8~~)

Use Formula $R = \frac{V}{I}$

Then ~~R_1~~ $R_1 = R_2 [1 - \alpha(T_2 - T_1)]$

3.9)

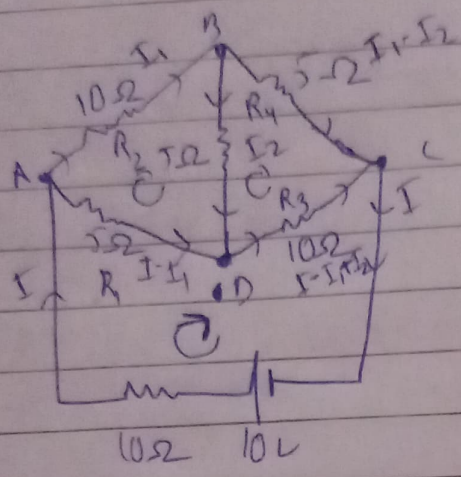

$$\frac{10}{5} = 2$$

$$\frac{R_2}{R_1} = \frac{R_4}{R_3} \quad \text{As } \frac{10}{5} \neq \frac{10}{10}$$

So it is a not wheatstone bridge

Use Kirchhoff's

law, $R_{\text{net}} = \frac{15 \times 15}{15+15} = 7.5$

$$-5(I - I_1) + 10(I_1) + 5I_2 = 0$$

- i $r = 10$

$$-10(I - I_1 + I_2) - 5(I_2) + 5(I_1 - I_2) V = 10V = 0$$

- ii $I = \frac{E_{\text{net}}}{R + R}$

$$10(I) + 5(I - I_1) = 10$$

$$+ 10(I - I_1 + I_2) = \frac{10V}{10 + 7.5}$$

- (iii)

Solving i & ii & iii,

Current in branch $AB = \frac{4}{17} A$, $BC = \frac{6}{17} A$, $CD = -\frac{4}{17} A$

In branch AD = $\frac{6}{17} \text{ A}$, In branch BD = $\left(\frac{-2}{17}\right) \text{ A}$

3.11/
emf = 8 V
 $r = 0.5 \Omega$

Volt = 120 V

Series resistor of 15.5 Ω

$$\begin{aligned} V' &= V - E \\ \text{(C.V.)} &= 120 - 8 \\ &= \underline{\underline{112 \text{ V}}} \end{aligned}$$

~~V = 120 - 8~~

$$I = \frac{V'}{R + r}$$

$$= \frac{112}{15.5 + 0.5} = \frac{112}{16} = 7 \text{ A}$$

$$\begin{aligned} IR &= 7 \times 15.5 \\ \text{Voltage drop} &= \underline{\underline{108.5 \text{ V}}} \end{aligned}$$

DC supply voltage = Terminal voltage of battery + Voltage drop across R

$$\begin{aligned} \therefore V_s &= 120 - 108.5 \\ &= \underline{\underline{11.5 \text{ V}}} \end{aligned}$$

A series resistor in a charging circuit limits the current drawn from the ext source. The current will be extremely high in its absence.

$$3.12 \quad n_e = 8.5 \times 10^{28} \text{ m}^{-3}$$

$$D = 30 \text{ m}$$

$$A = 2.0 \times 10^{-6} \text{ m}^2$$

$$I = 3 \text{ A}$$

$$I = neAV_d$$

$$V_d = \frac{I}{neA}$$

$e = \text{charge of } e$

$$V_d = \frac{3}{8.5 \times 10^{28} \times 2.0 \times 10^{-6} \times 1.6 \times 10^{-19}}$$

$$= \frac{3}{27 \times 10^3}$$

$$= 1.1 \times 10^{-22}$$

$$t = \frac{D}{v_d}$$

$$= \frac{3}{27 \times 10^3}$$

$$= 2.7 \times 10^4 \text{ s}$$

$$= 7.5 \text{ hr}$$

Additional Exercise:

3.14

Surface charge density, $\sigma = 10^{-9} \text{ C m}^{-2}$

Current over the entire globe, $I = 1900 \text{ A}$

$$r = 6.37 \times 10^6 \text{ m}$$

Surface area of the earth,
 $A = 4\pi r^2$

$$= 4\pi \times (6.37 \times 10^6)^2$$

$$= 5.09 \times 10^{14} \text{ m}^2$$

Charge on the earth surface,

$$q = \sigma \times A$$

$$= 10^{-9} \times 5.09 \times 10^{14}$$

$$= 5.09 \times 10^5 \text{ C}$$

$$I = \frac{q}{t}$$

$$t = \frac{q}{I} = \frac{5.09 \times 10^5}{1900}$$

$$= \underline{\underline{28.277 \text{ s}}}$$

3.15

a) $n = 6$ $E = 2.0 \text{ V}$

$r = 0.015 \Omega$ $R = 8.5 \Omega$

$$I = \frac{nE}{R + n\gamma}$$

$$= \frac{6 \times 2}{8.5 + 6 \times 0.015}$$

$$= \frac{12}{8.59} = 1.39 \text{ A}$$

Terminal voltage, $V = IR = 1.39 \times 8.5$
 $= \underline{11.87 \text{ V (Ans)}}$

$$I = \underline{1.39 \text{ A (Ans)}}$$

b) After a long time use, emf of the secondary cell, $E = 1.9 \text{ V}$

Int resistance of the cell, $r = 380 \Omega$

$$I = \frac{E}{r} = \frac{1.9}{380} = \underline{0.005 \text{ A (Maxim Current)}}$$

~~At~~ No, it cannot start the motor of the car

3.16 $R_1 = R_2$

$$\Rightarrow \frac{P_1 I_1}{A_1} = \frac{P_2 I_2}{A_2}$$

$$\Rightarrow \frac{P_1}{A_1} = \frac{P_2}{A_2} \text{ (Ans)}$$

$$\frac{R_1}{A_2} = \frac{\rho_1}{\rho_2}$$

$$= \frac{2.63 \times 10^{-8}}{1.72 \times 10^{-8}} = \frac{2.63}{1.72}$$

Mass = Vol \times density

$$M_1 = A_1 d_1$$

$$M_2 = A_2 d_2$$

$$\frac{M_1}{M_2} = \frac{A_1 d_1}{A_2 d_2}$$

$$\frac{M_1}{M_2} = \frac{2.63 \times 2.7}{1.72 \times 8.9} = 0.46$$

Hence, Aluminium is lighter than cable.

Since, aluminium is lighter, it is preferred for overhead power cables.

Q37 The ratio of voltage with current is a constant, which is equal to 19.7 & Manganin is a ohmic conductor

318

(a) When a steady current flows in a metallic conductor of non-uniform cross-section, the current flowing through the conductor is constant.

Current density, electric field, and drift speed are inversely proportional to the area of cross-section.
They aren't constant.

b) No. GaAs (Gallium Arsenide) doesn't follow Ohm's law

c) $I = \frac{V}{R}$ (According to Ohm's law)

If V is low, then R must be very low, so that I can be high

d) A (HT) supply of 6kV must have a very large resistance because if the internal ~~resistance~~ resistance is not large, then the current drawn can exceed the safety limits

3.19

a) greater

b) allows have lower temp of co-efficient of resistance than pure metals.


c) Independent

d) 10^{22}

3.20 (a) i) to get max^m resistance: connect it in series
ii) to get min^m resistance: connect it in parallel

iii) Ratio of max^m to min^m: $\frac{NR}{R/n} = \frac{n^2}{1}$


b) i) $1\Omega, 2\Omega, 3\Omega$

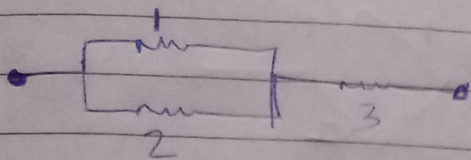

$$R' = \frac{2 \times 1}{2+1} + 3$$

$$= \frac{2}{3} + 3 = \underline{\underline{\frac{11}{3} \Omega}}$$


(ii) $\frac{11}{3} \Omega$

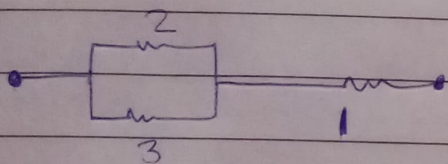

$$R' = \frac{2 \times 3}{2+3} + 1$$

$$= \frac{11}{5} \Omega$$


(iii) 6Ω

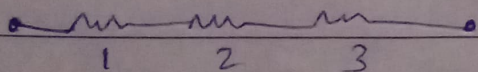

$$R' = 1+2+3$$



$$= \underline{\underline{6\Omega}}$$

(iv) $\frac{6}{11} \Omega$

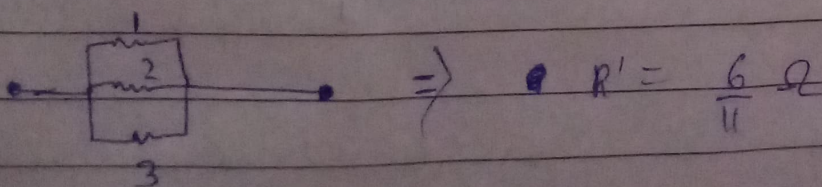

$$\Rightarrow R' = \frac{6}{11} \Omega$$

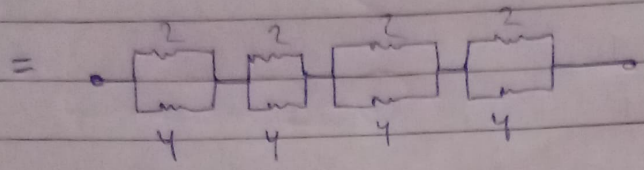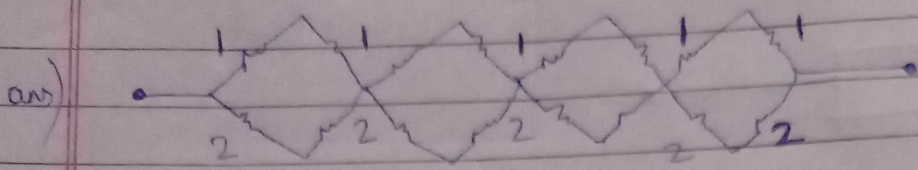c) Determine the eqv resistance of networks :




$$R_{eqv} = 4 \left(\frac{2 \times 4}{2+4} \right)$$

$$= 4 \left(\frac{8}{6} \right)$$

$$= \frac{32}{6}$$


$$= \frac{16}{3} \Omega$$

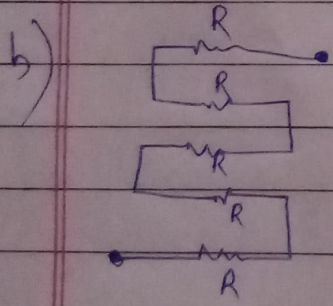

$$R_{net} = R + R + R + R + R$$

$$= \underline{5R}$$

Q321

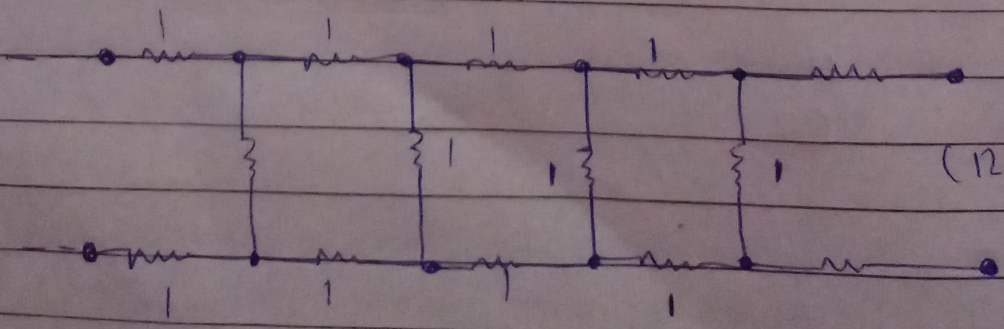

(12V, 0.5Ω)

Let eqv resistance in the circuit = R'

~~R~~

$$\therefore R' = 2 + \frac{R'}{R'+1}$$

$$(R')^2 - 2R' - 2 = 0$$

$$R' = \frac{2 \pm \sqrt{4+8}}{2}$$

$$= \frac{2 \pm \sqrt{12}}{2} = 1 \pm \sqrt{3}$$

Negative value of R' cannot be accepted.
Hence, equivalent resistance

$$R' = 1 + \sqrt{3}$$

$$= 1 + 1.73$$

$$= 2.73 \Omega$$

$$r = \underline{0.5 \Omega}$$

$$\text{Total resistance of the given circuit} = 2.73 + 0.5$$


$$= 3.23 \Omega$$

$$V = 12V$$

$$I = \frac{V}{R}$$

$$= \frac{12}{3.23} = 3.72A$$

3.22

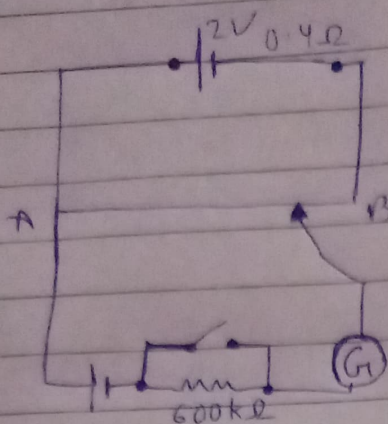

(a) $E_1 = 1.02 \text{ V}$
 Balance-point (d_1) = 67.3 cm

~~new~~ replaced by unknown emf (\mathcal{E})

new balance point (d_2) = 82.3

$$\frac{E_1}{\mathcal{E}} = \frac{d_1}{d_2}$$

$$\frac{1.02}{\mathcal{E}} = \frac{67.3}{82.3}$$

$$\mathcal{E} = \frac{82.3 \times 1.02}{67.3}$$

$$= \underline{\underline{1.247 \text{ V}}}$$

The value of unknown emf is 1.247 V

(b) ^{ans} Purpose of using ^{high} resistance of $600 \text{ k}\Omega$ to reduce the current through galvanometer.

(c) The balance point is not affected by the int resistance of the driver cell.

- (d) The point is not affected by the int resistances of the driver cell.
- (e) The circuit would not work well for determining an extremely small emf. As the circuit would be unstable, the balance point would be close to end A.

This can be modified if a series resistance is connected with the wire AB.

Q3:23


Potentiometer for comparison of 2 resistances.

$R = 10.0 \Omega$
 $l_1 = 58.3 \text{ cm}$

$E_1 = iR$

Unknown resistor = X

$E_2 = iX$

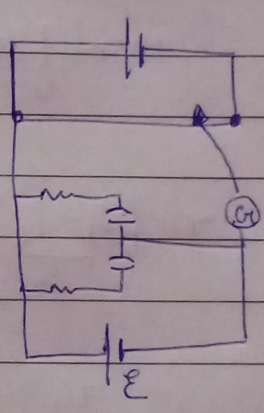

The relation connecting emf and balance point is,

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

$$\frac{iR}{iX} = \frac{l_1}{l_2}$$

$$X = \frac{l_1}{l_2} \times R$$

$$= \frac{68.5}{58.3} \times 10 = \underline{\underline{11.749 \Omega}}$$

The value of unknown resistance, X , is 11.75 Ω

If balance point is not obtained, we add a series resistance to it

~~Q 3.24~~

~~Q 3.24~~
Ans

Int resistance of the cell = r

$$l_1 = 76.3 \text{ cm}$$

$$R = 9.5 \Omega$$

$$l_2 = 64.8 \text{ cm}$$

Current flowing through the circuit = I

$$r = \left(\frac{l_1 - l_2}{l_2} \right) R$$

$$= \frac{76.3 - 64.8}{64.8} \times 9.5$$

$$= \underline{1.68 \Omega}$$

Int resistance of the cell is 1.68 Ω