

# Phy:-

①

$$R_{eq} = \frac{R_0 + R_0}{2} \parallel R$$

$$I = \frac{V}{R_{eq}}$$

P.D

$$V_R = I \left( \frac{R_0}{2} \parallel R \right)$$

$$V_R = \frac{V}{R_{eq}} \left( \frac{R_0}{2} \parallel R \right)$$

$$V_R = \left( \frac{R_0}{2} \parallel R \right)$$

$$V_R = \frac{R}{R + R_0} V$$

2 (1) By increasing R current through AB decreases So potential gradient decreases here a greater length of wire ~~is~~ should be needed for balancing same P.D So, null point shifted toward SB


(ii) By decreasing resistance of AB, current potential gradient does not change as  $k_2$  is open so there is no effect on null point.

(3) a) (i) to have lower value of potential gradient i.e. lower least count or greater sensitivity

ii area of cross section has to be uniform to get a uniform wire as per principle of potentiometer

(iii) emf driving cell has to be greater than emf of primary cells

b) 
$$PP = k = \frac{V}{L}$$

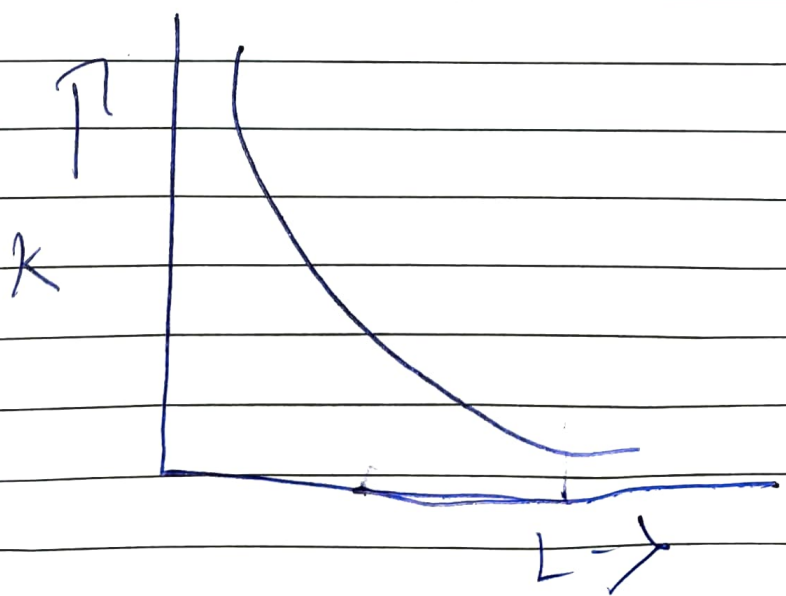

~~4) 1000~~

(i) so AI will loss

ii  $R_1$  decreases

Current  $\uparrow$  is

Potential Gradient  $\uparrow$  is

AI = Balance length  $\downarrow$  is

(5)

(i) Decreases

PD gradient increase

ii ~~increases~~

Actual PD across cell would increase