

3.1 Here  $\mathcal{E} = 12\text{V}$   
 $r = 0.4\Omega$   
 Current  $= R = 0$

$$I_{\text{max}} = \frac{\mathcal{E} = 12}{r = 0.4} = 30\text{A}$$

Q2 ~~AB~~

3.2  $I = \frac{\mathcal{E}}{R + r}$

$$R + r = \frac{\mathcal{E}}{I}$$

$$R = \frac{\mathcal{E}}{I} - r = \frac{10}{0.5} - 3 = 17\Omega$$

$$P.V = V = IR = 0.5 \times 17 = 8.5\text{V}$$

3.3.  $R_s = R_1 + R_2 + R_3 = 60\Omega$

$$\text{Current} = \frac{\mathcal{E} = 12}{R = 60} = 2\text{A}$$

P.d. across different resistors

$V_1 = IR_1$	$2 \times 1 = 2\text{V}$
$V_2 = IR_2$	$2 \times 2 = 4\text{V}$
$V_3 = IR_3$	$2 \times 3 = 6\text{V}$

3.4 >

$$\frac{19}{20}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_p = \frac{20}{19} \Omega$$

$$\frac{1}{2} + \frac{1}{4} + \frac{1}{5}$$

$$= \frac{19}{20}$$

⊙

$$= R_p = \frac{20}{19} \Omega$$

11 Current

$$I_1 = \frac{E}{R_1} = \frac{20}{2} \text{ 10A}$$

$$I_2 = \frac{E}{R_2} = \frac{20}{4} \text{ 5A}$$

$$I_3 = \frac{20}{5} \text{ 4A}$$

$$\text{Total Current} = 10 + 5 + 4 = 19A$$

3.5

$$R_1 = 100$$

$$R_2 = 117$$

$$t_1 = 27$$

$$L = 1.70 \times 10^{-4} \text{ C}^{-1}$$

$$L = \frac{R_2 R_1}{R_1 (t_2 - t_1)}$$

$$t_2 - t_1 = \frac{R_2 - R_1}{R_1 L} = \frac{117 - 100}{100 \times 1.70 \times 10^{-4}}$$

$$t_2 = 1000 + t_1 = 1000 + 27 = 1027 \text{ C}$$

3.6

$$L = 15 \mu\text{H}$$

$$A = 6.0 \times 10^{-2} \text{ A}^2$$

$$R = 5 \text{ } \Omega$$

$$P = \frac{I^2 R}{L}$$

$$\frac{5.0 \times 6.0 \times 10^{-7}}{15}$$

$$= 2.0 \times 10^{-7} \text{ W}$$

37

$$R_1 = 2.1 \Omega$$

$$R_2 = 27.5 \Omega$$

$$R_2 = 2.7 \Omega$$

$$R_2 = 100 \Omega$$

$$\Delta_{temp} = \frac{R_2 - R_1}{$$

$$R_1 (T_2 - T_1)$$

$$= \frac{2.7 - 2.1}{$$

$$2.1 (100 - 27)$$

$$= 0.6$$

$$2.1 \times 72.5$$

$$= 0.00394 \text{ } ^\circ\text{C}^{-1}$$

38

$$V = 230 \text{ V}$$

$$I = 3.2$$

$$P_2 = 2.8$$

$$\lambda = 1.70 \times 10^{-9} \text{ m}$$

$$R_1 = \frac{V}{I_1} = \frac{230}{3.2} = 71.875$$

$$R_2 = \frac{V_2}{I_2} = \frac{230}{2.8} = 82.143 \Omega$$

$$r = \frac{R_2 \cdot R_1}{R_1 + R_2}$$

$$I_2 - I_1 = \frac{I_2 - I_1}{R_1 + R_2}$$


$$\frac{82.143 - 71.875}{71.875 + 82.143}$$

$$71.875 \times 1.70 \times 10^{-4}$$

$$= \frac{10.208 \times 10^4}{71.875 \times 1.7} = 840 \times 35^\circ \text{C}$$



3.9

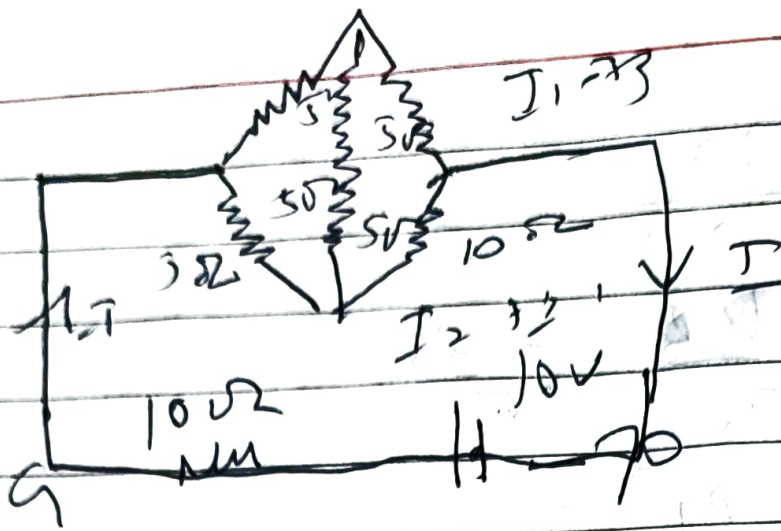

ABDA

$$10I_2 + 5I_3 - 5I_2 = 0$$

$$5(I_2 - I_3) - 10(-I_2 + I_3) - 5I_3 = 0$$

$$5I_2 + 10(I_2 + I_3) + 10(-I_2 + I_3) = 10$$

$$10I_1 - 5I_2 + 5I_3 = 0$$

$$5I_1 - 10I_2 = 20I_3 = 0$$

$$10I_1 + 25I_2 + 10I_3 = 0$$



$$I_{AB} = \frac{240}{17} \text{ A}$$

$$I_{BC} = I_1 - I_3 = \frac{6}{17} \text{ A}$$

$$I_{PR} = I_2 + I_3 = \frac{4}{17} \text{ A}$$

$$I = AD = I_2 = \frac{6}{17}$$

$$I_{BD} = I_3 = \frac{2}{17} \text{ A}$$

$$\text{total current} = \frac{10}{17}$$

$$3.10 \quad l = 35.9 \text{ m}$$

$$R = x = 7$$

$$S = x = 12.5 \text{ m}$$

$$d_{15} = \frac{100 - l}{l} \times 12$$

$$= \frac{100 - 39.5}{39.5} \times 12$$

$$= \frac{12.5 \times 39.5}{60.5} = 8.15 \text{ m}$$

$$3.11 \quad l_1 = 1.25 \text{ m}$$

$$l_1 = 35.0$$

$$l_2 = 65.0$$

$$z_2 = ?$$

$$\frac{G_2}{a_1} = \frac{12}{l_1}$$

$$R_2 = \frac{l_2}{A} \epsilon_4 = \frac{63 \times 10^{-5}}{55} = 2.25 \Omega$$

$$3.13 \quad n = 8.5 \times 10^{-6} \text{ m}^2$$

$$A = 2.0 \times 10^{-4} \text{ m}^2$$

$$E = 1.0 \times 10^9 \text{ C}$$

$$I = 300 \text{ A}$$

$$V_1 = \frac{I}{\epsilon n A}$$

$$\frac{3}{1.6 \times 10^{-19} \times 8.5 \times 10^{-6} \times 10^{28} \times 2 \times 10^{-6}}$$

M/S

$$\frac{3}{1.6 \times 8.5 \times 2 \times 10} \text{ m/s}$$

$$= 1.1 \times 10^{-4} \text{ m/s}$$

Repeat here

$$E = \frac{T}{4\pi}$$



$$\frac{3}{1.1 \times 10^{-4}}$$

$$= 2.73 \times 10^4 \text{ s} = 7.57 \text{ m}$$