

## Exercises

3.1 Emf  $\epsilon$ ,  $E = 12V$ .

Internal resistance of the battery,  $r = 0.4\Omega$

Max current drawn from the battery =  $I$

According to Ohm's law.

$$\bar{E} = Ir$$

$$I = \frac{E}{r}$$

$$= \frac{12}{0.4} = 30A$$

Current drawn from the battery =  $30A$ .

3.2 Emf of the battery,  $E = 10V$

Internal resistance of the battery =  $3\Omega$

Current in the circuit =  $0.5A$

Resistance of the resistor =  $R$

The relation for current using Ohm's law is,

$$I = \frac{E}{R+r}$$


$$0.5 = \frac{10}{R+3}$$

$$0.5 = \frac{10}{R+3} \Rightarrow 20\Omega = R+3$$

$$R = 20 - 3$$

$$R = 17\Omega$$

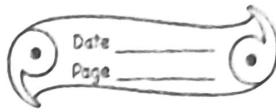Terminal voltage of the resistor is  
 $17\Omega$  or



Terminal voltage of the resistor =  $V$   
According to Ohm's Law.

$$V = IR$$

$$\begin{aligned} &= 0.5 \times 17 \\ &= 8.5 \text{ V} \end{aligned}$$

Therefore, the resistance of the resistor is  $17\Omega$  and the terminal voltage is  $8.5 \text{ V}$ .

3.3 a) Three resistor of resistance  $1\Omega, 2\Omega, 3\Omega$  are combined in series. Total resistance of the combination is given by the algebraic sum of individual resistances.

$$\text{Total resistance} = 1 + 2 + 3 = 6\Omega$$

b) Current flowing through the circuit =  $I$

Emf of the battery,  $E = 12 \text{ V}$

Total resistance of the circuit,  $R = 6\Omega$ .

The relation for current using Ohm's Law is

$$I = \frac{E}{R}$$

$$= \frac{12}{6} = 2 \text{ A}$$

Potential drop across  $1\Omega$  resistor =  $V_1$ ,

From Ohm's law, the value of  $V_1$  :-

$$V_1 = 2 \times 1 = 2 \text{ V} \quad \text{--- (i)}$$



Potential drop across  $2\Omega$  resistor =  $V_2$

Again from Ohm's law, the value of  $V_2$  :-

$$V_2 = 2 \times 2 = 4V \dots\dots (ii)$$

Potential drop across  $3\Omega$  resistor =  $V_3$

Again from Ohm's law. the value of  $V_3$  :-

$$V_3 = 3 \times 2 = 6V \dots\dots (iii)$$

$\therefore$  The potential drop across  $1\Omega, 3\Omega, 2\Omega$  resistors are,  $2V, 6V$  and  $4V$  respectively.

3.4(a) There are three resistors of resistance.

$$R_1 = 2\Omega, R_2 = 4\Omega, R_3 = 5\Omega$$

Total resistance ( $R$ ) is given by.

$$\begin{aligned} \frac{1}{R} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ &= \frac{1}{2} + \frac{1}{4} + \frac{1}{5} \\ &= \frac{10+5+4}{20} = \frac{19}{20} \end{aligned}$$

$$R = \frac{20}{19} \Omega$$

$\therefore$  Total resistance of the combination is  $\frac{20}{19}\Omega$ .

b) Emf of the battery,  $V = 20V$

Current ( $I_1$ ) flowing through resistor  $R_1$  :-

$$I_1 = \frac{V}{R_1} = \frac{20}{2} = 10A$$

Current ( $I_2$ ) flowing through resistor ( $R_2$ ) :-

$$R_{\text{in}} \cdot I_2 = V = \frac{20}{4} = 5 \text{ A}$$

Current ( $I_3$ ) flowing through resistor ( $R_3$ ) :-

$$I_3 = \frac{V}{R_3} = \frac{20}{5} = 4 \text{ A}$$

$$\text{Total current } I = I_1 + I_2 + I_3 = 10 + 5 + 4 = 19 \text{ A}$$

i. Current through each resistor is 10A, 5A and 4A respectively. and total current = 19A.

3.5 Room Temp,  $T = 27^\circ\text{C}$

Resistance of the heating element at  $T$ ,  $R = 100\Omega$

Let,  $T_1$  is the increased temperature of the filament.

Resistance of the heating element at  $T_1$ ,  $R_1 = 117\Omega$

Temp. co-efficient of the material of the filament.

$$\alpha = 1.70 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}$$

$\alpha$  is given by the relation :-

$$\alpha = \frac{R_1 - R}{R(T_1 - T)}$$

$$T_1 - T = \frac{R_1 - R}{R\alpha}$$

$$T_1 - 27 = \frac{117 - 100}{100(1.7 \times 10^{-4})}$$

$$T_1 - 27 = 1000$$

$$T_1 = 1027^\circ\text{C}$$

at  $102.5^{\circ}\text{C}$ , the resistance of the element is  $11.5\ \Omega$ .

3.6 length of the wire,  $l = 15\text{ m}$

area of cross-section of the wire,  $a = 6.0 \times 10^{-7}\text{ m}^2$

resistance of the material of the wire,  $R = 5.0\ \Omega$

resistivity of the material of the wire =  $\rho$

resistance is related with resistivity as -

$$R = \rho \frac{l}{a}$$

$$\rho = \frac{Ra}{l}$$

$$= \frac{5.0 \times 10^{-7}}{15} = 2 \times 10^{-8}\ \Omega\text{-m}$$

i.e. Resistivity of the material is  $2 \times 10^{-8}\ \Omega\text{-m}$ .

3.7 Temp.  $T_1 = 27.5^{\circ}\text{C}$

Resistance of silver wire at  $T_1$ ,  $R_1 = 2.1\ \Omega$

Temp.  $T_2 = 100^{\circ}\text{C}$

Resistance of silver wire at  $T_2$ ,  $R_2 = 2.7\ \Omega$

Temp co-efficient of silver =  $\alpha$

$$\alpha = \frac{R_2 - R_1}{R_1(T_2 - T_1)}$$

$$= \frac{2.7 - 2.1}{2.1(100 - 27.5)} = 0.0039\ ^{\circ}\text{C}^{-1}$$

i.e. The temp. co-efficient of silver is  $0.0039\ ^{\circ}\text{C}^{-1}$

3.8

Supply voltage  $V = 230V$ Initial current drawn,  $I_1 = 3.2A$ Initial resistance =  $R_1$ ,

$$R_1 = \frac{V}{I}$$

$$= \frac{230}{3.2} = 71.87 \Omega$$

Steady state value of the current,  $I_2 = 2.8A$ Resistance at the steady state =  $R_2$ , which is given as:-

$$R_2 = \frac{230}{2.8} = 82.14 \Omega$$

Temp. co-efficient of nichrome,  $\alpha = 1.70 \times 10^{-4} ^\circ C^{-1}$ Initial temp. of nichrome,  $T_1 = 27.0^\circ C$ Steady state temp. reached by nichrome =  $T_2$ 

$$\alpha = \frac{R_2 - R_1}{R_1(T_2 - T_1)}$$


$$1.70 \times 10^{-4} = \frac{82.14 - 71.87}{71.87 \times 1.70 \times 10^{-4}}$$

$$T_2 - 27^\circ C = 82.14 - 71.87 = 8^\circ C$$

$$T_2 = 840.5 + 27 = 867.5^\circ C$$

$\therefore$  The steady temp. of the heating element is  $867.5^\circ C$ .

3.9

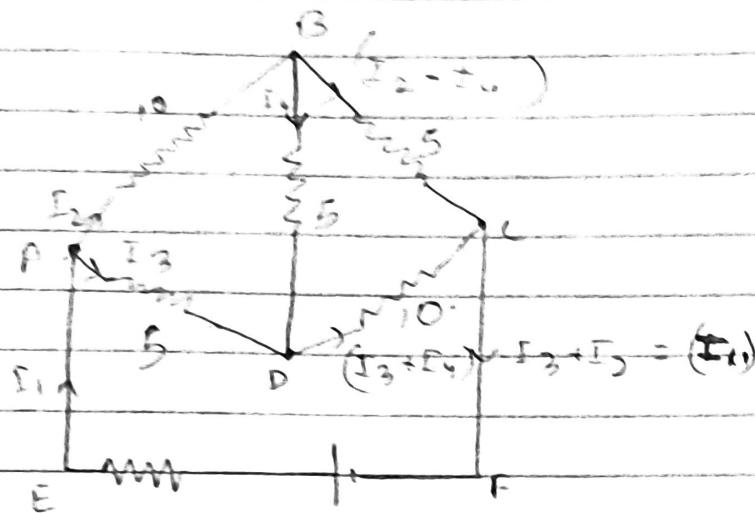

$I_1$  = current flowing through the outer circuit.

$I_2$  = current flowing through branch AB

$I_3$  = current flowing through branch AD

$I_4 - I_5$  = current flowing through branch BC

$I_3 + I_4$  = current flowing through branch DC

$I_5$  = current flowing through branch BD

For closed circuit ABDA, potential is zero,

$$10I_4 + 5I_4 - 5I_3 = 0$$

$$2I_2 + I_4 - I_3 = 0$$

$$I_3 = 2I_2 + I_4 \quad \text{--- (1)}$$

For closed circuit ABCFEA, potential is zero,

~~$$5(I_3 - I_4) - 10(I_3 + I_4) - 5I_4 = 0$$~~

~~$$5I_2 - 5I_4 - 10I_3 + -10I_4 - 5I_4 = 0$$~~

~~$$5I_2 - 10I_3 - 20I_4 = 0$$~~

$$I_2 = 2I_3 + 4I_4 \quad \text{--- (2)}$$

For closed circuit BCDD, potential is zero,

$$5(I_2 - I_4) - 10(I_3 + I_4) - 5I_4 = 0$$

$$5I_2 - 5I_4 - 10I_3 - 10I_4 - 5I_4 = 0$$

$$\boxed{10I_2 + 5I_4 - 5I_3 = 0}$$

$$5I_2 - 10I_3 - 20I_4 = 0$$

$$I_2 = 2I_3 + 4I_4 \quad \text{--- (2)}$$

For the closed circuit ABCEA, potential is zero,

$$-10 + 10(I_2) + 10(I_2) + 5(I_2 - I_4) = 0$$

$$10 = 15I_2 + 10I_1 - 5I_4$$

$$3I_2 + 2I_1 - I_4 = 2 \quad \text{--- (3)}$$

from eqn (1) & (2), we obtain

$$I_3 = 2(2I_3 + 4I_4) + I_4$$

$$I_3 = 4I_3 + 8I_4 + I_4$$

$$-3I_3 = 9I_4$$

$$3I_4 = I_3 \quad \text{--- (4)}$$

Putting equation (4) in eqn (1), we

$$I_3 = 2I_4 + I_4$$

$$-4I_4 = 2I_2$$

$$I_2 = -2I_4 \quad \text{--- (5)}$$

It is evident from the given figure that,

$$I_1 = I_3 + I_2 \quad \text{--- (6)}$$

Putting eq<sup>n</sup> ⑥ in ①:

$$3I_2 + 2(I_3 + I_2) - I_4 = 2$$

$$5I_2 + 2I_3 - I_4 = 2 \quad \text{--- } ⑦$$

Putting eq<sup>n</sup> ④ & ⑤ in eq<sup>n</sup> ⑦

$$5(-2I_4) + 2(-3I_4) - I_4 = 2$$

$$-10I_4 - 6I_4 - I_4 = 2$$

$$17I_4 = -2$$

$$I_4 = -\frac{2}{17} \text{ A.}$$

Eq<sup>n</sup> ④ reduces to

$$I_3 = -3(I_4)$$

$$= -3\left(-\frac{2}{17}\right) = \frac{6}{17} \text{ A.}$$

$$I_2 = -2I_4$$

$$= -\frac{4}{17} \text{ A.}$$

$$I_1 - I_4 = \frac{4}{17} - \left(-\frac{2}{17}\right) = \frac{6}{17} \text{ A.}$$

$$I_3 + I_4 = \frac{6}{17} + \left(-\frac{2}{17}\right) = \frac{4}{17} \text{ A.}$$

$$I_1 = I_3 + I_2$$

$$= \frac{6}{17} + \frac{4}{17} = \frac{10}{17} \text{ A.}$$


∴ Current in Branch

$$AB = \frac{4}{17} \text{ A}, \quad CD = -\frac{4}{17} \text{ A}, \quad BD = -\frac{2}{17}$$

$$BC = \frac{6}{17} \text{ A}, \quad AD = \frac{6}{17} \text{ A.}$$

$$\text{Total current} = \frac{4 + 6 - 4 + 6 - 2}{17} = \frac{10}{17} \text{ A}$$

3.10

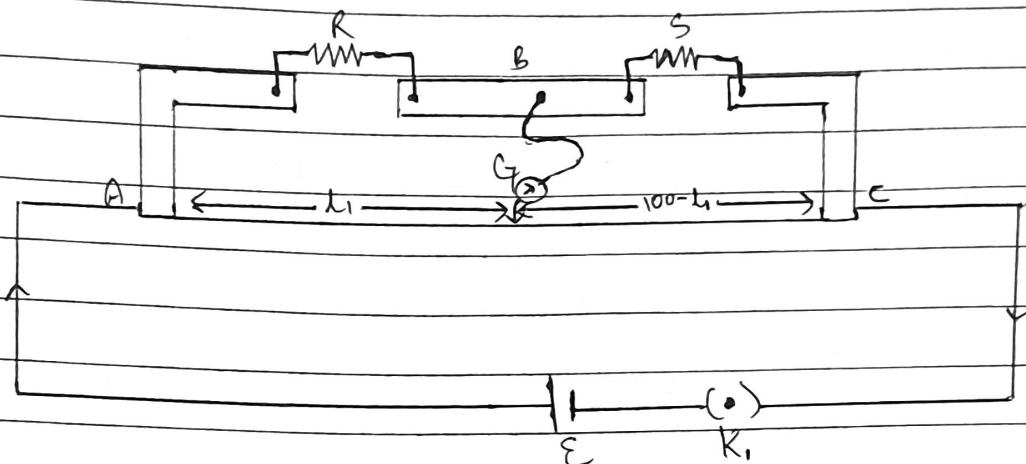

a) Balance point from end A,  $l_1 = 39.5 \text{ cm}$

Resistance of the resistor  $Y = 12.5 \Omega$

Condition for the balance is given as,

$$\frac{X}{Y} = \frac{100 - l_1}{l_1}$$

$$X = \frac{100 - 39.5}{39.5} \times 12.5 = 8.2 \Omega$$

Therefore, the resistance of resistor  $X$  is  $8.2 \Omega$

The connection between resistors in a Wheatstone or metre bridge is made of thick copper strips to minimize the resistance, which is not taken into consideration in the bridge formula.

b) If  $X$  and  $Y$  are interchanged, then  $l_1$  and  $100 - l_2$  get interchanged.

The balance point of the bridge will be  $100 - l_1$  from A.

$$100 - l_1 = 100 - 39.5 = 60.5 \text{ cm}$$

∴ The balance point is 60.5 cm from A.

c) When the galvanometer and cell are interchanged at the balance point of the bridge, the galvanometer will show no deflection. Hence, no current would flow through the galvanometer.

$$3.11 \quad E = 8.0 \text{ V}$$

$$M = 0.5 \Omega$$

$$V = 120 \text{ V}$$

$$R = 15.5 \Omega$$

∴ Voltage in the circuit =  $V'$

$R$  is connected to the storage battery in series. Hence,

$$V' = V - E$$

$$V' = 120 - 8 = 112 \text{ V}$$

Current flowing in the circuit =  $I$ ,  
so,

$$I = \frac{V'}{R + M}$$

$$= \frac{112}{15.5 + 0.5} = \frac{112}{16} = 7 \text{ A}$$

$$\text{Voltage across resistor } R \Rightarrow IR = 7 \times 15.5 = 108.5 \Omega$$

$$\text{Terminal voltage of battery} = 120 - 108.5 = 11.5 \text{ V}$$

A series resistor in a charging circuit limits the current drawn from the external source. The current will be extremely high in its absence. This is very dangerous.

$$3-12 \quad E_1 = 1.25 \text{ V}$$

$$l_1 = 35 \text{ cm}$$

The cell is replaced by another cell of emf  $E_2$ .

$$l_2 = 63 \text{ cm}$$

The balance condition is given by -

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

$$E_2 = E_1 \times \frac{l_2}{l_1}$$

$$= 1.25 \times \frac{63}{35} = 2.25 \text{ V}$$

$\therefore$  Emf of the second cell =  $2.25 \text{ V}$

3-13 Number density of free electron in copper conductor,  $n = 8.5 \times 10^{28} \text{ m}^{-3}$

$$L = 300 \text{ m}$$

$$A = 200 \times 10^{-6} \text{ m}^2$$

$$I = 3.0 \text{ A}$$

Current carried by the wire :-

$$I = n e V_d$$

where,

$$e = \text{Electron charge} = 1.6 \times 10^{-19} \text{ C}$$

$$V_d = \text{Drift velocity} = \frac{\text{length of the wire (L)}}{\text{Time taken to cover (t)}}$$

So,

$$I = \frac{nAe}{t}$$

$$t = \frac{nAed}{I}$$

$$t = \frac{3 \times 8.5 \times 10^{28} \times 2 \times 10^{-6} \times 1.6 \times 10^{-19}}{3.0}$$

$$t = 2.7 \times 10^4 \text{ s}$$

$\therefore$  Time taken by an electron to drift from one end of the wire to the other is  $2.7 \times 10^4 \text{ s}$ .

3.14. Surface charge density of the earth,  $\sigma = 10^{-9} \text{ C/m}^2$   
Current over the entire globe,  $I = 1800 \text{ A}$

Radius of the earth,  $r = 6.37 \times 10^6 \text{ m}$

Surface area of the earth,

$$\begin{aligned} A &= 2\pi r^2 \\ &= 4\pi (6.37 \times 10^6)^2 \\ &= 5.09 \times 10^{14} \text{ m}^2 \end{aligned}$$

Charge on the earth's surface,

$$\begin{aligned} q &= \sigma \times A \\ &= 10^{-9} \times 5.09 \times 10^{14} \\ &= 5.09 \times 10^5 \text{ C} \end{aligned}$$

Time taken to neutralize the earth's surface = t,

$$I = \frac{q}{t}$$

So,

$$\frac{t}{I} = \frac{q}{I}$$

$$= \frac{5.09 \times 10^5}{1800} = 282.77 \text{ s}$$

$\therefore$  Time taken to neutralize the earth's surface = 282.77 s

(15) Number of secondary cells,  $n = 6$

Emf of each secondary cell;  $E = 200 \text{ V}$

Internal resistance of each cell  $\alpha$  cell,  $r = 0.015 \Omega$

Series resistor is connected to the combination of cells.

Resistance of the resistor,  $R = 8.5 \Omega$

Current drawn from the supply =  $I$ ,

$$I = \frac{nE}{R + nr}$$

$$= \frac{6 \times 200}{8.5 + 6 \times 0.015} \\ = \frac{1200}{8.59} = 1.39 \text{ A}$$

Terminal voltage,  $V = IR = 1.39 \times 8.5 = 11.87 \text{ A}$

$\therefore$  The current drawn from the supply is 1.39 A and terminal voltage is 11.87 A.

b) After a long use, emf of the secondary cell,  
 $E = 1.09 \text{ V}$

Internal resistance of the cell,  $r = 3.80 \Omega$

Max current

$$= \frac{E}{r} = \frac{1.09}{3.80} = 0.005 \text{ A}$$

Hence, max

$\therefore$  The max current drawn from the cell is 0.005 A. Since a large current is

Required to start the motor of a car, the cell cannot be used to start a motor.

306. Resistivity of aluminium  $\rho_{Al} = 2.63 \times 10^{-8} \Omega m$

Relative density of Al,  $d_1 = 2.7$

Let,  $l_1$  be the length of Al wire and  $m_1$  its mass.

Resistance of Al wire =  $R_1$ ,

Area of Al wire =  $A_1$ ,

Resistivity of Cu,  $\rho_{Cu} = 1.72 \times 10^{-8} \Omega m$

Relative density of Cu,  $d_2 = 8.9$

Let,  $l_2$  be the length of Cu wire and  $m_2$  be its mass.

Resistance of the copper wire =  $R_2$

Area of Cu wire =  $A_2$

The two relations can be written as

$$R_1 = \frac{\rho_1 l_1}{A_1} \quad \text{--- (1)}$$

$$R_2 = \frac{\rho_2 l_2}{A_2} \quad \text{--- (2)}$$

It is given that,

$$R_1 = R_2$$

$$\frac{\rho_1 l_1}{A_1} = \frac{\rho_2 l_2}{A_2}$$

and,  $l_1 = l_2$

$$\therefore \frac{\rho_1}{A_1} = \frac{\rho_2}{A_2}$$

$$\frac{A_1}{A_2} = \frac{\rho_2}{\rho_1}$$

$$= \frac{2.63 \times 10^{-8}}{1.72 \times 10^{-8}} = \frac{2.63}{1.72}$$

Mass of Al wire,

$$m_1 = V \times d \\ = A_1 l_1 \times d_1 \quad \dots \quad (3)$$

mass of Cu wire,

$$m_2 = V \times d \\ = A_2 l_2 d_2 \quad \dots \quad (4)$$

Dividing eqn (3)  $\div$  (4) by eqn (4).

$$\frac{m_1}{m_2} = \frac{A_1 l_1 d_1}{A_2 l_2 d_2}$$

$$\frac{m_1}{m_2} = \frac{A_1 l_1}{A_2 l_2} \quad \left. \begin{array}{l} \text{q. } l_1 = l_2 \\ \end{array} \right\}$$

$$\frac{m_1}{m_2} = \frac{2.63}{1.72} \times \frac{2.7}{8.9} = 0.46$$

$\therefore$  From this relation we get to know that  $m_1$  is less than  $m_2$ . Hence, Al is lighter than copper.

$\therefore$  Aluminium-Aluminium is lighter and preferred for over head power supply cables over copper.

Q.7 It can be inferred from the given table that the ratio of voltage with current is a constant, which is equal to 19.7. Hence, manganin is an ohmic conductor i.e., the alloy obey Ohm's law. According to ohm's law, the ratio of voltage with current is the resistance of the conductor. Hence, the resistance of manganin is 19.7  $\Omega$ .

3018 a) When a steady current flows in a metallic conductor of non-uniform cross-section, the current flowing through the conductor is constant. Current density, electric field, and drift speed are inversely proportional to the area of cross-section. Therefore, they are not constant.

b) No, Ohm's law is not universally applicable for all conducting elements. Vacuum diode semi-conductor is a non-ohmic conductor.

c) According to Ohm's law, the relation for the potential is  $V = IR$   
Voltage ( $V$ ) is directly proportional to current ( $I$ )

$R$  is the internal resistance of the source

$$I = \frac{V}{R}$$

If  $V$  is low, then  $R$  must be very low, so that high current can be drawn from the source.

d) In order to prohibit the current from exceeding the safety limit, a high tension supply must have a very large internal resistance. If the internal resistance is not large, then the current drawn can exceed the safety limits in case of a short circuit.

319 a) Alloys of metals usually have greater resistivity than than of their constituent metals.

b) Alloys usually have much lower temperature coefficients of resistance than pure metals.

c) The resistivity of the alloy, manganin, is nearly independent of increase of temperature.

d) The resistivity of a typical insulator is greater than that of a metal by a factor of the order of  $10^{22}$ .

(20) Total number of resistors =  $n$

Resistance of each resistor =  $R$ .

i) When  $n$  resistors are connected in series, effective resistance  $R_s$  is the maximum given by the product  $nR$ .

Hence, maximum resistance of the combination,  
 $R_s = nR$ .

ii) When  $n$  resistors are connected in parallel, the effective resistance ( $R_p$ ) is the minimum, given by the ratio  $\frac{R}{n}$ .

Hence minimum resistance of the combination,  $R_p = \frac{R}{n}$


The ratio of the maximum to the minimum resistance is,

$$\frac{R_1}{R_2} = \frac{1R}{\frac{R}{n}} = n^2$$

b) The resistance of the given resistors is,


$$R_1 = 1 \Omega, R_2 = 2 \Omega, R_3 = 3 \Omega$$

i)  $R_{eq} = \frac{11}{3} \Omega$

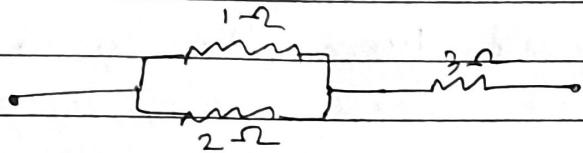


$$R_{eq} = \frac{2 \times 1}{2+1} + 3 = \frac{2}{3} + 3 = \frac{11}{3}$$

ii)  $R_{eq} = \frac{11}{5} \Omega$

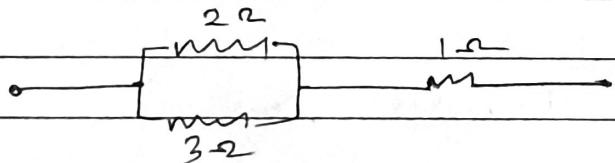

$$R_{eq} = \frac{2 \times 3}{2+3} + 1 = \frac{6}{5} + 1 = \frac{11}{5} \Omega$$


iii)  $R_{eq} = 6 \Omega$

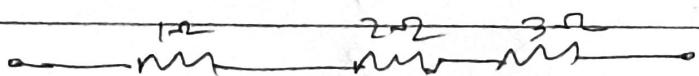

$$R_{eq} = R_1 + R_2 + R_3 = 1+2+3 = 6 \Omega$$


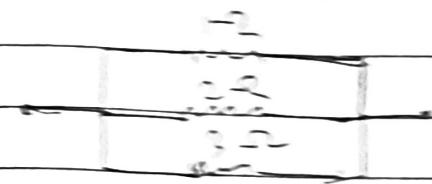
$$(i) \text{Req} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$



$$\text{Req} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2} = \frac{6 \times 2}{6 + 2} = \frac{12}{8} = 1.5 \Omega$$

$$\text{Req} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$


(ii) It can be observed from the given circuit that in the first small loop, two resistors of  $2\Omega$  each are connected in series.

$$\text{So, } \text{Req} = 1 + 1 = 2 \Omega$$

Also, two resistors of  $2\Omega$  each are also connected in series.

$$\text{So, } \text{Req} = 2 + 2 = 4 \Omega$$


$\therefore$  Circuit can be drawn as

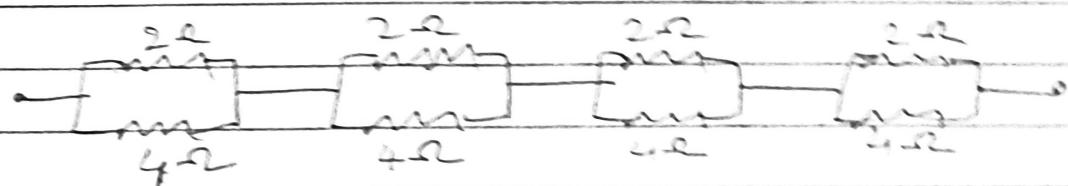

Now, for the 1st loop :-

$$\text{Req} = \frac{2 \times 4}{2 + 4} = \frac{8}{6} = \frac{4}{3} \Omega$$

Now, the circuit  $\rightarrow$

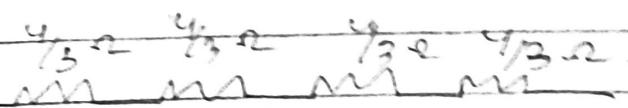


$$\text{Now, } \text{Req} = 4 \times \frac{4}{3} = \frac{16}{3} \Omega$$

b) In the given circuit all the resistors are connected in series.

So,

$$R_{eq} = R + R + R + R + R - \\ = 5R$$

3.21.

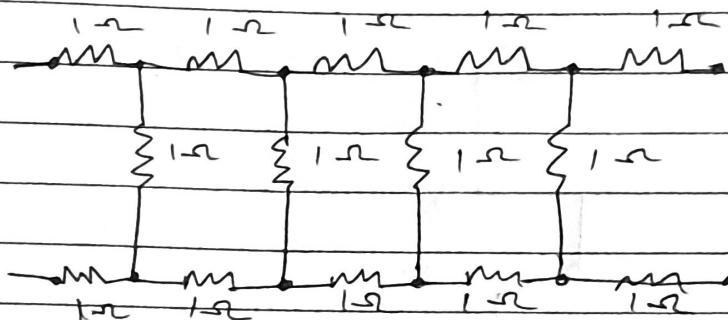

The resistance of each resistor,  $R = 1\Omega$

The network is infinite

$$R_{eq} = 2 + \frac{R_{in}}{(R_{eq} + 1)}$$

$$(R_{eq})^2 - 2R_{eq} - 2 = 0$$

$$R_{eq} = \frac{2 \pm \sqrt{4 + 8}}{2}$$

$$= \frac{2 \pm \sqrt{12}}{2} = 1 \pm \sqrt{3}$$

Negative value of  $R_{eq}$  can not be accepted.

So,

$$R_{eq} = (1 + \sqrt{3}) = 1 + 1.73 = 2.73\Omega$$


Internal resistance of the circuit,  $r_i = 0.5\Omega$

$$\text{Total resistance} = 2.73 + 0.5 = 3.23\Omega$$

Current drawn from the circuit,  $I = \frac{V}{R}$

$$= \frac{12}{3.23}$$

$$= 3.72 \text{ A}$$

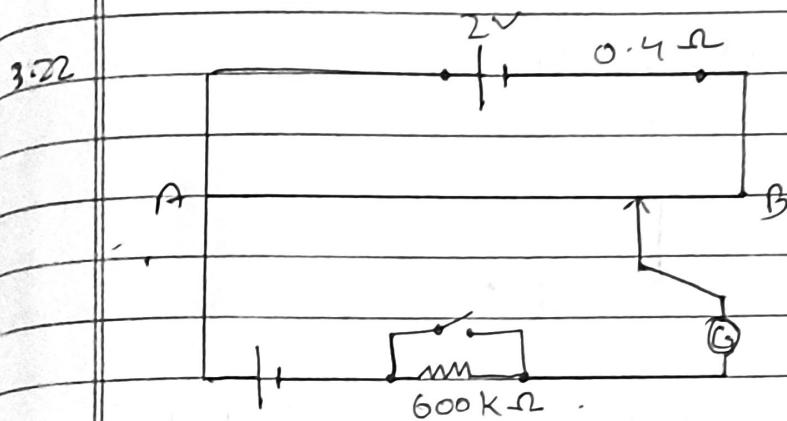

a) Emf of the cell,  $E_1 = 1.02 \text{ V}$

$$l_1 = 67.3 \text{ cm}$$

$$l_2 = 82.3 \text{ cm}$$

so,

$$\frac{E_1}{l_1} = \frac{E_2}{l_2}$$

$$E_2 = \frac{l_2}{l_1} E_1$$


$$= \frac{82.3}{67.3} \times 1.02 = 1.247 \text{ V}$$

b) The purpose of using the high resistance of 600 k ohm is to reduce the current through the galvanometer

c) The balance point is not affected by the presence of high resistance.

- d) The point is not affected by the internal resistance of the driver cell.
- e) The method would not work if the driver cell of the potentiometer had an emf of 1.0v instead of 2.0v. This is because if the emf of the driver cell of the potentiometer is less than the emf of the other cell, then there would be no balance point on the curve.
- f) The circuit would not work well for determining an extremely small emf. As the circuit would be unstable, the balance point would be close to end A. Hence, there would be a large percentage of error.

3.0.23

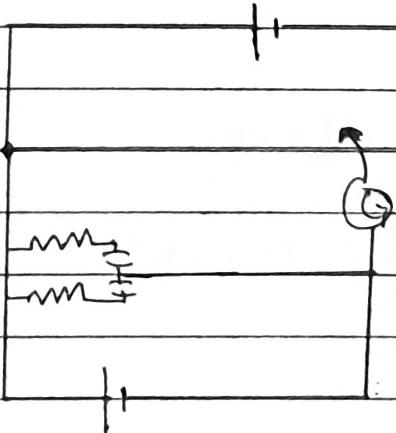

$$R = 10.0 \Omega$$

$$l_1 = 58.3 \text{ cm}$$

$$\text{current} = i$$

$$\text{P.D across } R, E_1 = iR$$

$$\text{Resistance of unknown resistor} = x$$

$$l_2 = 68.5 \text{ cm}$$

$$\text{P.D across } x, E_2 = ix$$

So,

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$


$$\frac{i_x R}{i_x} = \frac{l_1}{l_2}$$

$$x = \frac{l_1}{l_2} R$$

$$= \frac{68.5}{58.3} \times 10 = 11.749 \Omega$$

∴ Value of unknown resistor  $x = 11.75 \Omega$

3024.

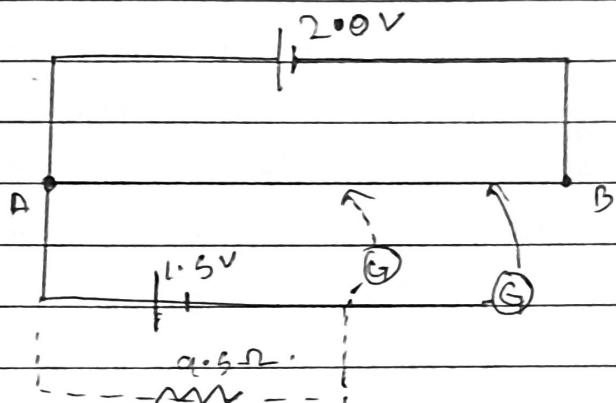

Internal resistance of cell =  $r$ .

$$l_1 = 76.3 \text{ cm}$$

External resistance  $iR = 9.5 \Omega$

$$l_2 = 64.8 \text{ cm}$$

Current =  $I$ .

$$r = \left( \frac{l_1 - l_2}{l_1} \right) R$$

$$= \frac{76.3 - 64.8}{76.3} \times 9.5 = 1.68 \Omega$$

$\therefore r$

∴ Resistance of the cell =  $1.68 \Omega$