

H.W

Homework

1.

In Bulb 1,

$$P = 50W$$

$$V = 220V$$

we know,

$$R = \frac{V^2}{P} = \frac{220 \times 220}{50}$$

$$R_1 = 968 \Omega$$

Bulb 2,

$$P = 100W$$

$$V = 220V$$

$$R = \frac{V^2}{P} = \frac{220 \times 220}{100}$$

$$R_2 = 484 \Omega$$

c) In Series

i will be same for both

$$P = i^2 R$$

$$P \propto R$$

So 50W will glow brighter.

c) In Parallel connection

V across both bulb will be same

as,

$$P = \frac{V^2}{R}$$

$$P \propto \frac{1}{R}$$

So, bulb with Resistance will glow brighter, i.e. $R_2 = 484 \Omega$
i.e. 100W.

2. Given,

$$P = 100W$$

$$V = 120V$$

$$R = ?$$

We know,

$$P = \frac{V^2}{R}$$

$$\text{So, } R = \frac{V^2}{P}$$

$$\Rightarrow R = \frac{14400}{100}$$

$$= 144 \Omega$$

3. (i) $P = V \times I$

$$P = 1500W$$

$$V = 250V$$

$$\therefore I = \frac{P}{V} = \frac{1500}{250} = 6A$$

(ii) Energy = $P \times t$

$$= 1500 \times 20$$

$$= 25000 \text{ W or J}$$

$$(iii) \text{ Total cost} = 15 \times 2.2 = 21 \text{ Rs}$$