

Ch-3 - Current Electricity

Exercises

8.1 $E = 12V$
 $r = 0.4\Omega$

$$E = P \cdot r$$

$$\Rightarrow 12 = P \cdot 0.4$$

$$\Rightarrow P = \frac{12}{0.4} = \frac{12 \times 10^3}{4} = 30A$$

8.2 $E = 10V$
 $r = 8\Omega$
 $P = 0.5A$

$$P = \frac{E}{R+r}$$

$$R+r$$

$$\Rightarrow 0.5 = \frac{10}{R+8}$$

$$\Rightarrow 0.5(R+8) = 10$$

$$\Rightarrow 0.5R + \frac{5}{2} \times 8 = 10$$

$$\Rightarrow 0.5R = 10 - \frac{3}{2}$$

$$\Rightarrow 0.5R = \frac{20-3}{2} = \frac{17}{2}$$

$$\Rightarrow R = \frac{17}{2} \times \frac{10^3}{5} = 17\Omega$$



3.3 a) 

$$\text{Total resistance} = 1\Omega + 2\Omega + 3\Omega \\ = 6\Omega$$

b) $\mathcal{E} = 12V$

$$R = 6\Omega$$

$$\Rightarrow \mathcal{I} = \frac{\mathcal{E}}{R}$$

$$\Rightarrow \mathcal{I} = \frac{12}{6} = 2A$$

Potential drop across 1Ω resistor $= V_1 = 2 \times 1 = 2V$

Potential drop across 2Ω resistor $= V_2 = 2 \times 2 = 4V$

Potential drop across 3Ω resistor $= V_3 = 2 \times 3 = 6V$

3.4. a) $R_1 = 2\Omega$

$R_2 = 4\Omega$

$R_3 = 5\Omega$

$$\Rightarrow \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\Rightarrow \frac{1}{R_p} = \frac{1}{2} + \frac{1}{4} + \frac{1}{5}$$

$$\Rightarrow \frac{1}{R_p} = \frac{2+1+2}{4} + \frac{1}{5}$$

$$\Rightarrow \frac{1}{R_p} = \frac{15+4}{20}$$

$$\Rightarrow \frac{1}{R_p} = \frac{19}{20} \Omega$$

$$\Rightarrow R_p = \frac{20}{19} \Omega$$

$$64 \quad E = 20V$$

$$R = \frac{20}{19} \Omega$$

$$D = \frac{E}{R} = \frac{20}{\frac{20}{19}} = 20 \times \frac{19}{20} = 19A$$

Current through 2Ω resistor = V

$$(D_1) \quad R_1$$

$$= \frac{20}{2} = 10A$$

Current through 4Ω resistor = V

$$(D_2) \quad R_2$$

$$= \frac{20}{4} = 5A$$

Current through 5Ω resistor = V = $20/5 = 4A$

$$(D_3) \quad R_3 \quad 5\Omega$$

$$\text{Total Current} = D_1 + D_2 + D_3$$

$$= 10A + 5A + 4A$$

$$= 19A$$

$$3.5 \quad T = 27^\circ C$$

$$R = 100 \Omega$$

$$R_1 = 117 \Omega$$

$$\alpha = 1.7 \times 10^{-4} / ^\circ C$$

$$\Rightarrow \alpha = \frac{R_1 - R}{R(T_1 - T)}$$

$$\Rightarrow T_1 - T = \frac{R_1 - R}{R\alpha}$$

$$R_1 = R [1 + \alpha (T_1 - T)]$$

$$117 = 100 [1 + 1.7 \times 10^{-4} (T_1 - 27)]$$

$$117 = 100 + 1.7 \times 10^{-2} (T_1 - 27)$$

$$\Rightarrow T_1 - 27 = \frac{117 - 100}{100(1.7 \times 10^{-4})}$$

$$\Rightarrow T_1 - 27 = \frac{17}{10^{-4}}$$

$$\Rightarrow T_1 - 27 = 1000$$

$$\Rightarrow T_1 = 1000 + 27$$

$$T_1 = 1027^\circ\text{C}$$

3.6 $A = 6.0 \times 10^{-7} \text{ m}^2$

$$l = 15 \text{ m}$$

$$R = 5.0 \Omega$$

$$\Rightarrow R = \frac{\rho l}{A}$$

$$\Rightarrow 5 = \frac{\rho \cdot 15}{6 \times 10^{-7}}$$

$$\Rightarrow 5 \times 6 \times 10^{-7} = 15 \rho$$

$$\Rightarrow \rho = \frac{15 \times 10^{-7}}{15}$$

$$= 2 \times 10^{-7} \Omega \text{ m}$$

3.7 $R_1 = 2.1 \Omega$

$$T_1 = 27.5^\circ\text{C}$$

$$R_2 = 2.7 \Omega$$

$$T_2 = 100^\circ\text{C}$$

$$\alpha = \frac{R_2 - R_1}{R_1(T_2 - T_1)} = \frac{2.7 - 2.1}{2.1(100 - 27.5)} = \frac{0.6}{210 - 57.75} = 0.0039^\circ\text{C}^{-1}$$

8.8

$$V = 230 \text{ V}$$

$$I_1 = 3.2 \text{ A}$$

$$I_2 = 2.8 \text{ A}$$

$$\alpha = 1.7 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}$$

$$T_1 = 27.0^\circ\text{C}$$

$$R_1 = \frac{V}{I_1} = \frac{230}{3.2} = 71.87 \text{ } \Omega$$

$$R_2 = \frac{V}{I_2} = \frac{230}{2.8} = 82.14 \text{ } \Omega$$

$$\Rightarrow \alpha = \frac{R_2 - R_1}{R_1(T_2 - T_1)}$$

$$\Rightarrow 1.7 \times 10^{-4} = \frac{82.14 - 71.87}{71.87(T_2 - 27)}$$


$$\Rightarrow 1.7 \times 10^{-4} = \frac{10.27}{71.87T_2 - 71.87(T_2 - 27)}$$

$$\Rightarrow T_2 - 27 = \frac{10.27}{71.87 \times 1.7 \times 10^{-4}}$$

$$\Rightarrow T_2 - 27 = 840.5$$

$$\Rightarrow T_2 = 840.5 + 27 = 867.5^\circ\text{C}$$

3.9

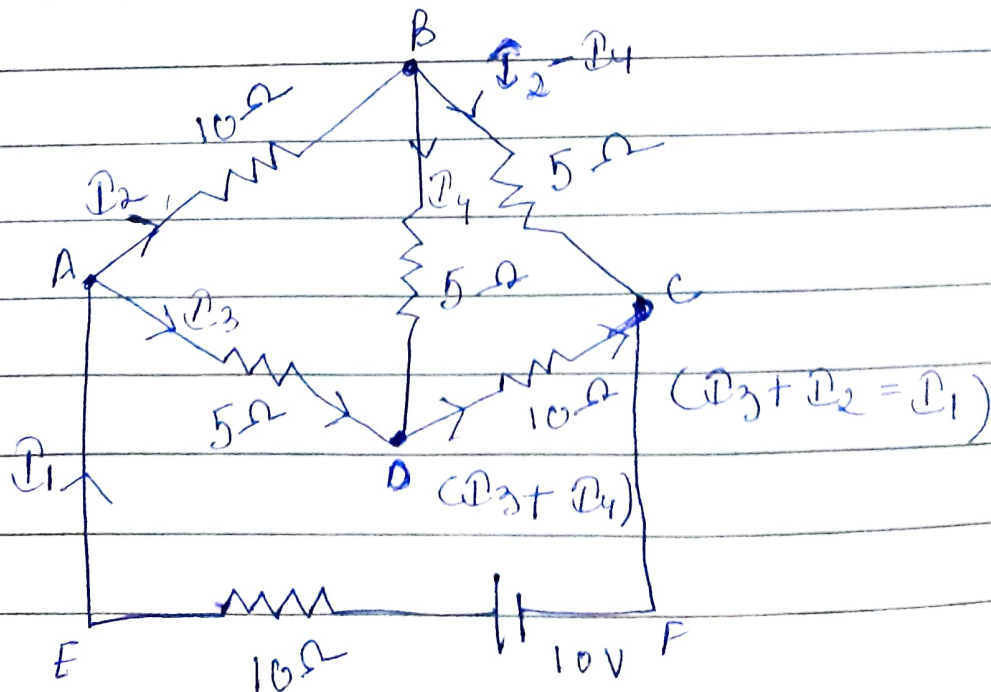

For ABCDA, $10P_2 + 5P_4 - 5(P_3) = 0$

$\Rightarrow 10P_2 + 5P_4 - 5P_3 = 0$

$\Rightarrow 5(2P_2 + P_4 - P_3) = 0$

$\Rightarrow 2P_2 + P_4 - P_3 = 0$

$\Rightarrow P_3 = 2P_2 + P_4$ — (i)

For BCDB,

$\Rightarrow 5(P_2 - P_4) - 10(P_3 + P_4) - 5P_4 = 0$

$\Rightarrow 5P_2 - 5P_4 - 10P_3 - 10P_4 - 5P_4 = 0$

$\Rightarrow 5P_2 - 10P_3 - 20P_4 = 0$

$\Rightarrow 5(P_2 - 2P_3 - 4P_4) = 0$

$\Rightarrow P_2 = 2P_3 + 4P_4$ — (ii)

For ABCFEA,

$\Rightarrow -10 + 10P_2 + 5(P_2 - P_4) + 10P_1 = 0$

$\Rightarrow -10 + 10P_2 + 5P_2 - 5P_4 + 10P_1 = 0$

$\Rightarrow 15P_2 + 10P_1 - 5P_4 = 10$

$\Rightarrow 5(3P_2 + 2P_1 - P_4) = 10$

$\Rightarrow 3P_2 + 2P_1 - P_4 = \frac{10}{5} = 2$

$\times 1$

$\Rightarrow 3P_2 + 2P_1 - P_4 = 2$ — (iii)

From eq (i), (ii), (iii), we get :-

$P_3 = 2P_2 + P_4$

$\Rightarrow P_3 = 2(2P_3 + 4P_4) + P_4$


$\Rightarrow P_3 = 4P_3 + 8P_4 + P_4$

$\Rightarrow -3P_3 = 9P_4$

$\Rightarrow P_3 = \frac{9P_4}{-3} = -3P_4$

$\times 1$

$\Rightarrow P_3 = -3P_4$ — (iv)

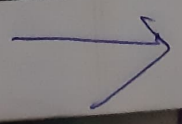

Putting eq (IV) in (I), we get =

$$\begin{aligned} I_3 &= 2I_2 + I_4 \\ \Rightarrow -3I_4 &= 2I_2 + I_4 \\ \Rightarrow -2I_2 &= I_4 + 3I_4 \\ \Rightarrow -2I_2 &= 4I_4 \\ \Rightarrow I_2 &= \frac{4I_4}{-2} = -2I_4 \\ \Rightarrow I_2 &= -2I_4 \quad \text{--- (V)} \end{aligned}$$

$$I_1 = I_3 + I_2 \quad \text{--- (VI)}$$

Putting eq (V) in eq (III), we get =

$$\begin{aligned} \Rightarrow I_3 &= 2I_2 + I_4 \quad 3I_2 + 2I_1 - I_4 = 2 \\ \Rightarrow 3I_2 + 2(I_3 + I_2) - I_4 &= 2 \\ \Rightarrow 3I_2 + 2I_3 + 2I_2 - I_4 &= 2 \\ \Rightarrow 5I_2 + 2I_3 - I_4 &= 2 \quad \text{--- (VII)} \end{aligned}$$

Putting eq (V) and (V) in eq (VII), we get =

$$\begin{aligned} 5I_2 + 2I_3 - I_4 &= 2 \\ \Rightarrow 5(-2I_4) + 2(-3I_4) - I_4 &= 2 \\ \Rightarrow -10I_4 - 6I_4 - I_4 &= 2 \\ \Rightarrow -17I_4 &= 2 \\ \Rightarrow I_4 &= \frac{2}{-17} \end{aligned}$$

$$\text{In eq (IV), } I_3 = -3I_4 = -3 \times \frac{2}{-17} = \frac{6}{17} \text{ A}$$

$$\text{In eq (V), } I_2 = -2I_4 = -2 \times \frac{2}{-17} = \frac{4}{17} \text{ A}$$

$$I_1 = I_3 + I_2$$

$$= \frac{6}{17} + \frac{4}{17} = \frac{10}{17} \text{ A}$$

$$I_2 - I_4 = \frac{4}{17} - \left(\frac{2}{17} \right) = \frac{4}{17} - \frac{2}{17} = \frac{2}{17} \text{ A}$$

$$I_3 + I_4 = \frac{6}{17} + \left(\frac{2}{17} \right) = \frac{6}{17} + \frac{2}{17} = \frac{8}{17} \text{ A}$$


$$I \text{ in branch AB} = \frac{4}{17} \text{ A}$$

$$I \text{ in branch BC} = \frac{6}{17} \text{ A}$$

$$I \text{ in branch CD} = \frac{4}{17} \text{ A}$$

$$I \text{ in branch AD} = \frac{6}{17} \text{ A}$$
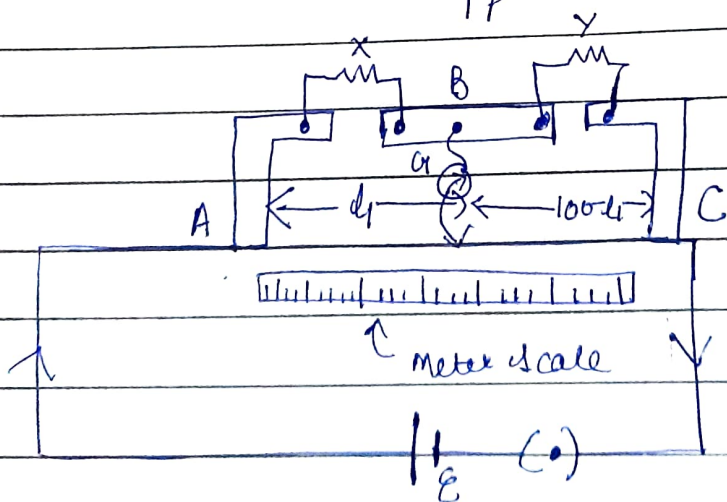
$$I \text{ in branch BD} = -\frac{2}{17} \text{ A}$$



$$d_1 = 39.5 \text{ cm}$$

$$R \text{ of } Y = 12.5 \Omega$$

$$\frac{X}{Y} = \frac{100 - d_1}{d_1} \Rightarrow X = \frac{100 - 39.5}{39.5} \times 12.5 = \frac{60.5}{39.5} \times 12.5$$

$$\Rightarrow X = \frac{605}{395} \times \frac{125}{100} \times \frac{10}{10} = 8.2 \Omega$$

b) Balance point of the bridge = $100 - d_1$
 $= 100 - 39.5$
 $= 60.5 \text{ cm from A}$

c) When the galvanometer and cell are interchanged at the balance point of the bridge, the galvanometer will show no deflection and therefore no current will pass through the galvanometer.

3.11

$$E = 8.0 \text{ V}$$

$$V = 120 \text{ V}$$

$$r = 0.5 \Omega$$

$$R = 15.5 \Omega$$

$$V' = V - E$$

$$= 120 - 8 = 112 \text{ V}$$

$$I = \frac{V'}{R + r} = \frac{112}{15.5 + 0.5} = \frac{112}{16} = 7 \text{ A}$$

$$V = IR = 7 \times 15.5 = 108.5 \text{ V}$$

$$\text{Terminal voltage} = 120 - 108.5 = 11.5 \text{ V}$$

3.12

$$E_1 = 1.25 \text{ V}$$

$$d_1 = 35 \text{ cm}$$

$$d_2 = 63 \text{ cm}$$

$$\frac{E_1}{E_2} = \frac{d_1}{d_2} \Rightarrow \frac{1.25}{E_2} = \frac{35}{63} \Rightarrow E_2 = \frac{1.25 \times 63}{35}$$

$$E_0 = 2.25 \text{ V}$$

$$8.13 \quad n = 8.5 \times 10^{28} \text{ m}^{-3}$$

$$d = 3 \text{ m}$$

$$A = 2 \times 10^{-6} \text{ m}^2$$

$$I = 3 \text{ A}$$

$$\Rightarrow I = neAv_d$$

$$\Rightarrow 3 = 8.5 \times 10^{28} \times 1.6 \times 10^{-19} \times 2 \times 10^{-6} \times v_d$$

$$\Rightarrow 3 = 8.5 \times 10^{28} \times 1.6 \times 10^{-19} \times 2 \times 10^{-6} \times \frac{d}{t}$$

$$\Rightarrow t = \frac{8.5 \times 10^{28} \times 1.6 \times 10^{-19} \times 2 \times 10^{-6} \times 3}{3}$$

$$\Rightarrow t = \frac{85}{10} \times 10^{28} \times \frac{16}{10} \times \frac{1}{10^{19}} \times \frac{2}{10^6} \times \frac{1}{10^6}$$

$$= 2720 \times 10^{28}$$

$$= 27200 \text{ s}$$

$$= 2.7 \times 10^4 \text{ s}$$

$$8.14 \quad \sigma = 10^{-9}$$

$$I = 1800 \text{ A}$$

$$v_e = 6.37 \times 10^6 \text{ m/s}$$

$$A = 4\pi v_e^2$$

$$= 4 \times 3.14 \times (6.37 \times 10^6)^2$$

$$= 4 \times \frac{314}{100} \times \frac{637}{100} \times 10^6 \times \frac{637}{100} \times 10^6$$

$$= 5.69 \times 10^{14} \text{ cm}^2$$

$$q = \sigma \times A$$

$$q = 10^{-19} \times 5.09 \times 10^{14}$$

$$= \frac{1}{10^{19}} \times \frac{5.09}{100} \times 10^{14}$$

$$= 5.09 \times 10^5 \text{ C}$$

$$P = \frac{q}{t}$$

$$\Rightarrow 1800 = \frac{5.09 \times 10^5}{t}$$

$$\Rightarrow t = \frac{5.09 \times 10^5}{1800}$$

$$t = 282.77 \text{ s}$$

3.15 a) $\mathcal{E} = 2.0 \text{ V}$
 $r = 0.015 \text{ } \Omega$
 $R = 8.5 \text{ } \Omega$

$$n = 6$$

$$P = \frac{n\mathcal{E}}{R + nr}$$

$$P = \frac{6 \times 2}{8.5 + 6 \times 0.015} = \frac{12}{8.59} = 1.39 \text{ A}$$

$$V = IR = 1.39 \times 8.5 = 11.87 \text{ V}$$

b) $\mathcal{E} = 1.9 \text{ V}$

$$r = 380 \text{ } \Omega$$

$$P = \frac{\mathcal{E}}{r} = \frac{1.9}{380} = 0.005 \text{ A}$$

The cell cannot be used to start a motor as a charge \rightarrow

Current is required to start the motor of a car.

3.16

$$\rho_{Al} = 2.63 \times 10^{-8} \Omega m$$

$$d_{Al} = 2.7$$

$$\rho_{Cu} = 1.72 \times 10^{-8} \Omega m$$

$$d_{Cu} = 8.9$$

$$R_{Al} = \rho_{Al} \frac{l_{Al}}{A_{Al}}$$

$$R_{Cu} = \rho_{Cu} \frac{l_{Cu}}{A_{Cu}}$$

ATQ,

$$R_{Al} = R_{Cu}$$

$$\Rightarrow \rho_{Al} \frac{l_{Al}}{A_{Al}} = \rho_{Cu} \frac{l_{Cu}}{A_{Cu}}$$

$$\Rightarrow \frac{\rho_{Al}}{A_{Al}} = \frac{\rho_{Cu}}{A_{Cu}} \quad (A_{Al} l_{Al} = l_{Cu})$$

$$\Rightarrow \frac{A_{Al}}{A_{Cu}} = \frac{\rho_{Cu}}{\rho_{Al}}$$

$$= \frac{2.63 \times 10^{-8} \Omega m}{1.72 \times 10^{-8} \Omega m} = \frac{2.63}{1.72}$$

$$m_{Al} = \text{volume} \times \text{density} \\ = A_{Al} l_{Al} \times d_{Al}$$

$$m_{Cu} = \text{volume} \times \text{density} \\ = A_{Cu} l_{Cu} \times d_{Cu}$$

$$\frac{m_{Al}}{m_{Cu}} = \frac{A_{Al} d_{Al}}{A_{Cu} d_{Cu}}$$

$$d_1 = d_2, \quad \frac{m_{Al}}{m_{Cu}} = \frac{A_{Al} d_{Al}}{A_{Cu} d_{Cu}}$$

$$\frac{m_{Al}}{m_{Cu}} = \frac{2.63}{1.72} \times \frac{2.7}{8.9} = 0.46 \quad \left(\frac{A_{Al}}{A_{Cu}} = \frac{2.63}{1.72} \right)$$

lesser

Here m_{Al} is lighter than m_{Cu} . So, aluminium is lighter than copper and hence, it is preferred for overhead power cables over copper.

3.17 From the given table, it is observed that the ratio of voltage with current is a constant i.e. 19.7. Hence, manganese is an ohmic conductor i.e. the alloy obeys Ohm's law. According to Ohm's law, the ratio of voltage with current is the resistance of the conductor. Hence, the resistance of manganese is 19.7 Ω .

3.18 a) When a ^{steady} current flows in a metallic conductor of non-uniform cross-section, the current flowing through a conductor is constant. Current density, electric field, drift speed are inversely proportional to the area of cross section hence they are not constant.

b) No, Ohm's law is not universally accepted applicable for all the conducting elements. Vacuum diode semiconductor is a non-ohmic conductor. Therefore, Ohm's law is not valid for it.

→

27 According to Ohm's law, $V = IR$ i.e. Voltage V is directly proportional to current I and internal resistance R .

$$I = \frac{V}{R}$$

If V is const, then R must be very low, so that high current can be drawn from the source.

28 In order to prevent the current from exceeding the safety limit, a high tension supply must have a very large internal resistance. If the internal resistance is not large, then the current drawn can exceed the safety limits in case of a short circuit.

3.19 ^{of metals} Alloys usually have much greater resistivity than that of their constituent metals.

29 Alloys usually have much lower temperature coefficient of resistance than pure metals.

30 The resistivity of the alloy manganin is nearly independent of increase of temperature.

31 The resistivity of a typical insulator is greater than that of a metal by a factor of the order of 10^{22} .

3.20 a) Total no. of resistors = n
resistance of each resistor = R

b) When we will combine the n resistors in series, R_1 resistance is the maximum ^{resistance} given by $R_1 = nR$ we will get

ii) When we combine the n resistors in parallel, we will obtain R_2 resistance as the minimum resistance given by $R_2 = \frac{R}{n}$


iii) Ratio of maximum to minimum = $R_1 : R_2$
 $= \frac{nR}{R}$
 $= n$

$$R_1 : R_2 = nR \times \frac{n}{R}$$

$$R_1 : R_2 = n^2$$

6) $R_1 = 1\Omega, R_2 = 2\Omega, R_3 = 3\Omega$

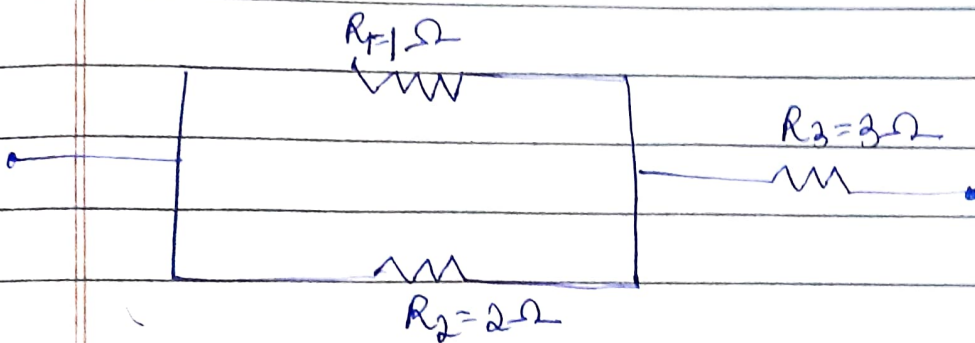ii) Equivalent resistance, $R_e = \frac{11}{3}\Omega$



$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{1} + \frac{1}{2} = \frac{2+1}{2} = \frac{3}{2}$$

$$R_p = \frac{2}{3}$$

$$R_e = R_p + R_3$$

$$= \frac{2}{3} + 3 = \frac{2+9}{3} = \frac{11}{3}\Omega$$

ii) Equivalent resistance, $R_e = \frac{11}{3}\Omega$


$$\frac{1}{R_p} = \frac{1}{2} + \frac{1}{3} = \frac{3+2}{6} = \frac{5}{6} \Omega, R_p = \frac{6}{5}$$

$$R_e = R_p + R_1$$

$$R_e = \frac{6}{5} + 1 = \frac{6+5}{5} = \frac{11}{5} \Omega$$

$$= \frac{5+6}{5} = \frac{11}{5}$$

iii) $R_e = 6 \Omega$

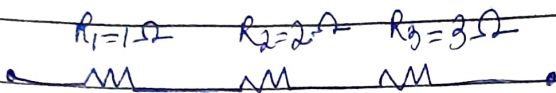


$$R_e = R_1 + R_2 + R_3$$

$$R_e = 1\Omega + 2\Omega + 3\Omega$$

$$R_e = 6\Omega$$

iv) $R_e = 6 \Omega$

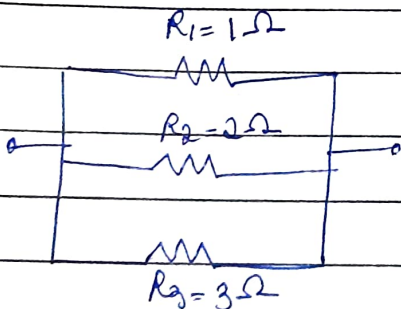

$$\frac{1}{R_p} = \frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_e} = \frac{1}{1} + \frac{1}{2} + \frac{1}{3}$$


$$\frac{1}{R_e} = \frac{6+3+2}{6} = \frac{11}{6}$$

$$R_e = \frac{6}{11} \Omega$$


||



10/6

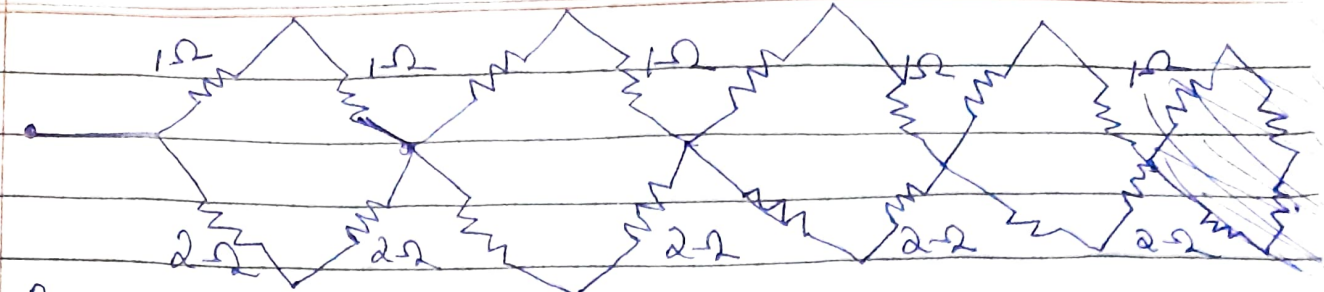
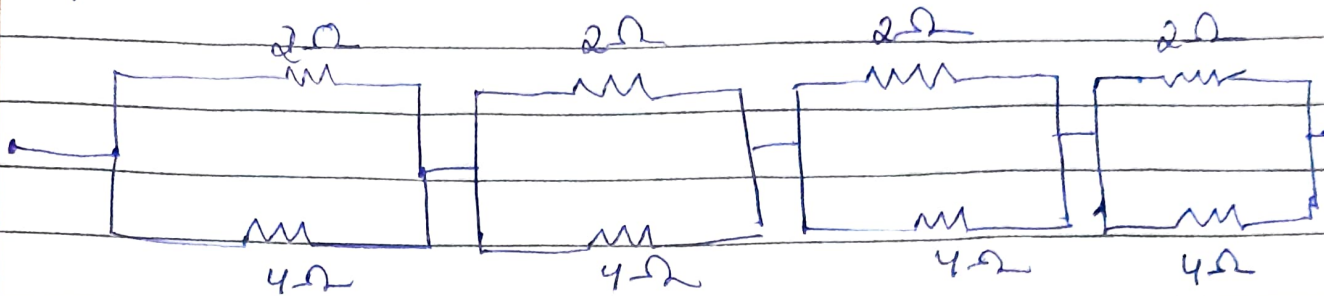
$$R_{s1} = 1 + 1 = 2\Omega \quad R_{s2} = 2 + 2 = 4\Omega$$



$$\frac{1}{R_p} = \frac{1}{2} + \frac{1}{4} = \frac{2+1}{4} = \frac{3}{4}$$

$$R_p = \frac{4}{3}\Omega$$



$$R_{se} = \frac{4}{3}\Omega + \frac{4}{3}\Omega + \frac{4}{3}\Omega + \frac{4}{3}\Omega$$

$$R_{se} = \frac{4 + 4 + 4 + 4}{3} = \frac{16}{3}$$

$$R_{se} = \frac{16}{3}\Omega$$

$$\text{Equivalent resistance} = \frac{16}{3}\Omega$$

3.21 $R = 10\Omega$

$R_{eq} \Rightarrow$ Equivalent resistance

$$R_{eq} = 2 + \frac{R_{eq}}{R_{eq} + 1}$$

$$\Rightarrow R_{eq} = 2R_{eq} - 2 = 0$$

$$\Rightarrow R_{eq} = \frac{2 \pm \sqrt{4+8}}{2} = \frac{2 \pm \sqrt{12}}{2} = 1 \pm \sqrt{3}$$

Date: / /
Page No.:

$$R_{eq} = (1 + \sqrt{3}) = 1 + 1.73 = 2.73 \Omega$$

$$R = 0.5 \Omega$$

$$R_{eq} = R_{eq} + 0.5$$
$$= 2.73 + 0.5$$
$$= 3.23 \Omega$$

$$V = 10V$$

we know,

$$P = \frac{V}{R}$$

$$I = \frac{10}{3.23} = 3.12A$$

3.22 a) $E_1 = 1.02V$

$$d_1 = 67.3 \text{ cm}$$

$$d = 82.3 \text{ cm}$$

$$\Rightarrow \frac{E_1}{d_1} = \frac{E}{d}$$

$$\Rightarrow \frac{1.02}{67.3} = \frac{E}{82.3}$$

$$\Rightarrow E = \frac{1.02 \times 82.3}{67.3} = 1.247V$$

b) The purpose of using the high resistance of $600k \Omega$ to reduce the current through the galvanometer when the movable contact is far from the balance point.

c) No, the balance point is not affected by this high resistance.

→

Date: / /
Page:

Q4 No, the method would not work if the driver cell of the potentiometer had an emf of 1.0 V instead of 2.0 V because if the emf of the driver cell of the potentiometer is less than the emf of the other cell, then there would be no balance point on the wire.

Q.23

$$l_1 = 76.3 \text{ cm}$$

$$R = 9.5 \Omega$$

$$l_2 = 64.8 \text{ cm}$$

$$\begin{array}{r} 76.3 \\ -64.8 \\ \hline 11.5 \end{array}$$

$$x = \left(\frac{l_1 - l_2}{l_2} \right) R$$

$$x = \frac{76.3 - 64.8}{64.8} \times 9.5 = 1.68 \Omega$$