

1. $\text{emf} = 12 \text{ V}$
 $r = 0.4 \Omega$

$$V = IR$$

$$12 = I \times 0.4$$

$$I = \frac{12}{0.4}$$

$$I = \frac{12 \times 10}{4}$$

$$= 30 \text{ A}$$

2. $\text{emf} = 10 \text{ V}$
 $r = 3 \Omega$ (internal resistance)
current in the circuit is 0.5 A

$$V = IR$$

$$10 = 0.5 \times R$$

$$R = \frac{10}{0.5}$$

$$R = \frac{10 \times 10}{5}$$

$$R = 20 \Omega$$


$$\text{Total } R = (20 - 3) \Omega$$
$$= 17 \Omega$$

$$V = IR$$

$$= 17 \times \frac{5}{10}$$

$$= 8.5 \text{ V}$$

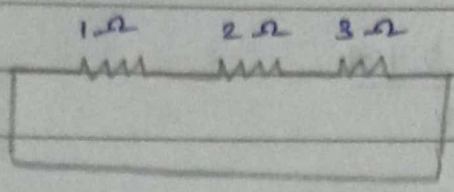3. (a) Three resistors 1Ω , 2Ω and 3Ω are combined in series.



(Sol.) Total resistance $(R) = (1 + 2 + 3)\Omega$
 $= 6\Omega$

(b) $V = IR$

Total $R = 6\Omega$

$V = 12V$

$V = IR$

$12 = I \times 6$

$I = 2A$


Voltage through the resistors:

$V(1) = 1 \times 2$
 $= 2V$

$V(2) = 2 \times 2$
 $= 4V$

$V(3) = 2 \times 3$
 $= 6V$

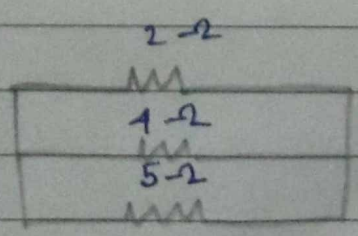4. Three resistors 2Ω , 4Ω and 5Ω are combined in parallel.



$$\frac{1}{R} = \frac{1}{2} + \frac{1}{4} + \frac{1}{5}$$

$$= \frac{10 + 5 + 4}{20}$$

$$= \frac{19}{20}$$

$$= \frac{20}{19} \Omega$$

(b) $V = IR$

$V = 20V$

Total resistance = $\frac{20}{19} \Omega$

$$20 = I \times \frac{20}{19}$$

$$I = \frac{20 \times 19}{20}$$

$$I = 19A$$

$$V(2) = 19 \times 2 = 38V$$

$$V(4) = 19 \times 4 = 76V$$

$$V(5) = 19 \times 5 = 95V$$

$$V = IR$$
$$38 = I \times \frac{20}{19}$$

$$I = \frac{38 \times 19}{20}$$

current for 2- Ω resistor

$$V = IR$$
$$20 = I \times 2$$
$$I = \frac{20}{2}$$

$$I = 10A$$

current for 4- Ω resistor

$$V = IR$$
$$20 = I \times 4$$
$$I = 5A$$

current for 5- Ω resistor

$$V = IR$$
$$20 = I \times 5$$
$$I = 4A$$

5. Resistance = 100Ω
temp = 27.0°C

$$R_t = 117^\circ\text{C}$$

$$\alpha = 1.70 \times 10^{-4} / ^\circ\text{C}$$

$$\alpha = \frac{R_t - R_{27}}{R_{27} (t - 27)}$$

$$t - 27 = \frac{17}{100 \times 1.70 \times 10^{-4}}$$

$$t = 1000 + 27$$

$$= 1027^\circ\text{C}$$

6. $L = 15 \text{ m}$

$$A = 6.0 \times 10^{-7} \text{ m}^2$$

$$R = 5.0 \Omega$$

$$R = \rho \frac{L}{A}$$

$$\rho = \frac{R A}{L}$$

$$= \frac{5 \times 6.0 \times 10^{-7}}{15}$$

$$= 2 \times 10^{-7} \Omega \text{ m}$$

$$7. R_{27.5} = 2.1 \Omega$$

$$R_{100} = 2.7 \Omega$$

$$\alpha = \frac{R_{100} - R_{27.5}}{R_{27.5} (100 - 27.5)}$$

$$= \frac{2.7 - 2.1}{2.1 (72.5)}$$

$$= \frac{0.6}{2.1 (72.5)}$$

$$= 0.0039 / ^\circ\text{C}$$

$$8. \text{Potential difference} = 230 \text{ V}$$

$$I_{27^\circ\text{C}} = 3.2 \text{ A}$$

$$I_{t^\circ\text{C}} = 2.8 \text{ A}$$

$$\text{Room Temp.} = 27^\circ\text{C}$$

$$\alpha = 1.70 \times 10^{-4} / ^\circ\text{C}$$

$$R = \frac{V}{I}$$

$$R_{27^\circ\text{C}} = \frac{2300 \Omega}{32} \quad R_{t^\circ\text{C}} = \frac{2300 \Omega}{28}$$

$$\alpha = 1.70 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}$$

$$\alpha = \frac{2800}{28} - \frac{2800}{32}$$

$$\frac{2300}{32} \quad (t-32)$$

$$1.70 \times 10^{-4} = \frac{82.143 - 71.875}{71.875 \times 9.9 \quad (t-32)}$$


$$t-32 = \frac{82.143 - 71.875}{71.875 (1.70 \times 10^{-4})}$$

$$t-32 = 840.347$$

$$t = 840.3 + 32$$

$$t = 867.3^\circ\text{C}$$

9.

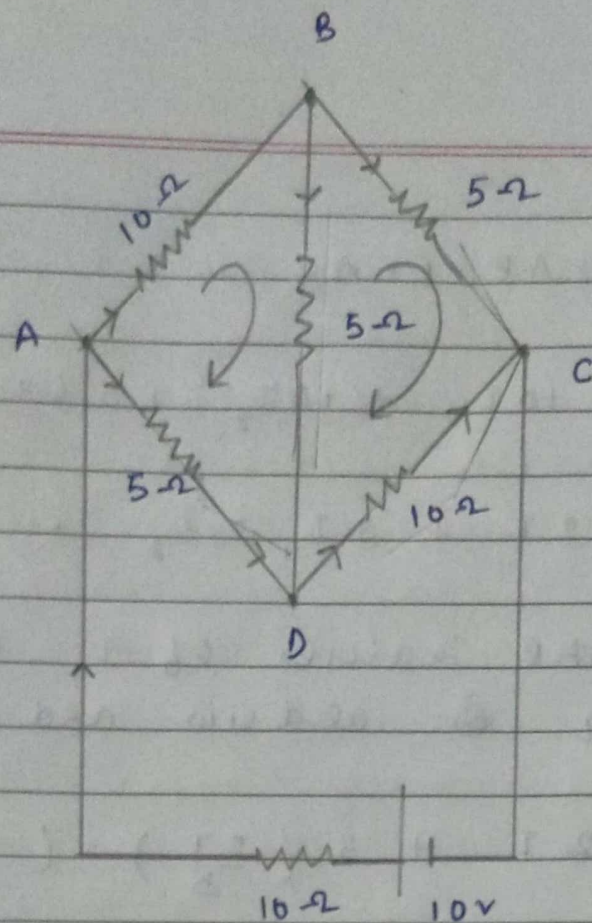

In loop ABDA

$$10 I_1 + 5 I_2 - 5 (I - I_1) = 0$$

$$2 I_1 + I_2 - I - I_1 = 0$$

$$I_1 + I_2 - I = 0 \quad \dots (i)$$

In loop BCDB

$$5 (I_1 - I_2) - 10 (I - I_1 + I_2) - 5 I_2 = 0$$

$$5 I_1 - 5 I_2 - 10 I + 10 I_1 - 10 I_2 - 5 I_2 = 0$$

$$3 I_1 - 4 I_2 = 2 I \quad \dots (ii)$$

$$I_1 = \frac{2 I}{5} \quad I_2 = -\frac{I}{5} \quad \dots (iii)$$

In loop ABCEFA

$$10 = 10I + 10I_2 + 5(I_1 - I_2)$$

$$2 = 2I + 3I_1 - I_2 \quad \dots (iv)$$

Putting the values of I_1 and I_2 from eq. (i) and (iv)

$$2 = 2I + 3\left(\frac{2I}{5}\right) - \left(-\frac{I}{5}\right)$$

$$2 = \frac{17}{5}I$$

$$I = \frac{10}{17} \text{ A}$$

Current in branch AB,

$$I_1 = \frac{2}{5} \times \frac{10}{7}$$

$$= \frac{4}{17} \text{ A}$$

$$I_2 = -\frac{1}{5}$$

$$= -\frac{2}{17} \text{ A}$$

Current in branch AB is $I_1 = \frac{4}{17} \text{ A}$

Current in branch BC is $I_1 - I_2$

$$= \frac{4}{17} + \frac{2}{17} = \frac{6}{17} \text{ A}$$

Current in branch AD is $I - I_1$,

$$= \frac{10}{17} - \frac{4}{17}$$

$$= \frac{6}{17} \text{ A}$$

Current in branch DC is $(I - I_1) + I_2$

$$= \frac{6}{17} - \frac{2}{17}$$

$$= \frac{4}{17} \text{ A}$$

10.

(a) $L = 39.5 \text{ cm}$

~~$R = 12.5 \Omega$~~

Resistance $y = 12.5$

Resistance $x = ?$

$$\frac{x}{y} = \frac{L}{100 - L}$$

$$x = \frac{L}{100 - L} \times y$$

$$= \frac{39.5 \times 12.5}{100 - 39.5}$$

$$= 8.16 \Omega$$


Date _____
Page _____

In meter bridge, the resistance at the connections is not taken in the consideration that's why the connections between resistors in a wheatstone bridge or meter bridge made of thick copper stripes because more is the thickness lower be the resistance. due to thick copper stripes, the resistance at the connections becomes minimum.

(b) If x and y are interchanged, then the balance length will also be interchanged. Thus, the balance becomes

$$100 - 39.5 = 60.5 \text{ cm}$$

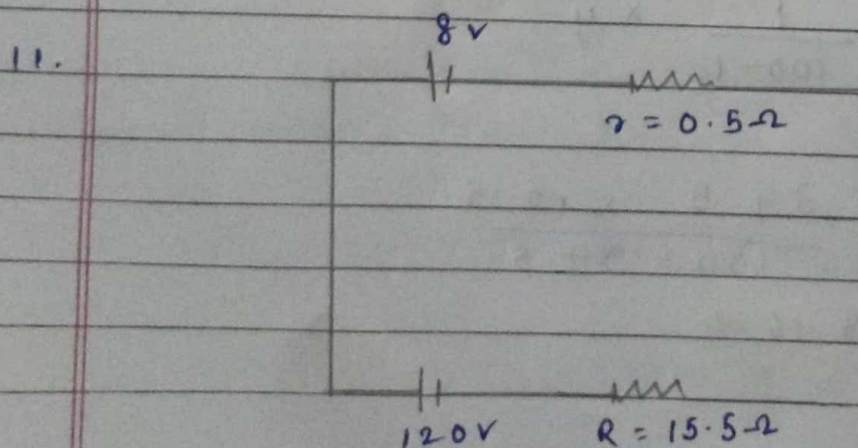(c) If the galvanometer and cell are interchanged at the balance point of the bridge, the balanced point is not obtained. The galvanometer shows no deflection.



Emf of the battery = 8V

emf of DC supply $V = 120V$

Since, the battery is being charged,
so effective emf in the circuit

$$\begin{aligned} E &= V - e \\ &= 120 - 8 \\ &= 112V \end{aligned}$$

Current in circuit

$$I = \frac{E}{R + r}$$

$$I = \frac{112}{0.5 + 15.5}$$

$$I = \frac{112}{16}$$

$$= 7A$$

The battery of 8V is being charged by 120V, so the terminal potential across battery of 8V will be greater than its emf.

$$\begin{aligned} \text{Terminal potential difference } V &= E + Ir \\ &= 8 + 7(0.5) \\ &= 11.5V \end{aligned}$$

The purpose of the series resistor is to control the current drawn from the external supply, otherwise the current in the circuit will be very high.

12. $E_1 = 1.25 \text{ V}$

$$L_1 = 35 \text{ cm}$$

$$L_2 = 63 \text{ cm}$$

$$\frac{E_1}{E_2} = \frac{L_1}{L_2}$$

$$\frac{1.25}{E_2} = \frac{35}{63}$$

$$\frac{1.25 \times 63}{35} = E_2$$

$$E_2 = 2.25 \text{ V}$$

13. $n = 8.5 \times 10^{28} / \text{m}^3$

$$L = 3 \text{ m}$$

$$I = 3 \text{ A}$$

$$e = 1.67 \times 10^{-19} \text{ C}$$

$$t = \frac{I}{v_d}$$

$$I = n e A v_d$$

$$v_d = \frac{I}{n e A}$$

$$t = \frac{L n e A}{I}$$

$$= \frac{3 \times 8.5 \times 10^{28} \times 1.6 \times 10^{-19} \times 2 \times 10^{-6}}{3}$$

$$t = 2.72 \times 10^1 \text{ s}$$