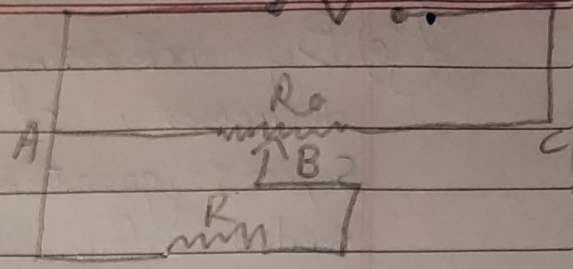


29.6.21

Ch-3 Home assignment

1) Let R_1 be the equivalent resistance betⁿ A & B i.e


$$R_1 = \frac{R_0/2 \times R}{R_0/2 + R} = \frac{R R_0}{R_0 + 2R}$$



Let R_{eq} be the resultant of R_1 & $\frac{R_0}{2}$ i.e $R_{eq} = R_1 + \frac{R_0}{2}$


$$R_{eq} = \frac{R R_0}{R_0 + 2R} + \frac{R_0}{2}$$
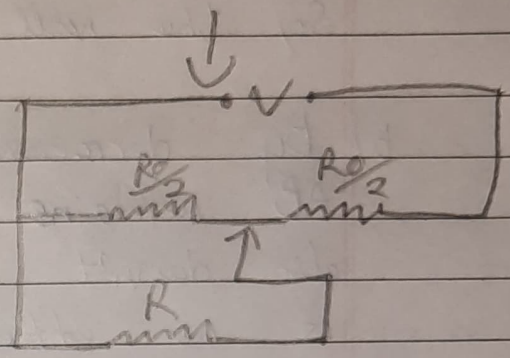
$$\Rightarrow R_{eq} = \frac{2R_1 + R_0}{2}$$




Current in the circuit, $I = \frac{V}{R_{eq}}$
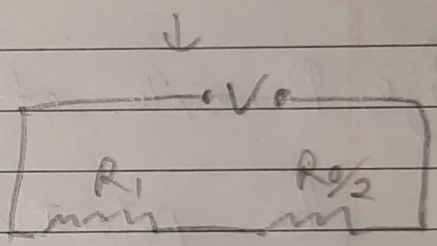
$$I = \frac{V}{\frac{2R_1 + R_0}{2}} = \frac{2V}{2R_1 + R_0}$$



Voltage across $R = V_{AB} =$ Voltage across R_1

$$R_1 = I R_1$$

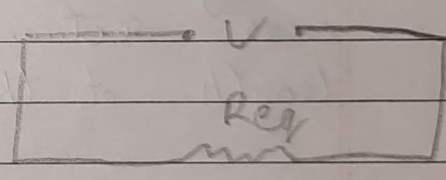

$$V_{AB} = \frac{2V}{2R_1 + R_0} \times \frac{R R_0}{R_0 + 2R}$$

$$= \frac{2V}{\frac{2R R_0}{R_0 + 2R} + R_0} \times \frac{R R_0}{R_0 + 2R} = \frac{2V (R_0 + 2R)}{R_0 (2R + R_0 + 2R)} \times \frac{R R_0}{R_0 + 2R}$$

$$= \frac{2VR}{4R + R_0}$$

So, Voltage across R_0

$$= \frac{2VR}{4R + R_0}$$

2) a) By increasing R , the current through AB decreases, so potential gradient decreases. So, a greater length of wire would be needed for balancing the same potential diff. So, the null point would shift towards B .

b) By decreasing resistance S , the current through AB remains the same, & potential gradient also doesn't change as K_2 is open, so there is no effect of S on null point.

3) a) Principle of potentiometer:

The potential drop across the length of a steady current carrying wire of uniform cross section is proportional to the length of the wire.


i) We use a long wire to have a lower value of potential gradient i.e. a greater sensitivity of the potentiometer.

ii) The area of cross section has to be ~~greater~~ uniform to get a 'uniform wire' as per the principle of potentiometer.

iii) The emf of the driving cell has to be greater than the emf of the primary cells as ~~no~~ otherwise no balance point would be obtained.

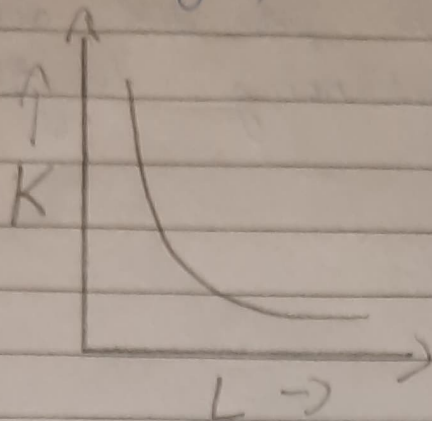b) Potential gradient, $K = V/L$

The required graph is shown below \rightarrow



- 4) a) The purpose of high resistance R_2 is to protect the galvanometer by decreasing the current through it for positions which are far away from balance point.
- b) When resistance R_1 is increased, the current through potentiometer wire circuit decreases. Due to it, potential gradient across it decreases. As a result, the balance point shift towards the end B.
- 4) When ~~emf~~ emf E is greater than $2V$, the balance point can not be obtained because the potential drop across the potentiometer wire will be less than $2V$.
- 2) When the key K is closed, the cell emf E gets short circuited. Due to it, the balance point is not obtained on the potentiometer wire.
- 5) a) If R_1 is decreased, current increases as a result potential gradient increases, so the balancing length would decrease.

b) When R_2 is increased, current decreases as a result terminal pot. diffⁿ across the cell increases. So the balancing length would increase.