

14.7.21

NCERT EXERCISES

Current Electricity



3.1) $E = 12 \text{ V}$
 $r = 0.4 \Omega$

$$I_{\text{max}} = \frac{E}{r} = \frac{12}{0.4} = 30 \text{ A}$$

3.2) $E = 10 \text{ V}$
 $r = 3 \Omega$
 $I = 0.5 \text{ A}$

$$\frac{E}{R+r} = I$$

$$\Rightarrow \frac{E}{I} = R+r \Rightarrow \frac{E}{I} - r = R$$

$$\Rightarrow R = \frac{10 \text{ V}}{0.5 \text{ A}} - 3 \Omega$$

$$\Rightarrow R = 20 - 3 = 17 \Omega$$

Terminal Voltage, $V = E - Ir$

$$= 10 - 0.5(3)$$

$$= 10 - 1.5 = 8.5 \text{ V}$$

3.3) a) $R_1 = 1 \Omega$ $R_2 = 2 \Omega$ $R_3 = 3 \Omega$

$$R_{\text{eq}} = R_1 + R_2 + R_3 = 1 + 2 + 3 = 6 \Omega$$

b) Emf, $E = 12 \text{ V}$

$$I = \frac{E}{R_{\text{eq}}} = \frac{12}{6} = 2 \text{ A}$$

Potential drop across each resistor is \Rightarrow

$$V_1 = IR_1 = 2 \times 1 = 2V$$

$$V_2 = IR_2 = 2 \times 2 = 4V$$

$$V_3 = IR_3 = 2 \times 3 = 6V$$

3.4) $R_1 = 2\Omega$ $R_2 = 4\Omega$ $R_3 = 5\Omega$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$= \frac{1}{\frac{1}{2} + \frac{1}{4} + \frac{1}{5}} = \frac{10 + 5 + 4}{20} = \frac{19}{20}$$

$$R_{eq} = \frac{20}{19} \Omega$$

b) Emf, $E = 20V$

$$I_{total} = \frac{E}{R_{eq}} = \frac{20}{\frac{20}{19}} = 19A$$

$$I_1 = \frac{E}{R_1} = \frac{20}{2} = 10A$$

$$I_2 = \frac{E}{R_2} = \frac{20}{4} = 5A$$

$$I_3 = \frac{E}{R_3} = \frac{20}{5} = 4A$$

3.5) $T_0 = 27^\circ C$

$T = ?$

$R_0 = 100\Omega$

$R_T = 117\Omega$

$$\alpha = 1.70 \times 10^{-4} \text{ } ^\circ C^{-1}$$

$$R = R_0 [1 + \alpha (T - T_0)]$$

$$\Rightarrow \cancel{100} \ 1.17 \ \Omega = 100 \ \Omega (1 + 1.70 \times 10^{-4} \text{ } ^\circ\text{C}^{-1} (T - 27^\circ\text{C}))$$

$$\Rightarrow 1.17 \ \Omega = 1 + 1.70 \times 10^{-4} \text{ } ^\circ\text{C}^{-1} (T - 27^\circ\text{C})$$

$$\Rightarrow 0.17 = 1.70 \times 10^{-4} \text{ } ^\circ\text{C}^{-1} (T - 27^\circ\text{C})$$

$$\Rightarrow \frac{0.17}{1.70 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}} = T - 27^\circ\text{C}$$

$$\Rightarrow \frac{1}{10^{-3} \text{ } ^\circ\text{C}^{-1}} = T - 27^\circ\text{C}$$

$$\Rightarrow 10^3 \text{ } ^\circ\text{C} = T - 27^\circ\text{C} \Rightarrow 1000 + 27 = T \Rightarrow T = 1027^\circ\text{C}$$

3.6) $l = 15 \text{ m}$ $I \approx 0$
 $A = 6.0 \times 10^{-7} \text{ m}^2$
 $R = 5 \ \Omega$

We know that, $R = \frac{\rho l}{A}$

$$\Rightarrow \rho = \frac{RA}{l} = \frac{5 \times 6^2 \times 10^{-7}}{153} = 2 \times 10^{-7} \ \Omega \text{ m}$$

3.7) $R_0 = 2.1 \ \Omega$ $T_0 = 27.5^\circ\text{C}$
 $R_T = 2.7 \ \Omega$ $T = 100^\circ\text{C}$
 $\alpha = ?$

We know that, $R_T = R_0 (1 + \alpha (T - T_0))$

$$\Rightarrow 2.7 \Omega = 2.1 \Omega (1 + \alpha (100 - 27.5)^\circ\text{C})$$

$$\Rightarrow \frac{2.7}{2.1} = 1 + \alpha \times 72.5$$

$$\Rightarrow \frac{2.7}{2.1} - 1 = \alpha \times 72.5$$

$$\Rightarrow \frac{2.7 - 2.1}{2.1 \times 72.5^\circ\text{C}} = \alpha \quad \Rightarrow \alpha = \frac{0.2}{0.6} = 2 \times 10^{-1}$$

$$= \frac{2 \times 10^2}{7 \times 72.5} = \frac{200}{507.5} = \frac{100}{253.75^\circ\text{C}}$$

$$= \frac{1}{253.75^\circ\text{C}}$$

$$= \frac{100}{25375} = 0.0039^\circ\text{C}^{-1}$$

$$\text{So, } \alpha = 0.0039^\circ\text{C}^{-1}$$

$$3.8) \quad V = 230\text{V} \quad T_0 = 27^\circ\text{C} \quad \alpha = 1.7 \times 10^{-4}^\circ\text{C}^{-1}$$

$$I_0 = 3.2\text{A}$$

$$R_0 = \frac{V}{I_0} = \frac{230}{3.2} = \frac{2300}{32} = 71.87 \Omega$$

$$I_T = 2.8\text{A}$$

$$R_T = \frac{230}{2.8} = \frac{2300}{28} = 82.14$$

$$R_T = R_0 (1 + \alpha (T - T_0))$$

$$\Rightarrow 82.14 = 71.87 (1 + 1.7 \times 10^{-4} (T - 27))$$

$$\frac{82.14 - 1}{71.87} = 1.7 \times 10^{-4} \text{ } ^\circ\text{C}^{-1} (T - 27^\circ\text{C})$$

$$\frac{1.1428 - 1}{1.7 \times 10^{-4}} = T - 27$$

$$\Rightarrow \frac{0.1428}{1.7 \times 10^{-4}} = T - 27$$

$$\Rightarrow \frac{0.1428 \times 10^5}{17} = T - 27$$

$$\Rightarrow \frac{1428 \times 10^0}{17} = T - 27$$

$$\Rightarrow 84 \times 10^0 + 27 = T \Rightarrow T = 840 + 27 = 867^\circ\text{C}$$

~~$$\Rightarrow T = 840 + 27 = 850^\circ\text{C}$$~~

3.9) By applying Kirchoff's loop law:

i) in ABDA $\Rightarrow 0 = 10(I_1 - I_2) + 5(I_3) - 5(I_2)$


$$\Rightarrow 2I_1 - 2I_2 + I_3 - I_2 = 0$$

$$\Rightarrow 2I_1 - 3I_2 + I_3 = 0 \quad \text{--- (i)}$$

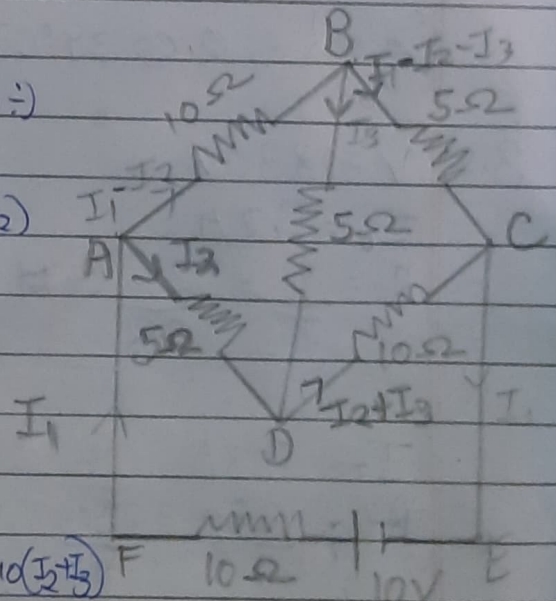ii) in BCDB $\Rightarrow 0 = 5(I_1 - I_2 - I_3) - 5I_3 - 10(I_2 + I_3)$

$$\Rightarrow I_1 - I_2 - I_3 - I_3 - 2I_2 - 2I_3 = 0$$

$$\Rightarrow I_1 - 3I_2 - 4I_3 = 0 \quad \text{--- (ii)}$$



iii) in ABC(EFA) $\Rightarrow 10 = 10I_1 + 10(I_1 - I_2) + 5(I_1 - I_2 - I_3)$

$$\Rightarrow 2 = 2I_1 + 2I_1 - 2I_2 + I_1 - I_2 - I_3$$

$$\Rightarrow 15I_1 - 3I_2 - I_3 = 2 \quad \text{--- (iii)}$$

Subtracting (ii) from (i)

$$2I_1 - 3I_2 + I_3 - I_1 + 3I_2 + 4I_3 = 0 - 0$$

$$= I_1 + 5I_3 = 0 \quad \text{--- (iv)}$$

Now, 2 (ii) from (iii) $\Rightarrow 5I_1 - 3I_2 - I_3 = 2$

$$-I_1 + 3I_2 + 4I_3 = 0$$

$$\hline 4I_1 \quad + 3I_3 = 2$$

~~$$4I_1 - 6I_2 - I_3 = 2$$~~

~~$$-2I_1 + 6I_2 + 8I_3 = 0$$~~

$$\Rightarrow 4I_1 + 3I_3 = 2$$

~~$$9I_1 \quad + 7I_3 = 2$$~~

~~$$\Rightarrow 8I_1 + I_3 = 2 \quad \text{--- (v)}$$~~

~~$$\Rightarrow 9I_1 + 7I_3 = 2 \quad \text{--- (v)}$$~~

Now subtracting (v) from 4(iv),

~~$$9I_1 + 45I_3 = 0$$~~

~~$$-9I_1 - 7I_3 = 2$$~~

~~$$\hline 42I_3 = -2$$~~

~~$$9I_1 + 20I_3 = 0$$~~

~~$$-4I_1 - 3I_3 = 2$$~~

~~$$\hline 17I_3 = -2$$~~

$$\Rightarrow \boxed{I_3 = \frac{-2}{17} \text{ A}}$$

~~$$\Rightarrow I_3 = \frac{-2}{42} = \frac{-1}{21}$$~~

Putting the value of I_3 in (iv) =

$$I_1 + 5I_3 = 0$$

$$\Rightarrow I_1 = -5I_3 = -5\left(\frac{-2}{17}\right) = \frac{10}{17}$$

$$\Rightarrow \boxed{I_1 = \frac{10A}{17}}$$

Putting the values of I_1 & I_3 in (i)

$$2I_1 - 3I_2 + I_3 = 0$$

$$\Rightarrow 3I_2 = 2I_1 + I_3 = 2\left(\frac{10}{17}\right) + \left(\frac{-2}{17}\right) = \frac{20}{17} - \frac{2}{17} = \frac{18}{17}$$

$$\Rightarrow I_2 = \frac{18}{17 \times 3} = \frac{6A}{17}$$

$$\Rightarrow \boxed{I_2 = \frac{6A}{17}}$$

Current flowing through :-

$$i) AB = I_1 - I_2 = \frac{10}{17} - \frac{6}{17} = \frac{4A}{17}$$

$$ii) AD = I_2 = \frac{6A}{17}$$

$$iii) BD = I_3 = \frac{-2A}{17}$$

$$iv) BC = I_1 - I_2 - I_3 = \frac{10}{17} - \frac{6}{17} - \left(\frac{-2}{17}\right) = \frac{6A}{17}$$

$$v) DC = I_2 + I_3 = \frac{6}{17} + \left(\frac{-2}{17}\right) = \frac{4A}{17}$$

Total Current
= ~~10A~~ $I_1 = \frac{10A}{17}$

a) 3.10) $L = 39.5 \text{ cm}$
 $Y = 12.5 \Omega$

$$\frac{X}{Y} = \frac{L}{100-L}$$

$$\Rightarrow \frac{X}{12.5} = \frac{39.5}{100-39.5} \quad \Rightarrow X = \frac{39.5 \times 12.5}{60.5} = 8.16 \Omega$$

Connections are made ~~at~~ by thick copper strips to minimise the resistances of connections which are not counted in the above formula.

b) If $X \leftrightarrow Y$, then $X = 12.5 \Omega$, $Y = 8.16 \Omega$

$$\frac{X}{Y} = \frac{L}{100-L}$$

$$\Rightarrow \frac{12.5}{8.16} = \frac{L}{100-L} \quad \Rightarrow 1.53 = \frac{L}{100-L}$$

$$\Rightarrow 1.53(100-L) = L \Rightarrow 153 - 1.53L = L$$

$$\Rightarrow L + 1.53L = 153$$

Balance point = 60.5 cm from A

$$\Rightarrow L(1+1.53) = 153$$

$$\Rightarrow L = \frac{153}{2.53} = 60.47 \approx 60.5 \text{ cm}$$

c) When the galvanometer & cell are interchanged at the balance point, the conditions of the balanced bridge are still satisfied, so again galvanometer will not show any current.

3.11) $E_{\text{ext}} = 8V$
 $r = 0.5\Omega$
 $V = 120V$
 $R = 15.5\Omega$

$$i = \frac{E_{\text{ext}}}{R_{\text{eq}}} = \frac{120 - 8}{15.5 + 0.5} = \frac{112}{16} = 7A$$

$$V_d = E + ir = 8 + 7(0.5) = 8 + 3.5 = 11.5V$$

The series resistor limits the current drawn from the ext. source. In its absence, the current will be extremely high.

3.12) $E_1 = 1.25V$ $E_2 = ?$
 $l_1 = 35\text{cm}$ $l_2 = 63\text{cm}$

We know that, $\frac{E_1}{E_2} = \frac{l_1}{l_2}$

$$\Rightarrow \frac{1.25}{E_2} = \frac{35}{63}$$

$$\Rightarrow E_2 = \frac{1.25 \times 63}{35} = 2.25V$$

3.13) $n = 8.5 \times 10^{28} \text{ m}^{-3}$
 $l = 3\text{m}$
 $A = 2 \times 10^{-6} \text{ m}^2$

$I = 3A$
 $e = 1.6 \times 10^{-19}C$

We know that, $I = enAv_d \Rightarrow V_d = \frac{I}{enA}$

$$=) \frac{V_d}{d} = \frac{3}{1.6 \times 10^{-19} \times 8.5 \times 10^{28} \times 2 \times 10^{-6}} = \frac{3}{1.6 \times 8.5 \times 2 \times 10^3}$$

$$= \frac{3}{27.2 \times 10^3}$$

$$= \frac{3}{272 \times 10^2} \frac{\text{m}}{\text{s}} = \frac{3}{272} \times 10^{-2}$$

~~2.1×10^{-4}~~

$$T = \frac{L}{V_d} = \frac{3}{\frac{3}{272 \times 10^2}} = 272 \times 10^2 = 2.72 \times 10^4 \text{ sec} \approx 7.5 \text{ hour.}$$

_____ X _____