

Ch-3  
Exercises

3.1)  $EMF(E) = 12\text{ V}$   
Internal resistance ( $R$ ) =  $0.4\ \Omega$

Then,  $E = IR$   
 $\Rightarrow I = \frac{E}{R}$

$I = \frac{12}{0.4}$   
 $= 30\text{ A}$

3.2)  $EMF = 10\text{ V}$   
Internal resistance ( $R$ ) =  $3\ \Omega$   
 $I = 0.5\text{ A}$

Then,  $I = \frac{E}{R+r}$

$\Rightarrow 0.5 = \frac{10}{3+r}$

$\Rightarrow 1.5 + 0.5r = 10$

$\Rightarrow 0.5r = 8.5$

$\Rightarrow r = \frac{8.5}{0.5}$   
 $= 17\ \Omega$

So,  $V = IR$

$= 0.5 \times 17$

$= 8.5\text{ V}$

$\therefore$  The terminal voltage of the battery is  $8.5\text{ V}$  when

the circuit is closed.

$$\begin{aligned} 3.3) \quad R_{eq} &= R_1 + R_2 + R_3 \\ &= 1 + 2 + 3 \\ &= 6 \Omega \end{aligned}$$

$$b) \quad \text{EMF} = 12 \text{ V}.$$

$$\begin{aligned} \text{Then, } I &= \frac{V}{R_{eq}} \\ &= \frac{12}{6} \\ &= 2 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{So, } V_1 &= IR_1 \\ &= 2 \times 1 \\ &= 2 \text{ V} \end{aligned}$$

$$\begin{aligned} V_2 &= IR_2 \\ &= 2 \times 2 \\ &= 4 \text{ V} \end{aligned}$$

$$\begin{aligned} V_3 &= IR_3 \\ &= 2 \times 3 \\ &= 6 \text{ V} \end{aligned}$$

∴ The potential drop across each resistor is 2V, 4V, and 6V respectively.

3.4)  $R_{eq} = \frac{1}{R_1}$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\Rightarrow \frac{1}{R_{eq}} = \frac{1}{2} + \frac{1}{4} + \frac{1}{5}$$

$$\Rightarrow \frac{1}{R_{eq}} = \frac{10+5+4}{20}$$

$$\Rightarrow \frac{1}{R_{eq}} = \frac{19}{20}$$

$$\Rightarrow R_{eq} = \frac{20}{19} \Omega.$$

b) EMF = 20V.

$$I_1 = \frac{V}{R_1}$$

$$= \frac{20 \cdot 10}{2}$$

$$= 10 \text{ A.}$$

$$I_2 = \frac{V}{R_2}$$

$$= \frac{20 \cdot 5}{4}$$

$$= 5 \text{ A.}$$

$$I_3 = \frac{V}{R_3}$$

$$= \frac{20}{5}$$

$$= 4 \text{ A.}$$

∴ The current through each resistor is 10 A, 5 A and 4 A respectively.

$$\text{Total current in circuit, } I = \frac{V}{R_{eq}}$$

$$= \frac{20}{\frac{20}{19}}$$

$$= 20 \times \frac{19}{20}$$

$$= 19 \text{ A.}$$

35) ~~Temp~~ Initial temperature ( $T$ ) =  $27^\circ\text{C}$ .

Resistance of the heating element at temp.  $T$   
=  $100 \Omega$ .

Let the increased temp. be  $T_1$ ,  
increased resistance =  $117 \Omega$ .

Coefficient of material of resistor ( $\alpha$ ) =  $1.7 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}$

So,

$$\alpha = \frac{R_1 - R}{R(T_1 - T)}$$

$$\Rightarrow 1.7 \times 10^{-4} = \frac{117 - 100}{100(T_1 - 27)}$$

$$\Rightarrow 1.7 \times 10^{-4} = \frac{17}{100T_1 - 2900}$$

$$\Rightarrow 100T_1 - 2900 = \frac{17 \cdot 10}{1.7 \times 10^{-4}}$$

$$\Rightarrow 100T_1 - 2900 = 10^5$$

$$\Rightarrow T_1 - 27 = 10^3$$

$$\Rightarrow T_1 = 1000 + 27 \\ = 1027^\circ \text{C}$$

3.c) ~~length~~ length of wire ( $l$ ) = 15 m.  
Cross-section area ( $A$ ) =  $6.0 \times 10^{-7} \text{ m}^2$   
Resistance ( $R$ ) =  $5 \Omega$ .

$$\text{Then, } R = \frac{\rho l}{A}$$

$$\Rightarrow 5 = \frac{\rho \times 15}{6 \times 10^{-7}}$$

$$\Rightarrow \frac{30 \times 10^{-7}}{15} = \rho$$

$$\Rightarrow \rho = 2 \times 10^{-7}$$

3.7) Resistance of silver wire ( $R$ ) =  $2.1 \Omega$   
 Temp. ( $T$ ) =  $27.5^\circ\text{C}$

At temp. ( $T_1$ ) =  $100^\circ\text{C}$ ,  
 Increased resistance ( $R_1$ ) =  $2.7 \Omega$ .

Then,  $\alpha = \frac{R_1 - R}{R(T_1 - T)}$   
 $= \frac{2.7 - 2.1}{2.1(100 - 27.5)}$   
 $= \frac{0.6}{2.1 \times 72.5}$   
 $= 0.0039^\circ\text{C}^{-1}$ .

3.8) Supply  $v = \text{Hage}(V) = 230 \text{ v}$ .

Initial current ( $I$ ) =  $3.2 \text{ A}$ .

Resistance ( $R$ ) =  $\frac{V}{I}$   
 $= \frac{230}{3.2}$   
 $= 71.875 \Omega$ .

~~find~~ Reduced current ( $I_1$ ) =  $2.8 \text{ A}$ .

Then, resistance ( $R_1$ ) =  $\frac{V}{I_1}$   
 $= \frac{230}{2.8}$

$$= 0.0445 \Omega$$

$$= 0.045 \Omega \text{ (approx.)}$$

Initial temp. ( $T$ ) =  $27^\circ\text{C}$  (Given)

Coefficient of material ( $\alpha$ ) =  $1.7 \times 10^{-4} \text{ }^\circ\text{C}^{-1}$  (Given)

$$\text{Then, } \alpha = \frac{R_1 - R}{R(T_1 - T)}$$

$$\Rightarrow 1.7 \times 10^{-4} = \frac{0.045 - 71.875}{71.875(T_1 - 27)}$$

$$\Rightarrow 1.7 \times 10^{-4} = \frac{82.142 - 71.875}{71.875(T_1 - 27)}$$

$$\Rightarrow 71.875(T_1 - 27) = \frac{10.267}{1.7 \times 10^{-4}}$$

$$\Rightarrow T_1 - 27 = \frac{10.267}{71.875 \times 1.7 \times 10^{-4}}$$

$$\Rightarrow T_1 = 840.265 + 27$$


$$= 867.265^\circ\text{C}$$

<sup>increased</sup>  
 $\therefore$  The temperature of the element is  $867.265^\circ\text{C}$

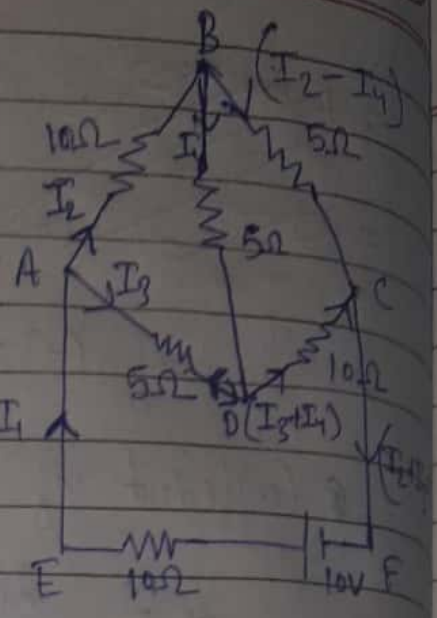3.9) Let the current through AB  $= I_2$

Similarly,  
the current through AD, BD, CD  
and BC are =

$I_3, I_4, I_3 + I_4$  and  $I_2 - I_4$  respectively.



In circuit ABDA,

$$10 I_2 + 5 I_4 - 5 I_3 = 0$$

$$\Rightarrow 2 I_2 + I_4 - I_3 = 0$$

$$\Rightarrow I_3 = 2 I_2 + I_4 \quad \text{--- (1)}$$

In circuit BCD, BCD,

$$5 (I_2 - I_4) - 10 (I_3 + I_4) - 5 I_4 = 0$$

$$\Rightarrow I_2 - I_4 - 2 (I_3 + I_4) - I_4 = 0$$

$$\Rightarrow I_2 - I_4 - 2 I_3 - 2 I_4 - I_4 = 0$$

$$\Rightarrow I_2 - 2 I_3 - 4 I_4 = 0$$

$$\Rightarrow I_2 = 2 I_3 + 4 I_4 \quad \text{--- (2)}$$



In circuit ABCFA,

$$-10 + 10I_1 + 10I_2 + 5(I_2 - I_4) = 0$$

$$\Rightarrow -10 + 10I_1 + 10I_2 + 5I_2 - 5I_4 = 0$$

$$\Rightarrow 10I_1 + 15I_2 - 5I_4 - 10 = 0$$

$$\Rightarrow 2I_1 + 3I_2 - I_4 - 2 = 0 \quad \text{--- (3)}$$

from eq. (1) and (2),

$$\begin{aligned} I_2 &= 2(2I_2 + I_4) + 4I_4 \\ &= 4I_2 + 2I_4 + 4I_4 \\ &= 2I_2 + I_4 + 2I_4 \\ &= 2I_2 + 3I_4 \quad \text{--- (4)} \end{aligned}$$

$$I_3 = 2(2I_3 + 4I_4) - I_4$$

$$\Rightarrow I_3 = 4I_3 + 8I_4 + I_4$$

$$\Rightarrow I_3 - 4I_3 = 9I_4$$

$$\Rightarrow -3I_3 = 9I_4$$

$$\Rightarrow I_3 = -3I_4 \quad \text{--- (5)}$$

Putting value of  $I_3$  obtained in eq. (1), in the equation (2),

$$I_2 = 2I_3 + 4I_4$$

$$\Rightarrow I_2 = 2(-3I_4) + 4I_4$$

$$\Rightarrow I_2 = -6I_4 + 4I_4$$

$$\Rightarrow I_2 = -2I_4 \quad \text{--- (5)}$$

Now, As  $I_1 = I_2 + I_3$

$$\Rightarrow I_1 = -2I_4 + (-3I_4)$$

$$= -5I_4 \quad \text{--- (6)}$$

Putting the values of  $I_1$  and  $I_2$  in eq. (3),

$$2I_1 + 3I_2 - I_4 - 2 = 0$$

$$\Rightarrow 2(-5I_4) + 3(-2I_4) - I_4 - 2 = 0$$

$$\Rightarrow -10I_4 - 6I_4 - I_4 = 2$$

$$\Rightarrow -17I_4 = 2$$

$$\Rightarrow I_4 = \frac{-2}{17} \text{ A.}$$

Now, putting the value of  $I_4$  in eq. (4) and (5),

$$\begin{aligned} I_3 &= -3I_4 \\ &= -3 \times \frac{-2}{17} \\ &= \frac{6}{17} \text{ A.} \end{aligned}$$

$$\begin{aligned} I_2 &= -2I_4 \\ &= -2 \left( \frac{-2}{17} \right) \\ &= \frac{4}{17} \text{ A.} \end{aligned}$$

$$\begin{aligned} I_1 &= -5I_4 \\ &= -5 \left( \frac{-2}{17} \right) \\ &= \frac{10}{17} \text{ A.} \end{aligned}$$

$$\begin{aligned} \text{Current in BC branch} &= I_2 - I_4 \\ &= \frac{4}{17} - \left( \frac{-2}{17} \right) \\ &= \frac{4}{17} + \frac{2}{17} \\ &= \frac{6}{17} \text{ A.} \end{aligned}$$

$$\begin{aligned} \text{Current in DC branch} &= I_3 + I_4 \\ &= \frac{6}{17} + \left( \frac{-2}{17} \right) \\ &= \frac{4}{17} \text{ A.} \end{aligned}$$

∴ Current in branches (FEA, AB, AD, BD, BC) are  $\frac{10}{17} \text{ A}$ ,  $\frac{4}{17} \text{ A}$ ,  $\frac{6}{17} \text{ A}$ ,  $\frac{-2}{17} \text{ A}$ ,  $\frac{6}{17} \text{ A}$  and  $\frac{10}{17} \text{ A}$  respectively.

~~3.10~~

3.10) a) Balance point is at 39.5 cm from A,

$$l_1 = 39.5 \text{ cm.}$$

$$100 - l_1 = 100 - 39.5 \\ = 60.5 \text{ cm.}$$

~~Given~~  $Y = 12.5 \Omega$  (Given)


According to the formula,

$$\frac{X}{l_1} = \frac{Y}{100 - l_1}$$

$$\Rightarrow \frac{X}{39.5} = \frac{12.5}{100 - 39.5}$$

$$\Rightarrow X = \frac{12.5 \times 39.5}{60.5}$$

$$= 8.16 \Omega.$$

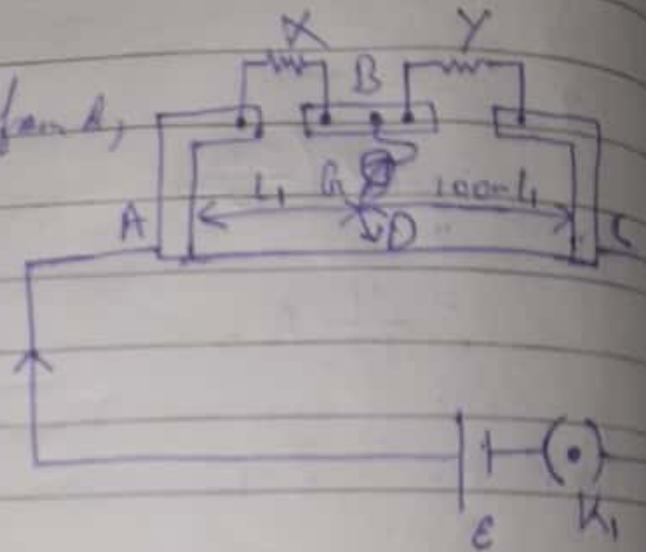

6) If  $X$  and  $Y$  are interchanged,

$$\frac{Y}{L} = \frac{X}{100-L}$$

$$\Rightarrow \frac{12.5}{L} = \frac{8.16}{100-L}$$

$$\Rightarrow 8.16 \times L = (100-L)(12.5)$$

$$\Rightarrow 8.16L = 1250 - 12.5L$$

$$\Rightarrow 20.66L = 1250$$


$$\Rightarrow L = \frac{1250}{20.66}$$

$$= 60.5 \text{ cm.}$$

$\therefore$  The balance point is at 60.5 cm from end A after interchanging  $X$  and  $Y$ .

7) If the ~~galvanometer~~ galvanometer and cell are interchanged, the position of the balance point remains unchanged, the balance p. galvanometer shows no current.

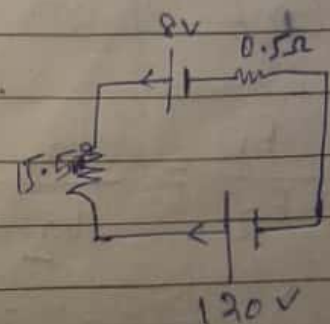8.11) EMF of battery = 8 V.  
Internal resistance ( $r$ ) = 0.5  $\Omega$ .  
Series resistor ( $R$ ) = 15.5  $\Omega$ .  
Supply voltage = 20 V.



$$\text{Net voltage} = 20 - 8 = 12 \text{ V.}$$

$$\text{Net resistance} = 15.5 + 0.5 \quad (\text{As resistor is connected in series})$$
$$= 16 \Omega$$

$$\text{Then, Current (I)} = \frac{V_{\text{net}}}{R_{\text{net}}}$$
$$= \frac{112.7}{16}$$
$$= 7 \text{ A.}$$

As the battery is ~~being~~ charging/being charged,

$$\text{Terminal voltage} = \mathcal{E} + I r$$
$$= 8 + 7 \times 0.5$$
$$= 8 + 3.5$$
$$= 11.5 \text{ V.}$$

A series resistor limits the current flowing in the circuit, otherwise it can be dangerous. So it is needed in a charging circuit.

3.12) EMF of 1<sup>st</sup> cell ( $\mathcal{E}_1$ ) = 1.25 V  
Balance point ( $l_1$ ) = 35 cm.  
 $l_2 = 63$  cm (shifted balance point)

Then,  
EMF of 2<sup>nd</sup> cell ( $\mathcal{E}_2$ ) is given by,

$$\frac{\mathcal{E}_1}{\mathcal{E}_2} = \frac{l_1}{l_2}$$

$$\Rightarrow \frac{1.25}{\mathcal{E}_2} = \frac{35}{63}$$

$$\Rightarrow \frac{E_2}{1.25} = \frac{68}{35}$$

$$\Rightarrow E_2 = \frac{68 \times 1.25}{35}$$

$$= 2.25 \text{ V.}$$

$\therefore$  The EMF of 2nd cell is 2.25 V.

8.18) Number density ( $n$ ) =  $8.5 \times 10^{28} \text{ m}^{-3}$

length of wire = 3 m.

Area of cross-section =  $2 \times 10^{-6} \text{ m}^2$ .

Current in wire = 3 A.

Charge of an electron =  $1.6 \times 10^{-19} \text{ C}$ .

By formula,

$$I = neAVd$$

$$\Rightarrow I = \frac{neAL}{t} \quad \left[ \because vd = \frac{L}{t} \right]$$

$$\Rightarrow 3 = \frac{8.5 \times 10^{28} \times 1.6 \times 10^{-19} \times 2 \times 10^{-6} \times 3}{t}$$

$$\Rightarrow t = 8.5 \times 10^{28} \times 1.6 \times 10^{-19} \times 2 \times 10^{-6}$$

$$= 27.2 \times 10^3 \text{ seconds}$$

$$= 2.72 \times 10^4 \text{ seconds.}$$

$\therefore$  An electron takes  $2.72 \times 10^4$  seconds to drift from one end of wire to another end.