

3.6) $l = 15 \text{ m}$, $A = 6 \times 10^{-2} \text{ m}^2$, $R = 5 \Omega$

$$\rho = \frac{RA}{l} = \frac{5 \times 6 \times 10^{-2}}{15} = 2 \times 10^{-2} \Omega \text{ m}$$

3.7) $R_1 = 2.1 \Omega$, $t_1 = 27.5^\circ \text{C}$
 $R_2 = 2.7 \Omega$, $t_2 = 100^\circ \text{C}$

$$\alpha = \frac{R_2 - R_1}{R_1(t_2 - t_1)} = \frac{0.6}{2.1(72.52)}$$

$$= \frac{0.6}{2(72.52)} = 0.00394^\circ \text{C}^{-1}$$

3.8) $V = 230 \text{ V}$, $I_1 = 3.2 \text{ A}$, $I_2 = 2.8 \text{ A}$

$$\alpha = 1.70 \times 10^{-4} \text{ }^\circ \text{C}^{-1}$$

$$V = I R$$

$$R_1 = \frac{2300}{32} = 71.575 \Omega$$


$$R_2 = \frac{V}{I_2} = \frac{2300}{28} = 82.143 \Omega$$

$$\alpha = \frac{R_2 - R_1}{R_1(t_2 - t_1)} \Rightarrow t_2 - t_1 = \frac{R_2 - R_1}{R_1 \alpha}$$

$$= \frac{10.265 \times 10^4}{71.575 \times 1.7} = 840.35^\circ \text{C}$$

$$\therefore t_2 = 840.35 + 27 = 867.35^\circ \text{C}$$

3.9)

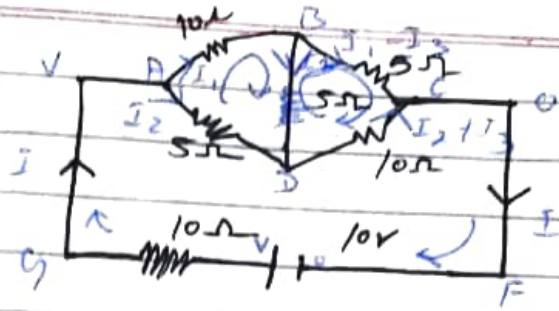

In loop ABDA :-

$$10I_1 + 5I_3 - 5I_2 = 0$$

In loop BCDB :-

$$5(I_1 - I_3) - 10(I_2 + I_3) - 5I_3 = 0$$

In ADCEGA :-

$$5I_2 + 10(I_2 + I_3) + 10(I_1 + I_2) = 10$$

$$5I_2 + 10(I_2 + I_3) + 10I_1 = 10$$

$$5I_2 + 10(I_2 + I_3) + 10(I_1 + I_2) = 10$$

$$10I_1 - 5I_2 + 5I_3 = 0 \quad \text{--- (i)}$$

$$5I_1 - 10I_2 - 20I_3 = 0 \quad \text{--- (ii)}$$

$$10I_1 + 25I_2 + 10I_3 = 10 \quad \text{--- (iii)}$$

$$I_{AB} = I_1 = \frac{4}{17} \text{ A}$$

$$I_{BC} = I_1 - I_3 = \frac{6}{17} \text{ A}$$


$$I_{DC} = \frac{4}{17} \text{ A}$$

$$I_{AD} = \frac{5}{17} \text{ A}$$

$$I_{BD} = \frac{-2}{12} \text{ A}$$

∴ total amount = $\frac{10}{17} \text{ A}$

3.10)

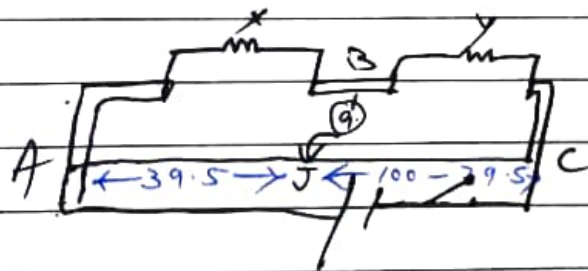

i) $l = 39.5 \text{ cm}$, $R_y = 12.5 \Omega$

$$\frac{R_x}{39.5} = \frac{12.5}{(100 - 39.5)}$$

$$R_x = \frac{12.5 \times 39.5}{60.5} = 8.15 \Omega$$

ii) $R = Y = 2.5 \Omega$ $S = X = 18.16$

$$\frac{12.5}{d} = \frac{8.16}{100-d} \Rightarrow 1250 - 12.5d = 8.16d$$

$$\Rightarrow 12.5d + 8.16d = 1250$$

$$\Rightarrow d = \frac{1250}{20.66} = 60.5 \Omega$$

∴) Then the conditions of the balanced bridge still remains satisfied and again the galvanometer will not show any current.

11.) $\text{Emf}(E) = 8V$, $r = 0.5 \Omega$, $V = E + Ir$, $R = 15.5 \Omega$
 $E'_{\text{net}} = 120 - 8 \cdot 0 = 112V$

$$I = \frac{E'}{R+r} = \frac{112}{15.5+0.5} = \frac{112}{16} = 7A$$

$$V = E + Ir = 8 + 7 \times \frac{5}{10} = 8 + 3.5 = 11.5V$$

12.) $\text{Emf}_1 = 1.25V$ $l = 35$ $l_2 = 63cm$
 $\text{Emf}_2 =$

$$\text{As } \frac{E_2}{E_1} = \frac{l_2}{l_1}$$

$$E_2 = \frac{l_2}{l_1} \times E_1 = \frac{63}{35} \times \frac{1.25}{1} = 2.25V$$

13.) $n = 8.5 \times 10^{25} m^{-3}$, $l = 3m$, $a = 2 \times 10^{-6} m^2$
 $I = 3A$

$$I = n_e e n A V_d \quad V_d = \frac{I}{enA} = \frac{3 \times 10^{-25} \times 10^{19}}{1.6 \times 8.5 \times 2 \times 10^{-6}} = 1.1 \times 10^{-7} m/s$$

$$t = \frac{l}{V_d} = \frac{3 \times 10^4}{1.1} = 2.73 \times 10^4 = 2.73 \times 10^4 s = 7.57 hr$$


14.) $\sigma = 10^{-9} \text{ cm}^{-2}$, $V = 400 \text{ kV}$, $I = 1800 \text{ A}$
 $R = 6.37 \times 10^6 \text{ m}$

Charge (q) = Surface area $\times \sigma = 4\pi R^2 \sigma$
 $= 4 \times 3.14 \times (6.37 \times 10^6)^2 \times 10^{-9}$
 $= 509.65 \times 10^3 \text{ C}$

$t = \frac{q}{I} = \frac{509 \times 10^3}{1800} = 283 \text{ sec}$

15) a) $\text{emf} = 2 \text{ V}$, $n = 6$, $r = 0.015 \Omega$, $R = 8.5 \Omega$
 $I = \frac{nE}{R + rn} = \frac{6 \times 2}{8.5 + 6 \times 0.015} = \frac{12}{8.59} = 1.4 \text{ A}$
 $V = 1.4 \times 8.5 = 11.9$

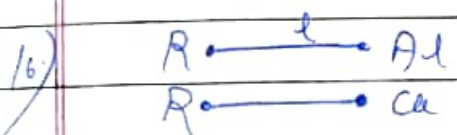b) $\text{emf} = 1.9 \text{ V}$, $r = 380 \Omega$
 $I = \frac{1.9}{380} = \frac{19}{3800} = 0.005 \text{ A}$




$S_{Al} = 2.63 \times 10^{-6} \text{ m}^2$
 $R_{DAl} = 2.7$

$S_{Cu} = 1.72 \times 10^{-8} \text{ m}^2$
 $R_{DCu} = 8.9$

mass = vol \times density
 $= Al \times d$

$\frac{m_{Cu}}{m_{Al}} = \frac{\rho_{Cu} d_{Cu}}{\rho_{Al} d_{Al}} = \frac{1.72 \times 10^{-8} \times 8.9}{2.63 \times 10^{-6} \times 2.7} = 2.2$

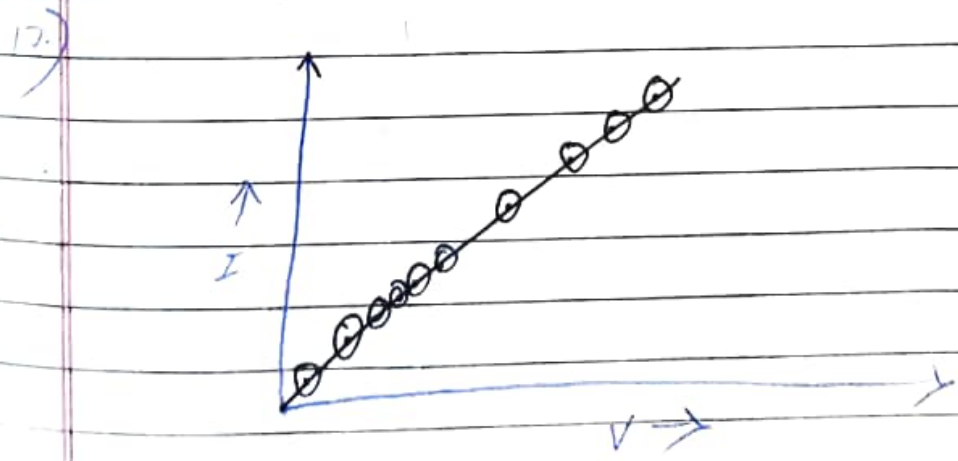$R = \frac{\rho l}{A}$ $\frac{\rho l}{A} \cdot d = \frac{\rho l d}{A}$



18.) a) only current is constant, other quantity vary inversely with the area of cross section.

b) No, non-ohmic conductor like, semiconductor diode, vacuum diode.

c) $I_{max} = \frac{E}{r}$, $I \propto \frac{1}{r}$ So, I_{max} is large if r is small.

d) If the internal resistance is not very high, then the current will exceed the safety limit in case the circuit is short-circuited accidentally.

19.) a) greater

c) nearly independent of

b) lower

d) 10^{22}


20.) a) For max effective - resistance all the n resistors must be connected in series $R_s = nR$

For minimum effective resistance all n resistors must be connected in parallel


$$\frac{1}{R_p} = \frac{1}{R} + \frac{1}{R} + \dots + \frac{1}{R} = \frac{n}{R}$$

$$R_p = \frac{R}{n}$$

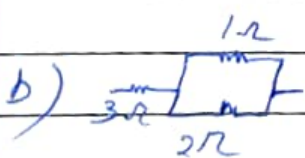
$$\text{Ratio} = \frac{nR}{R} \times \frac{1}{n} = n^2 : 1$$




$$R = \frac{11}{3} \Omega$$

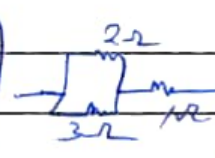


$$R = \frac{11}{5} \Omega$$

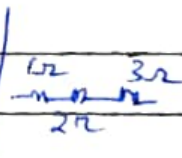



$$R = 6 \Omega$$

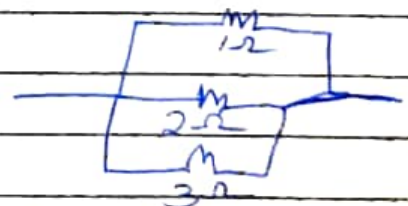

$$R = \frac{6}{11} \Omega$$

c)  $R = \frac{4}{3} \Omega \rightarrow R = 4 \times \frac{4}{3} = \frac{16}{3} \Omega$

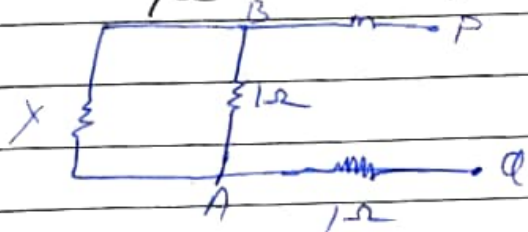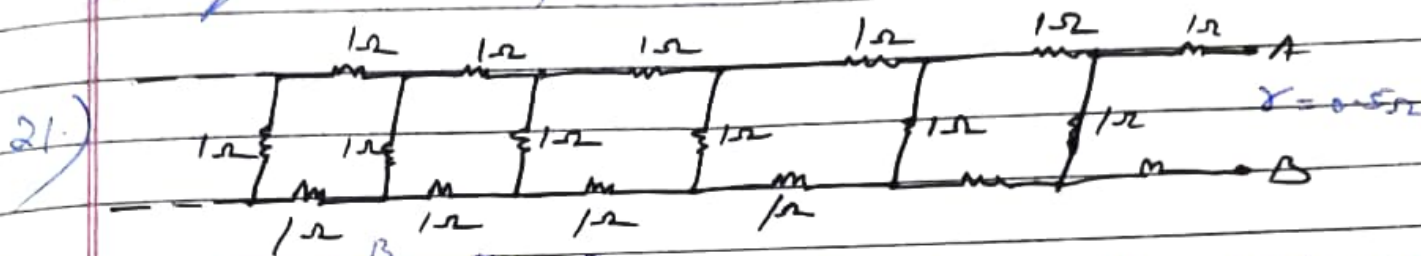d) equivalent Resistance R : $E_{eq} = 5R$



Resistance between P and Q

$$X = 1 + \frac{1 \times X}{1 + X} + 1 = \frac{2 + X}{X + 1}$$

$$X^2 + X = 2X + 2 + X$$

$$X^2 - 2X - 2 = 0$$

$$X = 1 + \sqrt{2}$$

$$X = 2.732 \Omega$$

$$I = \frac{E}{R + r}$$

$$= \frac{12}{2.732 + 0.5} = 3.713 A$$

22.) a) $E_1 = 1.02 V$, $V = 2V$, $r = 0.4 \Omega$, $l_1 = 67.3 cm$

$$E_2 = E \frac{E}{1.02} = \frac{82.3}{67.3}$$

$$E = \frac{823}{673} \times \frac{102}{100} = 1.25 V$$

b) Protects the galvanometer for position far away from the balance point by decreasing current through it.

c) No balance point is not affected, as no current flows through the standard cell at the balance point.

d) Yes, it changes the potential gradient and affects the balance point.

e) No, if E_2 emf there will be no balanced point on the wire AB.

f) Unsuitable, because the balance point will be very close to the end A and the % error measured is very large. Modified by putting R in series so that V_{end} is slightly greater than the emf measured.

23) $R = 10 \Omega$, $l_1 = 58.3 \text{ cm}$, x $l_2 = 68.5 \text{ cm}$

$$\frac{E_2}{E_1} = \frac{l_2}{l_1} \cdot \frac{x}{R} = \frac{l_2}{l_1} \quad x = \frac{l_2}{l_1} \times R = \frac{68.5}{58.3} \times 10 = 11.75 \Omega$$

We should reduce current in the outside circuit suitability by putting a series resistor.

24) $\delta = ?$, $V = 1.5 \text{ V}$, $l_1 = 76.3 \text{ cm}$, $l_2 = 64.8$
 $R = 9.5 \Omega$

$$\delta = R \left(\frac{l_1 - l_2}{l_2} \right) = \left(\frac{76.3 - 64.8}{64.8} \right) \times \frac{9.5}{10} = \frac{9.5 \times 11.5}{64.8} = 1.7 \Omega$$