

## Current Electricity    Chp-3

1. Given, emf = 12V ; internal resistance  $r = 0.4\Omega$   
 $\therefore$  Current drawn from the battery  $I = \frac{E}{R+r}$   
 In case of maximum current  $R=0$ .

$$I_{\text{max}} = \frac{E}{r}$$

$$= \frac{12}{0.4} = 30\text{A}.$$

2. Given, emf of battery  $E = 10\text{V}$   
 Internal resistance  $r = 3\Omega$   
 Current in circuit  $I = 0.5\text{A}$

The current in the circuit


$$= \frac{\text{emf}}{\text{Total resistance of the circuit}}$$

Total resistance of the circuit

$$I = \frac{E}{R+r}$$

$$0.5 = \frac{10}{R+3} \quad \text{or} \quad R+3 = 20$$

$$R = 17\Omega.$$

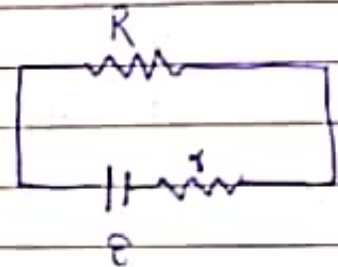

When the circuit is closed, the terminal voltage

$$V = E - Ir \Rightarrow 10 - 0.5 \times 3 = 10 - 1.5 = 8.5\text{V}.$$

Thus, the resistance in the circuit is  $17\Omega$  and terminal voltage of the battery when the circuit is closed is  $8.5\text{V}$ .


3. a)  $R_1 = 1\Omega$ ,  $R_2 = 2\Omega$  and  $R_3 = 3\Omega$   
 Resultant resistance in series

$$R_s = R_1 + R_2 + R_3$$

$$= 1 + 2 + 3 = 6\Omega.$$

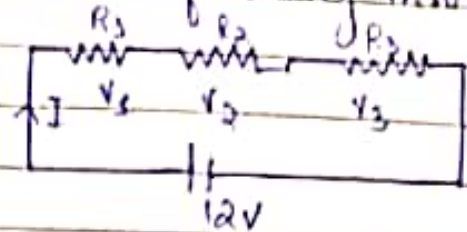b. The potential drop across each resistor is different when two or more resistors are connected in series combination. Let  $V_1, V_2, V_3$  be the potential drops across resistance  $R_1, R_2$  and  $R_3$  resp. and the current flowing through the circuit is  $I$ .

$$I = \frac{V}{R_s} = \frac{12}{6} = 2A.$$




Current is same through each resistor as they are in series.  
 Potential drop across resistance  $R_1, V_1 = IR_1 = 2 \times 1 = 2V$   
 Potential drop across resistance  $R_2, V_2 = IR_2 = 2 \times 2 = 4V$   
 Potential drop across resistance  $R_3, V_3 = IR_3 = 2 \times 3 = 6V$ .  
 Thus the potential drop across resistances  $1\Omega$  is  $2V$ .  
 Resistance  $2\Omega$  is  $4V$  and resistance  $3\Omega$  is  $6V$ .

4. a) Given,  $R_1 = 2\Omega, R_2 = 4\Omega, R_3 = 5\Omega$   
 Resultant resistance in parallel

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{2} + \frac{1}{4} + \frac{1}{5} = \frac{10 + 5 + 4}{20} = \frac{19}{20}$$

$$R_p = \frac{20}{19} \Omega.$$

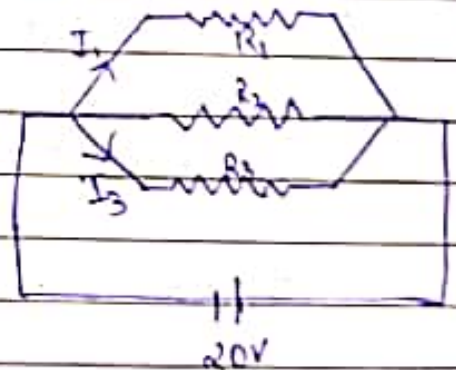

b.  $V = 20V$ .

Current through resistance  $R_1$

$$I_1 = \frac{V}{R_1} = \frac{20}{2} = 10A.$$

Current through resistance  $R_2$

$$I_2 = \frac{V}{R_2} = \frac{20}{4} = 5A.$$

Current through  $R_3 = I_3 = \frac{V}{R_3} = \frac{20}{5} = 4A.$

Total current drawn =  $10 + 5 + 4 = 19A.$



Thus, current drawn from the battery is 19 A.

5. Given, the resistance of heating element at temp.  $27^\circ\text{C}$ .

$$= R_{27} = 100 \Omega.$$

Resistance of heating element at temp.  $t^\circ\text{C} = R_t = 117 \Omega$ .

Temp. coefficient of resistance  $\alpha = 1.70 \times 10^{-4} / ^\circ\text{C}$ .

Temp. coefficient of resistance

$$\alpha = \frac{R_t - R_{27}}{R_{27} (t - 27)}$$

$$1.70 \times 10^{-4} = \frac{117 - 100}{100 (t - 27)}$$

$$t - 27 = \frac{17}{100 \times 1.70 \times 10^{-4}}$$

$$t - 27 = 100$$

$$t = 100 + 27 = 127^\circ\text{C}.$$

Thus, the temp. of element is  $127^\circ\text{C}$  when resistance is  $117 \Omega$ .

6. Given, Area of cross-section of wire  $(A) = 6.0 \times 10^{-7} \text{ m}^2$   
Length of the wire  $l = 15 \text{ m}$ .

Resistance of wire  $R = 5 \Omega$ .

Resistance of the wire  $R = \frac{\rho l}{A}$

$$\rho = \frac{RA}{l} = \frac{5 \times 6.0 \times 10^{-7}}{15} = 2 \times 10^{-7} \Omega \text{ m}.$$

7. Given, resistance of silver wire at  $27.5^\circ\text{C} = R_{27.5} = 2.1 \Omega$

Resistance of silver wire at  $100^\circ\text{C} = R_{100} = 2.7 \Omega$ .

Let the temp. coefficient of silver be  $\alpha$ .

$$\alpha = \frac{R_{t_2} - R_{t_1}}{R_{t_1} (t_2 - t_1)}$$

$$\alpha = \frac{R_{100} - R_{27.5}}{R_{27.5} (100 - 27.5)} = \frac{2.7 - 2.1}{2.1 \times 72.5} = 0.0039 / ^\circ\text{C}$$

8. Given, Potential difference = 230V  
 Initially current at 27°C =  $I_{27^\circ\text{C}} = 2.8\text{A}$   
 Final current at 0°C =  $I_{0^\circ\text{C}} = 2.8\text{A}$   
 Room temp. = 27°C.  
 Temp. coefficient of resistance

$$\text{Resistance at } 27^\circ\text{C} = R_{27^\circ\text{C}} = \frac{V}{I_{27^\circ\text{C}}} = \frac{230}{2.8} = \frac{2300}{28} \Omega$$

$$\text{Resistance at } 0^\circ\text{C} = R_{0^\circ\text{C}} = \frac{V}{I_{0^\circ\text{C}}} = \frac{230}{2.8} = \frac{2300}{28} \Omega$$

Temp. of coefficient of resistance

$$\alpha = \frac{R_t - R_{27}}{R_{27} (t - 27)}$$

$$1.7 \times 10^{-4} = \frac{\frac{2300}{28} - \frac{2300}{28}}{\frac{2300}{28} (t - 27)}$$

$$\Rightarrow t - 27 = \frac{82.143 - 71.875}{71.875 \times 1.7 \times 10^{-4}} = 810.347$$

$$t = 810.347 + 27 = 837.3^\circ\text{C}$$


9. From Kirchoff's 1st law i.e. loop law  
 $\sum V = \sum IR$

In loop ABDA, Distributing the current

$$10I_1 + 5I_2 - 5(2 - I_1) = 0$$

$$2I_1 + I_2 - I_1 + I_2 = 0$$

$$3I_1 + I_2 = I$$

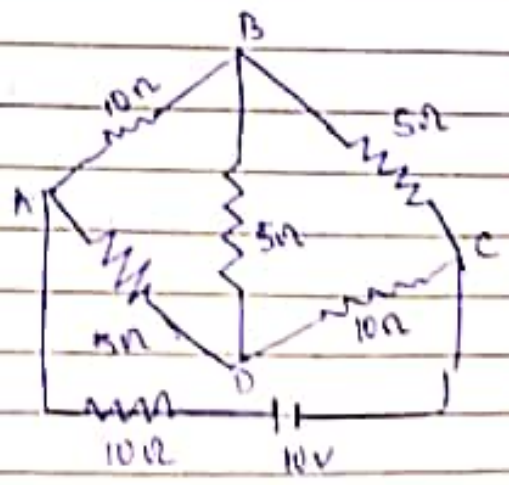

In loop BCDB

$$5(I_1 - I_2) - 10(I_1 - I_2 + I_1) - 5I_2 = 0$$



$$I_1 - I_2 - 2I + 2I_1 - 2I_2 - I_2 = 0$$

$$3I_1 - 4I_2 = 2I \quad \text{--- (ii)}$$

By solving the (eq. i) and (eq. ii) we get

$$I_1 = \frac{2I}{5} \quad \text{and} \quad I_2 = -\frac{I}{5} \quad \text{--- (iii)}$$

In loop ABCFA.

$$10 = 10I + 10I_1 + 5(I_1 - I_2)$$

$$2 = 2I + 3I_1 - I_2 \quad \text{--- (iv)}$$

Putting the value of  $I_1$  and  $I_2$  from (eq. iii) and (eq. iv) we get.

$$2 = 2I + 3\left(\frac{2I}{5}\right) - \left(-\frac{I}{5}\right)$$

$$2 = \frac{17I}{5}$$

$$I = \frac{10A}{17}$$

Current in branch AB  $I_1 = \frac{2}{5} \times \frac{10}{17} = \frac{4}{17} A$ .

$$\text{and } I_2 = \frac{-I}{5} = \frac{-2}{17} A.$$

Current in branch AD is  $I_3 = \frac{4}{17} A$

Current in branch BC is  $I_1 - I_2 = \frac{4}{17} - \left(\frac{-2}{17}\right) = \frac{6}{17} A$ .

Current in branch AD is  $I - I_3 = \frac{10}{17} - \frac{4}{17} = \frac{6}{17} A$ .

Current in branch DC is  $(I - I_3) + I_2 = \frac{6}{17} + \left(\frac{-2}{17}\right) = \frac{4}{17} A$

10.  
a. Balance point from end A  
 $l = 31.5 \text{ cm.}$

Resistance of resistor  $Y = 12.5 \Omega$ .

Resistance of resistor  $X = ?$

Acc. to the condition of balanced Wheatstone bridge.

$$\frac{X}{Y} = \frac{L}{100-L}$$

$$X = \frac{L}{100-L} \cdot Y$$

$$X = \frac{39.5 \times 12.5}{100 - 39.5} = 8.16 \Omega$$

The resistance of resistor  $X$  is  $8.16 \Omega$ .

(b) If  $X$  and  $Y$  are interchanged, then the balanced length will also be interchanged. Thus, the balance length becomes  $100 - 39.5 = 60.5 \text{ cm}$ .

(c) If the galvanometer and cell are interchanged at the balancing point of the bridge, the balance point is not obtained. The galvanometer shows no deflection.

11. EMF of the battery  $\epsilon = 8 \text{ V}$ , EMF of the supply  $V = 120 \text{ V}$ .  
Since, the battery is being charged, the effective EMF in the circuit

$$E = V - \epsilon = 120 - 8 = 112 \text{ V}$$

Current in circuit

$$I = \frac{\text{Effective EMF}}{\text{Total resistance}} = \frac{E}{r + R}$$

$$= \frac{112}{0.5 + 15.5} = \frac{112}{16} = 7 \text{ A}$$

12. Given,  $E_1 = 1.25 \text{ V}$ ,  $l_1 = 35 \text{ cm}$ ,  $l_2 = 63 \text{ cm}$ .  
As we know that in case of potentiometric the potential gradient remains constant.



ie  $E \propto I$

$$\frac{E_1}{E_2} = \frac{I_1}{I_2}$$

$$\frac{1.25}{E} = \frac{35}{63}$$

$$E = \frac{1.25 \times 63}{35} = 2.25 \text{ V}$$

13. Given, number density of  $e^-$   $n = 8.5 \times 10^{28} / \text{m}^3$   
length of wire = 3m.

Current  $i = 3\text{A}$ . Charge of  $e^- = 1.6 \times 10^{-19} \text{ C}$ .

Time taken by  $e^-$  to drift from one end to another of the wire

$$t = \frac{\text{length of the wire}}{\text{Drift velocity}} = \frac{l}{V_d} \quad \dots (i)$$

Using the relation,  $I = neAv_d$

$$\text{or } V_d = \frac{I}{neA} \quad \dots (ii)$$

Putting the value in Eq (i) from Eq (ii)

$$t = \frac{I l}{neA} = \frac{3 \times 8.5 \times 10^{28} \times 1.6 \times 10^{-19} \times 2 \times 10^{-6}}{3}$$

$$t = 2.72 \times 10^4 \text{ s} = 7 \text{ h } 33 \text{ min}$$

14. Given, radius of earth  $R = 6.37 \times 10^6 \text{ m}$ .

Negative surface charge density  $\sigma = 10^{-9} \text{ C/m}^2$

Potential difference  $V = 400 \text{ kV} = 400 \times 10^3 \text{ V}$

Current on the globe  $I = 1800 \text{ A}$

$$\text{Surface area of earth } A = 4\pi R^2 = 4 \times 3.14 \times (6.37 \times 10^6)^2$$

$$= 509.64 \times 10^{12} \text{ m}^2$$

Charge on earth surface  $Q = \text{Area of earth surface} \times \text{Surface charge density}$

$$Q = n e = 509.61 \times 10^{12} \times 10^{-19}$$

$$= 509.61 \times 10^3 \text{ C.}$$

We know that  $Q = It$ .

$\therefore$  Time required to neutralise earth's surface

$$t = \frac{Q}{I} = \frac{509.61 \times 10^3}{1800}$$

$$t = 283.1 \text{ s or } t = 4 \text{ min } 43 \text{ s.}$$

15. Six cells are joined in series

EMF of each cell  $E = 2 \text{ V}$

Total EMF of circuit  $= n \times E = 6 \times 2 = 12 \text{ V.}$

No. of cells,  $n = 6.$

Internal resistance of each cell  $r = 0.015 \Omega.$

Total internal resistance  $= n \times r = 6 \times 0.015 = 0.09 \Omega.$

External load  $R = 8.5 \Omega.$

Current in the circuit

$$I = \frac{nE}{n r + R} = \frac{12}{0.09 + 8.5} = 1.4 \text{ A.}$$

The terminal voltage of battery  $V = IR = 1.4 \times 8.5 = 11.9 \text{ V.}$

b. EMF of cell  $E = 1.9 \text{ V.}$

Internal resistance of cell  $r = 380 \Omega$

Maximum current can be drawn from the cell, if there is zero external resistance, therefore

$$I_{\text{max}} = \frac{E}{r} = \frac{1.9}{380} = 0.005 \text{ A.}$$

16. a. Current does not depend on area of conductor, as current remains constant. Current density is inversely proportional to area of cross-section ( $J \propto \frac{1}{A}$ ), electric field and drift speed also depend on area ( $E \propto \frac{1}{A}$  and  $V_d \propto \frac{1}{A}$ ). As current density, electric field and



drift speed do not remain constant as area changes

b. No, Ohm's law is not universally applicable for all conducting elements. Vacuum tubes, semiconductors, diodes, transistors, thermistors and electrolytes are the example of elements which do not obey Ohm's law.

c. For very high current, the internal resistance should be low by acc. to the formula  $I_{max} = \frac{V}{r}$ . As lesser be the value of  $r$  (internal resistance) more is the current.

d. A high tension supply must have a very large internal resistance because if the circuit is shorted the internal resistance is not large enough than current drawn will exceed the safe limit and will cause the damage.

19.

a. The resistivity of alloys of metals usually have greater resistivity than that of their constituent metals.

b. Alloys usually have much lower temp. coefficient of resistance than pure metals.

c. The resistivity of alloy manganin is nearly independent of increases of temp. because the coefficient of resistance is very low and its resistivity is quite large.

d. The resistivity of a typical insulator (like one of amber) is greater than that of a metal by a factor of the order of  $10^{22}$ . Because insulator has maximum resistivity in comparison of metals and alloys.

20. a. To get the maximum effective resistance, we connect  $n$  resistors in series combination.

$$R_{\text{max}} = R + R + \dots + n \text{ times} = nR \quad \dots (i)$$

To get the minimum effective resistance, we connect the  $n$  resistors in parallel combination.

$$\frac{1}{R_{\text{min}}} = \frac{1}{R} + \frac{1}{R} + \dots + n \text{ times} = \frac{n}{R}$$

$$R_{\text{min}} = \frac{R}{n} \quad \dots (ii)$$

Ratio of maximum to minimum resistance

$$= \frac{R_{\text{max}}}{R_{\text{min}}} = \frac{nR \cdot n}{R} \quad (\text{From eq. (i) and (ii)})$$

$$= n^2$$

b. Given,  $R_1 = 1 \Omega$ ,  $R_2 = 2 \Omega$  and  $R_3 = 3 \Omega$ .

(i) To get the equivalent resistance as  $1 \frac{1}{3} \Omega$ .

Here  $R_1$  and  $R_2$  in parallel is

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = 1 + \frac{1}{2} = \frac{3}{2}$$

$$R_p = \frac{2}{3} \Omega$$

Now,  $R_p$  and  $R_3$  are in series, the equivalent resistance

$$R = R_p + R_3 = \frac{2}{3} + 3 = \frac{11}{3} \Omega$$

(ii) To get the equivalent resistance as  $\frac{11}{5} \Omega$ .



The  $R_2$  and  $R_3$  are in parallel,

$$\frac{1}{R_p} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{2} + \frac{1}{3} = \frac{3+2}{6} = \frac{5}{6}$$

$$R_p = \frac{6}{5} \Omega$$

Now,  $R_p$  and  $R_1$  in series, So resultant resistance

$$R = R_p + R_1 = \frac{6}{5} + 1 = \frac{11}{5} \Omega$$

(iii) To get the equivalent resistance as  $6 \Omega$ .

Resultant resistance

$$R_s = R_1 + R_2 + R_3 = 1 + 2 + 3 = 6 \Omega$$

(iv) To get the equivalent resistance as  $\frac{6}{11} \Omega$ .

$$\frac{1}{R_p} = \frac{1}{1} + \frac{1}{2} + \frac{1}{3} = \frac{6+3+2}{6} = \frac{11}{6}$$

$$\text{Resultant resistance } R_p = \frac{6}{11} \Omega$$

(c) Hence  $1 \Omega$  and  $1 \Omega$  are in series

$$\therefore R_s = 1 + 1 = 2 \Omega$$

and  $2 \Omega$  and  $2 \Omega$  are in series

$$R'_s = 2 + 2 = 4 \Omega$$

Now,  $R_s$  and  $R'_s$  in parallel

$$\frac{1}{R'} = \frac{1}{R_s} + \frac{1}{R'_s} = \frac{1}{2} + \frac{1}{4} = \frac{2+1}{4} = \frac{3}{4}$$

$$\therefore \text{Resultant resistance } R' = \frac{4}{3} \Omega$$

21. Let the effective resistance of the network is  $x \Omega$ . If one part of the network has resistance  $(1 \Omega, 1 \Omega)$  is separated as shown, the effective resistance remains  $x$  (as it is infinitely network) Here  $x$  and  $1 \Omega$  are in parallel.

$$\frac{1}{R_p} = \frac{1}{x} + \frac{1}{1} = \frac{1+x}{x}$$

$$R_p = \frac{x}{1+x}$$

New resistance  $R_p$  of  $x \Omega$  and  $1 \Omega$  are in series, so the resultant resistance

$$R = R_p + 1 + 1 = \frac{x}{1+x} + 1 + 1 = \frac{x}{1+x} + 2 \quad \dots (i)$$

In case of infinite resistance, the value of  $R$  remains  $x$

$$\therefore x = \frac{x}{1+x} + 2$$

$$x(x+1) = x + 2 + 2x$$

$$x^2 - 2x - 2 = 0$$

$$x = \frac{-(-2) \pm \sqrt{4+8}}{2} = \frac{2 \pm \sqrt{12}}{2} = 1 \pm \sqrt{3}$$

The value of resistance can't be -ve, so the resistance of network

$$x = 1 + \sqrt{3} = 1 + 1.732$$

$$x = 2.732 \Omega$$

Total resistance of the circuit =  $2.732 + 0.5 = 3.232 \Omega$

Current drawn from the supply

$$I = \frac{V}{R} = \frac{12}{3.232} = 3.72 \text{ A}$$

22.0. Here  $E_1 = 1.02 \text{ V}$ ,  $l_1 = 67.3 \text{ cm}$ ,  $E_2 = E = ?$  and  $l_2 = 82.3 \text{ cm}$

$$E \propto l$$

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

$$\frac{1.02}{E} = \frac{67.3}{82.3}$$

$$E = \frac{1.02 \times 82.3}{67.3} = 12.47 \text{ V}$$



- b. The use of very high resistance of 600 kΩ is to allow a very small current through the galvanometer when it is too far from the balance point.
- c. No, the balance point is not affected by high resistance of 600 kΩ.
- d. No, the balance point is not affected by the internal resistance of the driver cell.
- e. If the emf of the driver cell is less than the cell, the method cannot work.
- f. No, the circuit does not work for determining an extremely small emf of millivolt because in this situation, the balance point is very near to end. To modify, we use high resistance in series with the cell. This decreases the current in the pot. gradient decreases.

23. Here  $l_1 = 58.3 \text{ cm}$ ,  $l_2 = 68.5 \text{ cm}$ ,  $R = 10 \Omega$ .  
 Let  $I$  be the current in the potentiometer wire.  
 $E_1$  and  $E_2$  be the potential drops across  $R$  and  $X$ .  
 Then,

$$\frac{E_2}{E_1} = \frac{IR}{IR} = \frac{R}{R} \quad \dots (i)$$

$$\text{or } \lambda = \frac{E_2}{E_1} \cdot R \quad \dots (ii)$$

Acc. to the principle of potentiometer

$$\frac{E_2}{E_1} = \frac{l_2}{l_1}$$

From Eq. (i) we get

$$r_1 = \frac{l_2}{l_1} \cdot R = \frac{68.5}{58.3} \times 10 = 11.75 \Omega.$$

24. New balancing length when cell is in open circuit

$$l_1 = 76.3 \text{ cm}$$

Balancing length when cell is in closed-circuit

$$l_2 = ~~65.5~~ 64.8 \text{ cm}.$$

$$\text{and } R = 9.5 \Omega.$$

The internal resistance of the cell is given by

$$r = \left( \frac{l_1}{l_2} - 1 \right) R$$

$$= \left( \frac{76.3}{64.8} - 1 \right) \times 9.5 = 1.68 \Omega.$$