

1. When the sliding contact is in middle, a resistance of  $R_0/2$  is connected in series with a parallel combination of  $R$  and  $R_0/2$ .

Hence, net resistance is given by :

$$R_{eq} = \frac{R_0}{2} + \frac{R_0 \parallel R}{2}$$

Current flowing through the circuit is given by :

$$I = \frac{V}{R_{eq}}$$

Potential across  $R$  is given by :

$$V_R = I \left( \frac{R_0 \parallel R}{2} \right)$$

$$V_R = \frac{V}{R_{eq}} \left( \frac{R_0 \parallel R}{2} \right)$$

$$\text{Solving, } V_R = \frac{R}{4R + R_0} V$$


2. (a) By increasing  $R$  the current through  $AB$  decreases, so potential gradient decreases. Hence a greater length of wire would be needed for balancing the same potential difference. So the null point would shift towards  $B$ .

(b) By decreasing resistance  $S$ , the current through  $AB$  remains the same, potential gradient does not change. As  $K_2$  is open so there is no effect of  $S$  on null point.

3. (a) Principle of potentiometer : The potential drop across the length of a steady current carrying wire of uniform cross section is proportional to the length of the wire.

- Page \_\_\_\_\_
- (i) We use a long wire to have a lower value of potential gradient i.e. a lower 'least count' or greater sensitivity of the potentiometer.
- (ii) The area of cross-section has to be uniform to get a 'uniform wire' as per the principle of the potentiometer.
- (iii) The emf of the driving cell has to be greater than the emf of the primary cells as otherwise no balance point would be obtained.

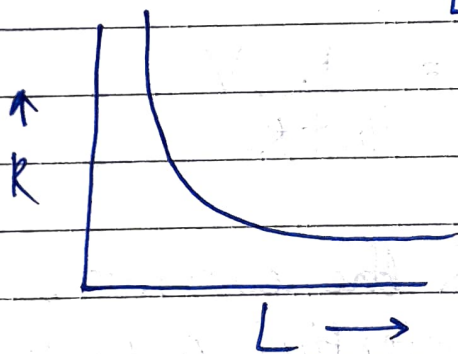(b) Potential gradient  $k = \frac{V}{L}$



4. (a) The purpose of high resistance  $R_2$  is to protect the galvanometer by decreasing the current through it for positions, which are far away from the balance point.
- (b) When resistance  $R_1$  is increased, the current through the potentiometer wire circuit decreases. Due to it, the potential gradient across potentiometer wire decreases. As a result of it, the balance point shifts towards the end.

Page \_\_\_\_\_

(c) (1) When emf  $\epsilon$  is greater than  $2V$  the balance point cannot be obtained on potentiometer wire because the potential drop across the potentiometer wire will be less than  $2V$ .

(2) When the key is closed, the cell emf  $\epsilon$  gets short circuited. Due to it, the balance point is not obtained on the potentiometer wire.

5. (a) decreases. It is because as  $R_1$  decreases, the current in potentiometer circuit increases. Due to it, the potential gradient of potentiometer wire increases. As a result of it the same emf will be balanced on smaller length of potentiometer wire.

(b) Increases. As  $R_2$  increases the current  $I (= \frac{\epsilon}{r + R_2})$  decreases. This increases the terminal pot. diff.  $V(\epsilon - Ir)$  across the unknown cell. As a result of it, the terminal pot. diff. of cell  $\epsilon$  will be balanced on larger length of potentiometer wire.