


Name:- Pratik Kumar Moduli ; section:- DB

School no.:- 9703


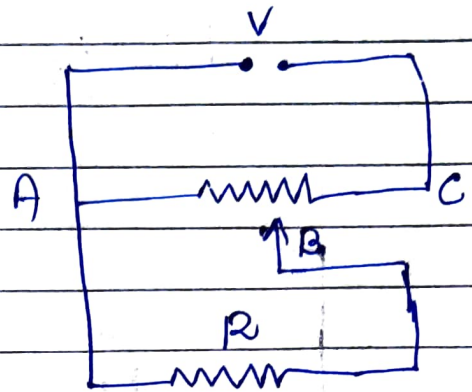
## Home Assignment

$$\begin{aligned} 1) \quad R_{\text{total}} &= \frac{R_0}{2} + \frac{R_0 \times R}{2} \\ &= \frac{R_0}{2} + R \\ &= \frac{R_0 (R_0 + 4R)}{2(R_0 + 2R)} \end{aligned}$$



$$I_{\text{total}} = \frac{V}{R_{\text{total}}}$$

Current through R

$$= I_2 = I_{\text{total}} \times \frac{R_0 \times R}{\frac{R_0}{2} + R}$$


$$\mathcal{Q} = I_{\text{total}} \times \frac{R_0}{R_0 + 2R}$$

$$= \frac{V \cdot 2(R_0 + 2R)}{R_0 (R_0 + 4R)} \times \frac{R_0 \times R}{R_0 + 2R}$$

$$= \frac{2VR_0R}{R_0 (R_0 + 4R)}$$

$$\text{Voltage across R} = I_2 R = \left( \frac{2VR}{R_0 + 4R} \right)$$

2)

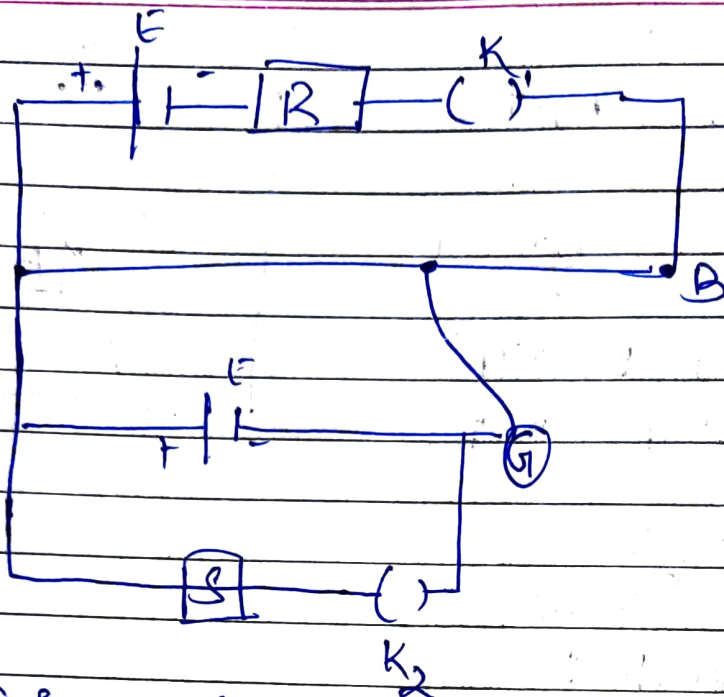

(i) By increasing resistance  $R$  the current through  $AB$  decrease, so potential gradient decrease. Hence a greater length of wire would be needed for balancing the same potential difference so the Null point would shift towards  $B$ .

(ii) By decreasing resistance  $S$ , the current through  $AB$  remain the same potential gradient does not change. As  $K_2$  is open so there is no effect of  $S$  on null point.

3) Principle of potentiometer:-

The potential drop across the length of a steady current carrying wire uniform cross section is proportional to the length of the wire.

(i) we use a long wire to have a lower value ~~of potential gradient~~ to potential gradient i.e a lower least count or greater sensitivity of the potentiometer.





(ii) The area of cross-section has to be uniform to get a 'uniform wire' as per the principle of potentiometer.

(iii) The emf of the driving cell has to be greater than ~~the~~ the emf of the primary cell as otherwise no balance point would be obtained.

(b) Potential gradient  $k = \frac{V}{L}$

∴ The required graph is shown below:-

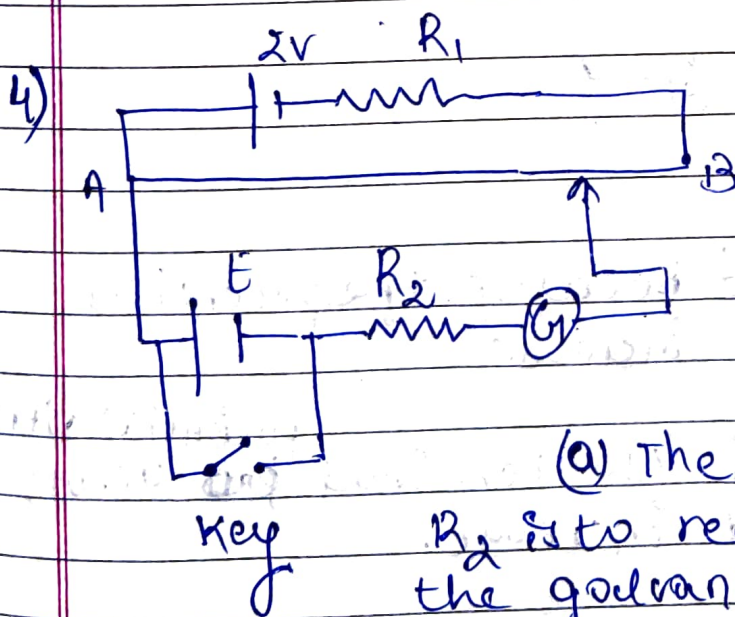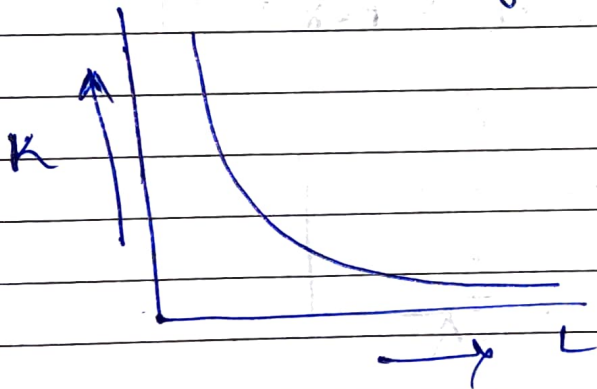


(a) The purpose of high resistance  $R_2$  is to reduce the current through the galvanometer when jockey is far from balance point, this save the galvanometer and the cell from being damaged.

(b) When resistance  $R_1$  is decreased the potential gradient of potentiometer wire increase, so balance point (S) shifts to longer length of wire.

(c) (i) The balance point is not ~~also~~ obtained because maximum emf across potentiometer wire is  $2V$ .

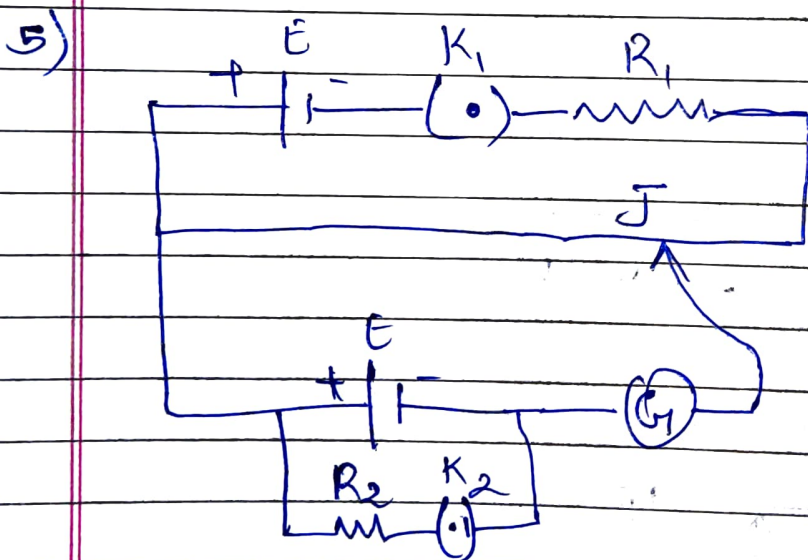(ii) When key (K) is closed, the terminal potential difference of cell is zero, so balance point cannot be between A and B (since  $V = kL \Rightarrow L = 0$  for  $V = 0$ )



(i)  $R_1$  is increased because the potential gradient would increase.

(ii)  $R_2$  is increased the terminal potential difference across the cell would increase.