

Electric Current \rightarrow NCERT

3.1) ~~$V = IR$~~ We know, $I = \frac{\mathcal{E}}{R+r}$ [$R \rightarrow$ external resistance]
 $r \rightarrow$ internal "

$$\therefore I_{\max} = \frac{\mathcal{E}}{R+r} \quad (\text{when } R = 0)$$

$$= \frac{\mathcal{E}}{r} = \frac{12}{0.4} \text{ A} = 30 \text{ A}$$

3.2) $I = \frac{\mathcal{E}}{R+r}$


$$\Rightarrow 0.5 = \frac{10}{R+3}$$

$$\Rightarrow 0.5R + 1.5 = 10$$

$$\Rightarrow 0.5R = 9.5 \rightarrow 8.5$$

$$\Rightarrow R = 17 \Omega$$

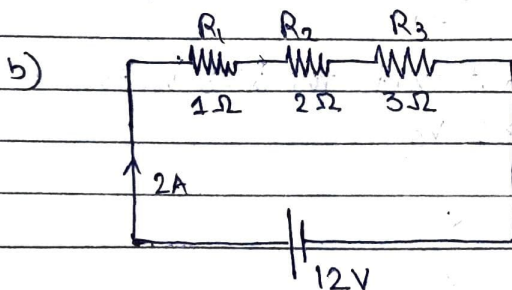3.3) a) $R_{\text{eq}} = 1\Omega + 2\Omega + 3\Omega = 6\Omega$



$$I = \frac{V}{R} = \frac{12}{6} = 2 \text{ A}$$

$$R_1: V_1 = IR_1 = 2 \times 1 = 2 \text{ V}$$


$$R_2: V_2 = IR_2 = 2 \times 2 = 4 \text{ V}$$

$$R_3: V_3 = IR_3 = 2 \times 3 = 6 \text{ V}$$

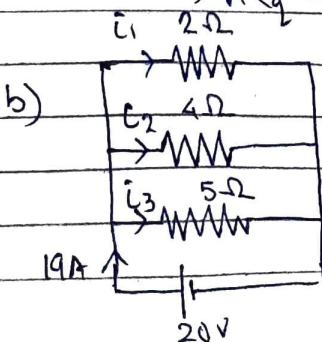3.4) $R_{\text{eq}} = \frac{1}{\frac{1}{2} + \frac{1}{4} + \frac{1}{5}}$

$$\Rightarrow \frac{1}{R_{\text{eq}}} = \frac{3}{4} + \frac{1}{5} \Rightarrow \frac{1}{R_{\text{eq}}} = \frac{(15+4)}{20}$$

$$\Rightarrow R_{\text{eq}} = \frac{20}{19} \Omega$$



Total current

$$\text{drawn } (I) = \frac{20}{19} \times 19 = 19 \text{ A}$$

$$i_1 = \frac{20}{2} = 10 \text{ A} ; i_2 = \frac{20}{4} = 5 \text{ A} ; i_3 = \frac{20}{5} = 4 \text{ A}$$

3.5) We know, $R \propto T$

$$\therefore R = kT \quad \alpha = 1.7 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{T_1}{T_2} \Rightarrow \frac{100}{100 - T} = \frac{1.7 \times 10^{-4} \times 27}{1.7 \times 10^{-4} \times T}$$

$$\alpha = R_1 - R_2$$

$$\frac{R(T_1 - T_2)}{R_1 - R_2}$$

$$\Rightarrow T_1 - T_2 = R_1 - R_2$$

$$\frac{R(T_1 - T_2)}{R_1 - R_2}$$

$$\Rightarrow T_1 - T_2 = R_1 - R_2 \Rightarrow T - 27 = 100 - 100$$

$$R \alpha$$

$$100 (1.7 \times 10^{-4})$$

$$\Rightarrow T - 27 = 100 \Rightarrow T = 1027 \text{ } ^\circ\text{C}$$

3.6) $R = \frac{\rho L}{A}$ [$\rho = \text{Resistivity}$]

$$\Rightarrow 5 = \frac{\rho \times 18}{6 \times 10^{-7}}$$

$$\Rightarrow \frac{5 \times 6 \times 10^{-7}}{18} = \rho \Rightarrow \rho = 2 \times 10^{-7}$$

3.7) $R_2 = R_1 [1 + \alpha(T_2 - T_1)]$

$$\Rightarrow 2.7 = 2.1 [1 + \alpha(100 - 27.5)]$$

$$\Rightarrow \frac{2.7}{2.1} = [1 + \alpha(72.5)]$$

$$\Rightarrow \frac{2.7}{2.1} - 1 = \alpha(72.5) \Rightarrow \frac{0.6}{2.1} = 72.5 \alpha$$

$$\Rightarrow \alpha = \frac{2 \times 10^2}{7 \times 125} = \frac{4}{7 \times 145}$$

$$= 0.0039 \text{ } ^\circ\text{C}^{-1}$$

$$3.8) H_1 = I^2 R_T \quad R_2 = R_1 [1 + \alpha(T_2 - T_1)]$$


$$= 3.2 \times 230^2 \times 300 \Rightarrow 230 = \frac{230}{3.2} [1 + \alpha(72 - 27)]$$

$$\Rightarrow \frac{22.8}{287} = 1 + (1.7 \times 10^{-4})(T_2 - 27)$$

$$\Rightarrow \frac{1}{97} = 1.7 \times 10^{-4} (T_2 - 27)$$

$$\Rightarrow T_2 = 867^\circ\text{C}$$

3.9)

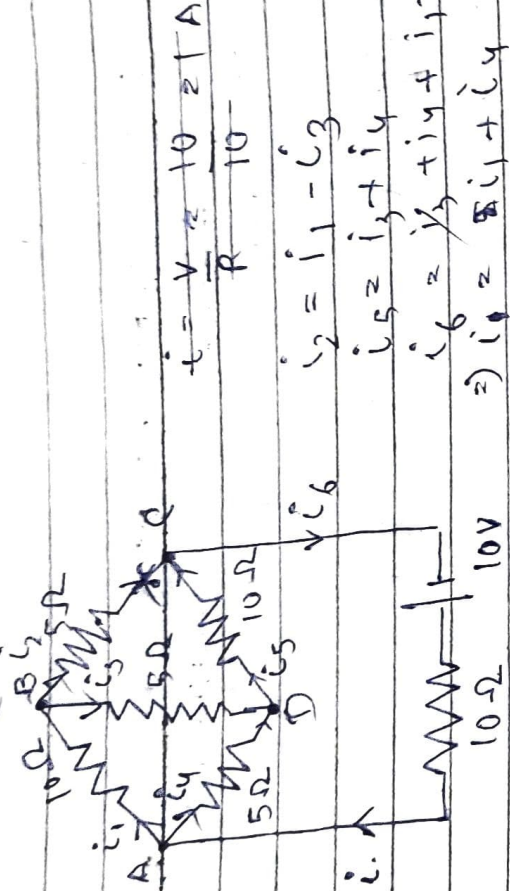

$$i = \frac{V}{R} = \frac{10}{10} = 1\text{A}$$

$$i_2 = i_1 - i_3$$

$$i_5 = i_3 + i_4$$

$$i_6 = \frac{1}{2} i_3 + i_4 + i_5 - i_3$$

$$\Rightarrow i_6 = i_1 + i_4$$

in closed circuits potential is zero.

$$i_1 \times 10 + i_3 \times 5 - i_4 \times 5 = 0$$

$$\Rightarrow 10i_1 + 5i_3 - 5i_4 = 0$$

$$\Rightarrow 2i_1 + i_3 - i_4 = 0$$

$$\Rightarrow 2i_1 + i_3 = i_4$$

$$2i_1 + i_3 = i_4$$

$$2i_1 - 8i_3 = 4i_4$$

$$(i_1 - i_3) \times 5 - 10(i_3 + i_4) - 5(i_3) = 0$$

$$5i_1 - 35i_3 = 50i_4$$

$$-3i_3 = 10i_4$$

$$\Rightarrow 5i_1 - 35i_3 - 2i_3 - 2i_4 - i_3 = 0$$

$$\Rightarrow i_1 - 4i_3 - 2i_4 = 0$$

$$\Rightarrow i_1 - 4i_3 = 2i_4$$

$$-10 + 10i_1 + 10(i_1) + 5(i_1 - i_3) = 0$$

$$\Rightarrow -10 + 20i_1 + 10i_1 - 5i_3 = 0$$

$$\Rightarrow 30i_1 + 2i_1 - 5i_3 = 10$$

$$\Rightarrow 32i_1 - 5i_3 = 10$$

$$i_2 = 2i_1 + i_3$$
$$\Rightarrow 4i_3 = 2i_2$$

$$\text{Also, } i = 11i_2$$

$$\therefore i_3 = \frac{2}{17} A \quad i_2 = 3(i_3) = \frac{6}{17} A$$

$$i_1 = 2(i_3) = \frac{4}{17} A$$

$$AB = \frac{4}{17} A \quad BC = \frac{6}{17} A \quad CD = \frac{4}{17} A$$

$$AD = \frac{6}{17} A \quad BD = \frac{2}{17} A$$

$$\text{Total} = \frac{10}{17} A$$

3.10) a) Balance pt. from A, $l_1 = 39.5 \text{ cm}$
Resistance of the resistor $Y = 12.5 \Omega$
Condition for the balance is given as

$$X = \frac{100 - l_1}{l_1}$$

$$2) X = 8.2 \Omega$$

The connections between resistors is made up of copper strips to minimize resistance.

b) If x & Y are interchanged, then l_1 & $100 - l_1$ get interchanged, then l_1 and $100 - l_1$ get interchanged.
The balance pt. of the bridge will be $100 - l_1$ from A.
 $100 - l_1 = 100 - 39.5 = 60.5 \text{ cm}$

c) When the galvanometer & cell are interchanged at the balance point of the bridge, the galvanometer will show no deflection. Thus no current flows through galvanometer.

$$3.11) V_{\text{eff}} = V - E$$
$$= 120 - 8 = 112 \text{ V}$$

$$I = \frac{V_{eff}}{R+r}$$

$$= \frac{112}{15.5+5} = 112 \approx 7A$$

voltage across resistor $R \Rightarrow V = 7 \times 15.5 = 108.5V$

terminal voltage = $120 - 108.5 = 11.5V$

3.12 A series resistor in charging circuit limits the current drawn from the external source.

$$3.12) E_1 = 1.25V \quad I_1 = 63 \mu A$$

$$I_1 = 35 \mu A \quad E_2 = 2$$

$$\frac{E_1}{E_2} = \frac{I_1}{I_2}$$

$$\Rightarrow E_2 = 1.25 \times \frac{63}{35} = 2.25V$$

$$3.13) I = n A e V_{eff}$$

$$\Rightarrow n A (1.6 \times 10^{-19}) \frac{1}{t}$$

$$\Rightarrow t = \frac{n A e V_{eff}}{I} \quad (1.6 \times 10^{-19}) d$$

$$= \frac{8.5 \times 10^{28} \times 1.6 \times 10^{-19} \times 1.6 \times 10^{-19} \times 2 \times 10^6 \times 3}{3}$$

$$= 2.7 \times 10^4 s$$

$$3.14) \sigma = 10^{-9} C m^{-2}$$

$$I = 1800 A$$

$$r = 6.37 \times 10^6 m$$

$$A = 4\pi r^2$$

$$= 4\pi (6.37 \times 10^6)^2 = 5.09 \times 10^{14} m^2$$

$$q = \sigma \times A$$

$$= 10^{-9} \times 5.09 \times 10^{14}$$

$$= 5.09 \times 10^5 C$$

$$I = \frac{q}{t} \Rightarrow t = \frac{q}{I} = 282.77 s$$

$$3.15) \quad a) \quad I = \frac{2 \times 6}{(60 \times 0.15 + 8.5)} \quad A = \frac{2 \times 6}{2.515 + 8.5} = \frac{12}{11.015} = 1.09 \text{ A}$$

$$V = IR = 1.39 \times 8.5 = 11.87 \text{ V}$$

$$b) \quad I_{\max} = \frac{E}{R} = \frac{1.9}{380} = 0.005 \text{ A}$$

Since a large current is reqd. to start the motor of a car, the cell cannot be used to start a motor.

$$3.16) \quad R_1 = \rho_1 \frac{l_1}{A_1} \quad \& \quad R_2 = \rho_2 \frac{l_2}{A_2}$$

$$R_1 = R_2$$

$$\rho_1 \frac{l_1}{A_1} = \rho_2 \frac{l_2}{A_2}$$

$$\& \quad l_1 = l_2$$

$$\therefore \rho_1 = \rho_2$$

$$\Rightarrow \frac{A_1 \rho}{A_2} = \frac{\rho}{1.72} = 2.63$$

$$m_1 = \text{vol} \times \text{density} = A_1 l_1 \times d_1 = A_1 l_1 d_1$$

$$m_2 = A_2 l_2 \times d_2$$

$$\therefore \frac{m_1}{m_2} = \frac{2.63}{1.72}$$

$$= 0.46$$

\therefore Aluminium of lighter.

3.17) The ratio of voltage & current is a const 19.7. Hence material is an ohmic conductor.

3.18) a) When a steady current flows in a metallic conductor of non-uniform cross-section, the current flowing through the conductor is const. Current density, electric

field and drift speed are inversely proportional to the area of cross-section. Therefore, they are not constant.

b) No, Ohm's law is not universally applicable for all conducting elements. Vacuum diode semiconductor is a non-ohmic conductor. Ohm's law is not valid for it.

c) According to Ohm's law the relation for potential is $V = IR$. voltage (V) & current (I)
 $I = V/R$

If V is low then R must be low so that high current can be drawn from the source.

d) In order to prohibit the current from exceeding the safety limit, a high tension supply must have a very large internal resistance. If the internal resistance is not large, then the current drawn can exceed the safety limits in case of a short circuit.

3.19 a) Alloys of metals usually have greater resistances than that of a metal by a their constituent metals.

b) Alloys usually have lower temperature coefficient of resistance than pure metals.

c) The resistivity of the alloy, manganin, is nearly independent of increase of temperature.

d) The resistivity of a typical insulator is greater than that of a metal by a factor of the order 10^{22} .

3.20 a) Total resistors = n each of resistance = R

i) When n resistors are connected in series, effective resistance R_1 is the maximum, given by the product nR

Hence, max Resistance of combination $R_1 = nR$


ii) When n resistors are connected in parallel the effective resistance (R_2) is the minimum given by R/n .

Hence, min Resistance of combination $R_2 = R/n$


$$\text{iii) } \frac{R_1}{R_2} = \frac{nR}{R/n} = n^2$$

b) $R_1 = 1\ \Omega$, $R_2 = 2\ \Omega$, $R_3 = 3\ \Omega$


i) $R_{eq} = 11/3$

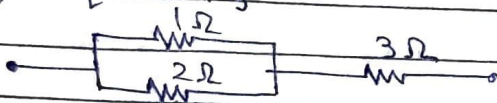


ii) $R_{eq} = 11/5\ \Omega$

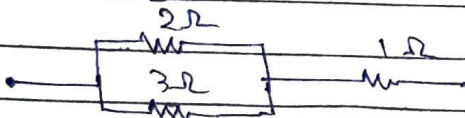


iii) $R_{eq} = 6\ \Omega$

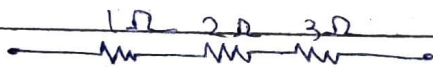

iv) $R_{eq} = 6/11\ \Omega$

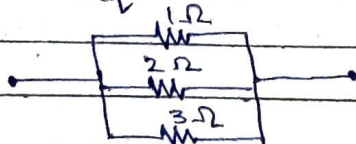

c) a) Redraw circuit,

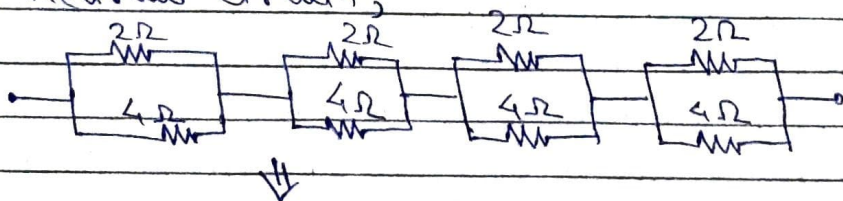

$\therefore R_{eq} = \frac{4}{3} \times 4 = \frac{16}{3}\ \Omega$

b) All are in series thus $R_{eq} = 5 \Omega$
 $\approx 5 \Omega$

3.21

$$R_{eq} = 2 + \frac{R_{eq}}{R_{eq} + 1}$$

$$\Rightarrow (R_{eq})^2 - 2R_{eq} - 2 = 0$$

$$\Rightarrow R_{eq} = \frac{2 \pm \sqrt{4 + 8}}{2} = 1 \pm \sqrt{3}$$

$$R_{eq} = 1 + \sqrt{3} = 2.73 \Omega$$

$$r = 0.5 \Omega$$

$$\text{Total } R = 3.23 \Omega$$

$$\text{Current drawn (I)} = \frac{12}{3.23} \approx 3.72 \text{ A}$$

3.22 a) Const. emf of the given standard cell, $E_1 = 1.02 \text{ V}$

Balance point on the wire, $l_1 = 67.3 \text{ cm}$

\therefore new balance pt. $l = 82.3 \text{ cm}$

The relation connecting emf and balance pt. is,

$$\frac{E_1}{l_1} = \frac{E}{l}$$

$$E = \frac{l}{l_1} \times E_1$$

$$= \frac{82.3}{67.3} \times 1.02 = 1.247 \text{ V}$$

b) The purpose of using the high resistance $600 \text{ k}\Omega$ to reduce the current through the galvanometer when the movable contact is far from the balance pt.

c) The balance pt. is not affected by the presence of high resistance.

d) The pt. is not affected by the internal resistance of the driver cell.

e) The method would not work if the driver cell of the potentiometer had an emf of 1 V instead of 2 V . This is because if the emf of the driver cell of the potentiometer is less than the emf of the other cell, then there would be no balance pt. on the wire.

f) The circuit would not work well for determining an extremely small emf. As the circuit would be unstable, the balance pt. would be close to end A. Hence there would be a large percentage of error. The given circuit can be modified if a series resistance is connected with the wire AB. The potential drop across AB is slightly greater than the emf measured. The percentage error would be small.

3.23

$$R = 10 \Omega, \quad l_1 = 58.3$$

$$E_1 = iR, \quad l_2 = 68.5 \text{ cm}, \quad E_2 = iX$$

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

$$\Rightarrow X = \frac{l_1}{l_2} \times R = \frac{68.5}{58.3} \times 10 = 11.749 \Omega$$

If we fail the potential drop across R & X must be reduced by putting resistance in series with it.

3.24

$$\text{We, know } r = \frac{l_1 - l_2}{l_2} R$$

$$= \frac{76.3 - 64.8}{64.8} \times 9.5 = 1.68 \Omega$$