

Current Electricity

3.1 Emf of the battery, $E = 12\text{V}$
Internal resistance of battery $= 0.4\Omega$
Maximum current drawn $= I$
According to ohm's law
 $E = I\gamma$

$$I = \frac{E}{\gamma}$$
$$= \frac{12}{0.4} = 30\text{A}$$

The maximum current drawn from the given battery is 30A .

3.2 $E = 10\text{V}$
 $\gamma = 3\Omega$
 $I = 0.5\text{A}$
Resistor $= R$

$$I = \frac{E}{R + \gamma}$$

$$R + \gamma = \frac{E}{I}$$
$$= \frac{10}{0.5} = 20\Omega$$

$$\therefore R = 20 - 3 = 17\Omega$$

Terminal voltage of the resistor $= V$
According to ohm's law
 $V = IR$
 $= 0.5 \times 17 = 8.5\text{V}$

3.3 (a) Three resistors of resistance 1Ω , 2Ω and 3Ω are combined in series. Total resistance of the combination is given by the algebraic sum of individual resistances

$$\text{Total resistance} = 1 + 2 + 3 = 6\Omega$$

(b) Current flowing through the circuit = I

$$E = 12V$$

$$R = 6\Omega$$

$$I = \frac{E}{R}$$

$$= \frac{12}{6} = 2A$$

Potential drop across 1Ω resistor = V_1

$$V_1 = 2 \times 1 = 2V \quad \text{--- (i)}$$

Potential drop across 2Ω resistor = V_2

$$V_2 = 2 \times 2 = 4V \quad \text{--- (ii)}$$

Potential drop across 3Ω resistor = V_3

$$V_3 = 2 \times 3 = 6V \quad \text{--- (iii)}$$

3.4 (a) There are three resistors of resistances $R_1 = 2\Omega$, $R_2 = 4\Omega$ and $R_3 = 5\Omega$

They are ~~connected~~ connected in parallel. Hence, total resistance (R) of the combination is given by,

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$= \frac{1}{2} + \frac{1}{4} + \frac{1}{5} = \frac{19}{20}$$

Total resistance of the combination is $\frac{20}{19}\Omega$

(b)

$$V = 20V$$

$$I_1 = \frac{V}{R_1} = \frac{20}{2} = 10A$$

Current (I_2) flowing through resistor R_2 is given by,

$$I_2 = \frac{V}{R_2} = \frac{20}{4} = 5A$$

Current (I_3) flowing through resistor R_3 is given by,

$$I_3 = \frac{V}{R_3} = \frac{20}{5} = 4A$$

Total current, $I = I_1 + I_2 + I_3 = 10 + 5 + 4 = 19A$

3.5

$$T = 27^\circ C$$

$$R = 100\Omega$$

Let T_1 is the increased temperature of the filament

$$R_1 = 117\Omega$$

$$\alpha = 1.70 \times 10^{-4} C^{-1}$$

$$\alpha = \frac{R_1 - R}{R(T_1 - T)}$$

$$T_1 - T = \frac{R_1 - R}{R\alpha}$$

$$T_1 - 27 = \frac{117 - 100}{100(1.7 \times 10^{-4})}$$

$$T_1 - 27 = 1000$$

$$T_1 = 1027^\circ C$$

3.6

$$l = 15 \text{ m}$$

$$a = 6.0 \times 10^{-7} \text{ m}^2$$

$$R = 5.0 \Omega$$

Resistivity of the material of the wire = ρ
Resistance is related with the resistivity as

$$R = \frac{\rho l}{A}$$

$$\rho = \frac{RA}{l}$$

$$= \frac{5 \times 6 \times 10^{-7}}{15} = 2 \times 10^{-7} \Omega \text{ m}$$

3.7

$$T_1 = 27.5^\circ \text{C}$$

$$R_1 = 2.1 \Omega$$

$$T_2 = 100^\circ \text{C}$$

$$R_2 = 2.7 \Omega$$

Temperature coefficient of Silver = α

$$\alpha = \frac{R_2 - R_1}{R_1(T_2 - T_1)}$$

$$= \frac{2.7 - 2.1}{2.1(100 - 27.5)} = 0.0039^\circ \text{C}^{-1}$$

3.8

$$V = 230 \text{ V}$$

$$I_1 = 3.2 \text{ A}$$

$$R_1 = \frac{V}{I}$$

$$= \frac{230}{3.2} = 71.87 \Omega$$

$$I_2 = 2.8 \text{ A}$$

$$R_2 = \frac{230}{2.8} = 82.14 \Omega$$

Temp Temp
Temperature

co-efficient of nichrome, $\alpha = 1.70 \times 10^{-4} \text{ } ^\circ \text{C}^{-1}$


$$T_1 = 27.0^\circ \text{C}$$

$$\alpha = \frac{R_2 - R_1}{R_1(T_2 - T_1)}$$

$$T_2 - 27^\circ \text{C} = \frac{82.14 - 71.87}{71.87 \times 1.7 \times 10^{-4}} = 840.5$$

$$T_2 = 840.5 + 27 = 867.5^\circ \text{C}$$

3.9

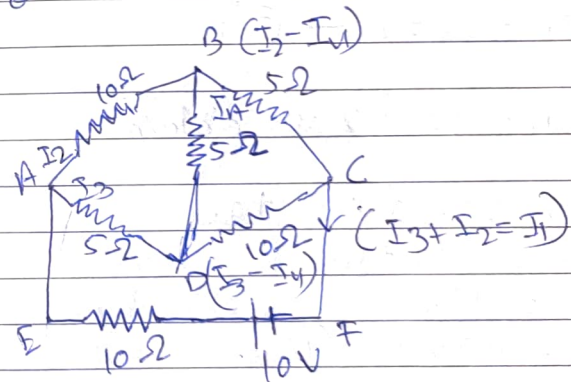

I_1 = Current flowing through the outer circuit

I_2 = current flowing through branch AB

I_3 = Current flowing through branch CD

$I_2 - I_4$ = Current flowing through branch AC

$I_3 + I_4$ = Current flowing through branch CD

I_4 = Current flowing through branch BD

For the closed circuit ABDA, potential is zero

$$10I_2 + 5I_4 - 5I_3 = 0$$

$$2I_2 + I_4 - I_3 = 0$$

$$I_3 = 2I_2 + I_4 \quad \text{--- (1)}$$

For the closed circuit BCDB potential is zero

$$5(I_2 - I_4) - 10(I_3 + I_4) - 5I_4 = 0$$

$$5I_2 + 5I_4 - 10I_3 - 20I_4 = 0$$

$$I_2 = 2I_3 + 4I_4 \quad \text{--- (2)}$$

For the closed circuit ABCFEA

$$-10 + 10(I_1) + 10(I_2) + 5(I_2 - I_4) = 0$$

$$10 = 15I_2 + 10I_1 - 5I_4$$

$$3I_2 + 2I_1 - I_4 = 2 \quad \text{--- (3)}$$

From eqn. 1 and 2 we obtain

$$I_3 = 2(2I_3 + 4I_4) + I_4$$

$$I_3 = 4I_3 + 8I_4 + I_4$$

$$-3I_3 = 9I_4$$

$$-3I_4 = +I_3 \quad \text{--- (4)}$$

$$\text{Current branch AB} = \frac{4}{17} \text{ A}$$

$$\text{branch BC} = \frac{6}{17} \text{ A}$$

$$\text{'' CD} = \frac{-4}{17} \text{ A}$$

$$\text{'' AD} = \frac{6}{17} \text{ A}$$

$$\text{branch BD} = \left(\frac{-2}{17}\right) \text{ A}$$

$$\text{Total current} = \frac{4}{17} + \frac{6}{17} + \frac{-4}{17} + \frac{6}{17} + \frac{2}{17} = \frac{10}{17} \text{ A}$$

$$3.11 \text{ (a) } E = 8.0 \text{ V}$$

$$r = 0.5 \Omega$$

$$V = 120 \text{ V}$$

$$R = 15.5 \Omega$$

Effective voltage = V'

$$V' = V - E$$

$$V' = 120 - 8 = 112 \text{ V}$$

$$I = \frac{V'}{R+r} = \frac{112}{15.5+0.5} = \frac{112}{16} = 7 \text{ A}$$

Voltage across resistor R given by the product
 $IR = 7 \times 15.5 = 108.5 \text{ V}$

DC supply voltage = Terminal voltage of battery
 + Voltage drop across R

Terminal voltage of battery = $120 - 108.5 = 11.5 \text{ V}$

A series resistor in a charging circuit limits the current drawn from the external source

$$3.12 \quad E_1 = 1.25 \text{ V}$$

$$T_1 = 35 \text{ cm}$$

The cell is replaced by another cell of emf E_2
 New balance point of the potentiometer, $l_2 = 30 \text{ cm}$

$$\frac{E_1}{E_2} = \frac{1}{2}$$

$$E_2 = E_1 \times \frac{1_2}{1_1}$$

$$= 1.25 \times \frac{63}{35} = 2.25V$$

Therefore emf of the secondary cell is 2.25V.

3.13 Number density of free electrons in a copper conductor, $n = 8.5 \times 10^{28} \text{ m}^{-3}$ length of the copper wire, $l = 3.0 \text{ m}$.

Area of cross-section of the wire, $A = 2.0 \times 10^{-6} \text{ m}^2$
Current carried by the wire, $I = 3.0 \text{ A}$

$$e = \text{Electric charge} = 1.6 \times 10^{-19} \text{ C}$$

v_d = Drift velocity

$$I = nAe v_d$$

$$= \frac{3 \times 8.5 \times 10^{28} \times 2 \times 10^{-6} \times 1.6 \times 10^{-19}}{3.0}$$

$$= 8.27 \times 10^4 \text{ s}$$

3.14

$$\sigma = 10^{-9} \text{ cm}^{-2}$$

$$I = 1800 \text{ A}$$

$$r = 6.37 \times 10^6 \text{ m}$$

Surface area of the earth,

$$A = 4\pi r^2$$

$$= 4\pi \times (6.37 \times 10^6)^2$$

$$= 5.09 \times 10^{14} \text{ m}^2$$

charge on the earth surface,

$$q = \sigma \times A$$

$$= 10^{-9} \times 5.09 \times 10^{14}$$

$$= 5.09 \times 10^5 \text{ C}$$

Time taken to neutralize the earth's surface = t

$$I = \frac{q}{t}$$

Current,

$$t = \frac{q}{I}$$

$$= \frac{5.09 \times 10^5}{1800} = 282.77 \text{ s}$$

3.15

(a) $n = 6$

$$E = 2.0 \text{ V}$$

$$r = 0.015 \Omega$$

Resistance of the resistor, $R = 8.5 \Omega$

Current drawn from the supply = I

$$I = \frac{NE}{R + nr}$$

$$= \frac{6 \times 2}{8.5 + 6 \times 0.015} = \frac{12}{8.59} = 1.39 \text{ A}$$

$$V = IR = 1.39 \times 8.5 = 11.87 \text{ A}$$

- (b) After a long use, emf of the secondary cell, $E = 1.9 \text{ V}$
Internal resistance of the cell, $r = 380 \Omega$

$$\text{Maximum current} = \frac{E}{r} = \frac{1.9}{380} = 0.005 \text{ A}$$

- 17 It can be inferred from the given table that the ratio of voltage with current is a constant, which is equal to 19.7. Hence, manganin is an ohmic conductor, the alloy obeys ohm's law. According to ohm's law, the ratio of voltage with current is the resistance of the conductor. Hence the resistance of manganin is 19.7 Ω .

- 18 (a) When a steady ~~current~~ current flows in a metallic conductor of non uniform cross section, the current flowing through the conductor is constant.

- (b) No, ohm's law is not universally applicable for all conducting elements. Vacuum diode semiconductor is a non ohmic conductor. ohm's law is not valid for it.

- (c) According to ohm's ~~law~~ law, the relation for all ~~conducting~~ ~~and~~ elements. Vacuum

- (c) According to ohm's law the relation for the potential is $V = IR$

Voltage (V) is directly proportional to current

(I).

R is the internal resistance of the source.

$$I = \frac{V}{R}$$

- (d) In order to prohibit the current from exceeding the safety limit, a high tension supply must have a very large internal resistance. If the internal resistance is not large, then the current drawn can exceed the safety limits in case of a short circuit.

- 2.19 (a) Alloys of metals usually have greater resistivity than that of ~~the~~ their constituent metals

- (b) Alloys usually have a lower temp. coefficient of resistance than pure metals

- (c) The resistivity of the ~~resistance~~ alloy, manganin is nearly independent of increase of temperature.

- (d) The resistivity of a typical insulator is greater than that of a metal by a factor of the order of 10^{22} .

3.21 The resistance of each resistor connected in the given circuit, $R = 1\Omega$
Equivalent resistance of the given circuit = R

$$\therefore R = 2 + \frac{R}{R+1}$$

$$(R)^2 - 2R - 2 = 0$$

$$R = \frac{2 \pm \sqrt{4+8}}{2}$$

$$= \frac{2 \pm \sqrt{12}}{2} = 1 \pm \sqrt{3}$$

Negative value of R' cannot be ~~not~~ accepted.

$$R = (1 + \sqrt{3}) = 1 + 1.73 = 2.73\Omega$$

$$r = 0.5\Omega$$

Total resistance of the given circuit = $2.73 + 0.5 = 3.23\Omega$

Supply voltage, $V = 12V$

3.22 (a) $E_1 = 1.02V$

Balance point on the wire, $l_1 = 67.3\text{ cm}$

A cell of unknown emf, ϵ replaced the ~~star~~ standard cell. Therefore new balance point on the wire, $l = 82.3\text{ cm}$.

$$\frac{E_1}{l_1} = \frac{\epsilon}{l}$$

$$\epsilon = \frac{l}{l_1} \times E_1 = \frac{82.3}{67.3} \times 1.02 = 1.247V$$

(b) The purpose of using the high resistance of $600\text{ k}\Omega$ is to reduce the current through the galvanometer when the movable contact is far from the balance point.

(c) The balance point is not ~~affected~~ affected by the ~~external~~ presence of high resistance

(d) The point is not affected by the internal resistance of the driver cell.

Ex 3.23 $R = 10.0\Omega$

Balance point for this resistance, $l_1 = 58.3\text{ cm}$
Current in the potentiometer wire = i

Hence, potential drop across R , $E_1 = iR$

Resistance of the unknown resistor = X

Balance point for this resistor, $l_2 = 68.5\text{ cm}$

$$E_2 = iX$$

A/G

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

$$\frac{iR}{iX} = \frac{l_1}{l_2}$$

$$X = \frac{l_2}{l_1} \times R$$

$$= \frac{68.5}{58.3} \times 10 = 11.749\Omega$$

3.24

Internal resistance of the cell = r
Balance point of the cell in open circuit,
 $l_1 = 76.3 \text{ cm}$

An external resistance (R) is connected to the circuit with $R = 9.5 \Omega$

New balance point of the circuit, $l_2 = 64.8 \text{ cm}$
Current flowing through the circuit = I

The relation connecting resistance is

$$r = \left(\frac{l_1 - l_2}{l_2} \right) R$$

$$= \frac{76.3 - 64.8}{64.8} \times 9.5 = 1.69 \Omega$$