

Current Electricity
Next Solution

31

$$E = 12V$$

$$r = 0.4$$

Maximum current = I

$$E = I r$$

$$I = \frac{E}{r}$$

$$= \frac{12}{0.4} = 30A$$

32

$$E = 10V$$

$$r = 3\Omega$$

$$I = 0.5A$$

Resistance of Resistor = R

$$I = \frac{E}{R+r}$$

$$R+r = \frac{E}{I} = \frac{10}{0.5} = 20\Omega$$

$$R = 20 - 3 = 17\Omega$$

Terminal Voltage of Resistor = V

$$V = IR \\ = 0.5 \times 17 \\ = 8.5 \text{ V}$$

3.3
a) $R_s = 1\Omega + 2\Omega + 3\Omega = 6\Omega$

b) Current = I
Emf of battery = E = 12V
 $R = 6\Omega$

$$I = \frac{E}{R} = \frac{12}{6} = 2\text{A}$$

$$V_1 = 2 \times 1 = 2\text{V}$$

$$V_2 = 2 \times 2 = 4\text{V}$$

$$V_3 = 2 \times 3 = 6\text{V}$$

Potential drop across 1Ω , 2Ω , 3Ω resistors are 2V , 4V and 6V

24

a)

$R_1 = 2\Omega$
 $R_2 = 4\Omega$
 $R_3 = 5\Omega$

$$\frac{1}{R_{eq}} = \frac{1}{2} + \frac{1}{4} + \frac{1}{5}$$

$$R_{eq} = \frac{19}{20}$$

$$R_{eq} = \frac{20}{19}$$

b) Emf of battery $V = 20V$

$$I_1 = \frac{V}{R_1} = \frac{20}{2} = 10A$$

$$I_2 = \frac{V}{R_2} = \frac{20}{4} = 5A$$

$$I_3 = \frac{V}{R_3} = \frac{20}{5} = 4A$$

$$I = I_1 + I_2 + I_3 = 10 + 5 + 4 = 19A$$

3.5

33

$T = 27^\circ\text{C}$
Resistance of heating element at T , $R = 100\Omega$

T_1 is increased temperature
Resistance of heating element at T_1 , $R_1 = 117\Omega$

Temperature co-efficient of material of filament

$$\alpha = 1.7 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}$$

$$\alpha = \frac{R_1 - R}{R(T_1 - T)}$$

$$T_1 - T = \frac{R_1 - R}{R\alpha}$$

$$T_1 - 27 = \frac{117 - 100}{100(1.7 \times 10^{-4})}$$

$$T_1 - 27 = 1000$$

$$T_1 = 1027^\circ$$

36

Length of wire = 15 m
 Area = $6.0 \times 10^{-7} \text{ m}^2$
 $R = 5.0 \Omega$
 Resistivity = ρ

$$R = \frac{\rho l}{A}$$

$$\rho = \frac{RA}{l}$$

$$= \frac{5 \times 6 \times 10^{-7}}{15} = 2 \times 10^{-7} \Omega \text{ m}$$

3.7

$$T_1 = 27.5^\circ \text{C}$$

Resistance of silver wire
 at T_1 , $R_1 = 2.1 \Omega$

$$T_2 = 100^\circ \text{C}$$

Resistance of silver wire at T_2 , $R_2 = 2.7 \Omega$

Temperature coefficient of silver

$$\alpha = \frac{R_2 - R_1}{R_1 (T_2 - T_1)}$$

$$= \frac{2.7 - 2.1}{2.1 (100 - 27.5)} = 0.0039^\circ \text{C}^{-1}$$

3.5

$$V = 230V$$
$$I_1 = 3.2A$$

$$R_1 = \frac{V}{I} = \frac{230}{3.2} = 71.87\Omega$$

Steady state value of current, $I_2 = 2.8A$

$$R_2 = \frac{230}{2.8} = 82.14\Omega$$

$$\alpha = 1.7 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}$$

$$T_1 = 27^\circ\text{C}$$

Study state temperature reached by nichrome = T_2 .

T_2 can be obtained

$$\alpha = \frac{R_2 - R_1}{R_1(T_2 - T_1)} = \frac{82.14 - 71.87}{71.87(T_2 - 27)}$$

$$= 840.5$$

$$T_2 = 840.5 + 27 = 867.5^\circ\text{C}$$

39

I_1 = current flowing through
outer circuit

I_2 = current through branch AB

I_3 = current through branch AD

$I_2 - I_4$ = Current through BC

$I_3 + I_4$ = Current through CD

I_4 = Current through BD

In circuit ABDA

$$10I_2 + 5I_4 - 5I_3 = 0$$

$$I_3 = 2I_2 + I_4 \quad \text{--- (1)}$$

For circuit BCD

$$5(I_2 - I_4) - 10(I_3 + I_4) + 5I_4 = 0$$

$$I_2 = 2I_3 + 4I_4 \quad \text{--- (2)}$$

In circuit ABC FEA

$$-10 + 10(I_1) + 10(I_2) + 5(I_2 - I_1) + 10$$

$$10 = 5I_2 + 10I_1 - 5I_4$$

$$3I_2 + 2I_1 - I_4 = 2 \quad \text{--- (3)}$$

from loop 2

$$I_3 = 2(2I_3 + 4I_4) + I_4$$

$$I_3 = 4I_3 + 8I_4 + I_4$$

$$-3I_3 = 9I_4$$

$$-3I_4 = I_3 \quad \text{--- (4)}$$

$$I_3 = 2I_2 + I_4$$

$$I_2 = -2I_4$$

$$I_1 = I_3 + I_2$$

Current in branch

$$AB = \frac{4}{17} A$$

$$BC = \frac{6}{17} A$$

$$CD = -\frac{4}{17} A$$

$$AD = \frac{6}{17} A$$

$$BD = -\frac{2}{17} A$$

$$\begin{aligned} \text{Total current} &= \frac{4}{17} + \frac{6}{17} - \frac{4}{17} + \frac{6}{17} - \frac{2}{17} \\ &= \frac{10}{17} A \end{aligned}$$

310

a) B
R

b)

c)

Balance point found
 Distance of balance point from end A = 100 cm
 Distance of mass from end A = 25 cm
 $100 \times 1 = 25 \times 2$
 $100 = 50$
 $100 - 50 = 50$

When 1 and 2 are interchanged
 Distance of mass from end A = 75 cm
 Distance of balance point from end A = 50 cm
 $100 \times 1 = 75 \times 2$
 $100 = 150$
 $100 - 150 = -50$

When the galvanometer
 and cells are interchanged
 at balance point of the
 bridge. The galvanometer
 will show no deflection.
 Hence, no current will
 flow through the galvanometer.

311

$$E = 8.0 \text{ V}$$

$$r = 0.5 \Omega$$

$$V = 120 \text{ V}$$

$$R = 15.5 \Omega$$

Effective voltage = V'

$$V' = V - E$$

$$V' = 120 - 8 = 112 \text{ V}$$

$$I = \frac{V'}{R+r} = \frac{112}{15.5+0.5} = \frac{112}{16} = 7 \text{ A}$$

Voltage, $IR = 7 \times 15.5 = 108.5 \text{ V}$

DC supply Voltage - Terminal Voltage + Voltage drop across

$$\begin{aligned} \text{Terminal Voltage} &= 120 - 108.5 \\ &= 11.5 \text{ V} \end{aligned}$$

A series resistor in a charging circuit limits the current drawn from external source

de-current will be distributed
high in its absence. Critical
very dangerous

$$E_1 = 1.25V$$

Balance point = $l_1 = 35\text{cm}$

The cell is replaced by
another cell of emf E_2

New balance point, $l_2 = 63\text{cm}$

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

$$E_2 = E_1 \times \frac{l_2}{l_1}$$

$$= 1.25 \times \frac{63}{35} = 2.25V$$

3.13

$$n = 8.5 \times 10^{28} \text{ m}^{-3}$$

$$A = 2 \times 10^{-6} \text{ m}^2$$

$$I = n A e v_d$$

$$I = n A e \rho \frac{L}{E}$$

$$t = \frac{n A e \rho L}{I}$$

$$= \frac{3 \times 8.5 \times 10^{28} \times 2 \times 10^{-6} \times 1.6 \times 10^{19}}$$

$$= 2.7 \times 10^4 \text{ s}$$

3.14

$$\sigma = 10^{-9} \text{ C m}^{-2}$$

$$I = 1800 \text{ A}$$

$$r = 6.37 \times 10^6 \text{ m}$$

$$A = 4 \pi r^2$$

$$= 4 \pi (6.37 \times 10^6)^2$$

$$= 5.09 \times 10^{14} \text{ m}^2$$

$$q = \sigma \times A$$

$$= 10^{-9} \times 5.09 \times 10^{14}$$

$$= 5.09 \times 10^5 \text{ C}$$

$$I = \frac{qV}{r}$$

$$I = \frac{qV}{r} = \frac{5.09 \times 10^5}{1800} = 282.78$$

2.15

(a) Number of secondary cells =
Emf of each secondary cell, $E = 20V$

$$r = 0.015 \Omega$$

$$R = 8.5 \Omega$$

$$I = \frac{nE}{R + nr}$$

$$= \frac{6 \times 2}{8.5 + 6 \times 0.015} = \frac{12}{8.59} = 1.39A$$

$$V = IR = 1.39 \times 8.5 = 11.87A$$

$$(b) E = 1.9V$$

$$r = 380 \Omega$$

$$\text{Maximum current} = \frac{E}{r} = \frac{1.9}{380} = 0.005A$$

since a large current is required to start the motor of a car, the cell cannot be used to start a motor

316

$$\rho_{Al} = 2.63 \times 10^{-8} \Omega \cdot m$$

$d_1 = 2.7$
 l_1 be length of aluminium wire and m_1 be its mass

Resistance of aluminium wire R_1

Area of cross-section of aluminium wire A_1

Resistivity of copper, $\rho_{Cu} = 1.72 \times 10^{-8} \Omega \cdot m$
 $d_2 = 8.9$

$$R_1 = \rho_1 \frac{l_1}{A_1}$$

$$R_2 = \rho_2 \frac{l_2}{A_2}$$

$$R_1 = R_2$$

$$L_1 = L_2$$

$$\frac{P_1}{A_1} = \frac{P_2}{A_2}$$

$$\frac{A_1}{A_2} = \frac{P_1}{P_2}$$

$$= \frac{2.63 \times 10^{-8}}{1.72 \times 10^{-8}} = \frac{2.63}{1.72}$$

$$M_1 = \text{Volume} \times \text{Density} \\ = A_1 L_1 \times d_1 = A_1 L_1 d_1$$

$$M_2 = \text{Volume} \times \text{Density} \\ = A_2 L_2 \times d_2 = A_2 L_2 d_2$$

$$\frac{M_1}{M_2} = \frac{A_1 L_1 d_1}{A_2 L_2 d_2}$$

$$L_1 = L_2$$

$$\frac{M_1}{M_2} = \frac{A_1 d_1}{A_2 d_2}$$

$$\frac{A_1}{A_2} = \frac{2.63}{1.72}$$

$$\frac{m_1}{m_2} = \frac{2.63 \times 2.7}{1.72 \times 89} = 0.4$$

It can be inferred from this ratio that m_1 is less than m_2 . Hence, aluminium is lighter than copper.

Since aluminium is lighter it is preferred for overhead power cables over copper.

3.17

It can be inferred from the given table that the ratio of voltage with current is a constant which is equal to 19.7.

Hence manganese is an ohmic conductor if the alloy obey ohm's law. According to ohm's law, the ratio of voltage with ~~resistance~~ current is resistance.

Hence, the resistance of manganese is 19.7Ω .

When a steady current flows in a metallic conductor of non-uniform cross-section, the number of free electrons per unit volume is constant. The drift speed of electrons is proportional to the area of cross-section. Charges are not conserved.

No, Ohm's law is not universally applicable for all conducting elements. Vacuum diode semiconductor is a non-ohmic conductor. Ohm's law is not valid for it.

According to Ohm's law the relation of potential is $V = IR$

If V is low then R must be very low so that high current can be drawn from source.

2) In order to prohibit the current from exceeding the safety limit, a high tension supply must have a very large internal resistance. If the internal resistance is not large then the current drawn can exceed the safety limits in case of short-circuit.

3.19

a) Alloys of metals usually have greater resistivity than that of their constituent metals.

b) Alloys usually have lower temperature coefficient of resistance than pure metals.

c) The resistivity of an alloy manganin is nearly independent of increase of temperature.

d) The resistivity of a typical insulator is greater than that of a metal by a factor of order of 10^9 .

34
i) Total number of resistors = n
Resistance of each resistor = R

ii) n resistors in series effective resistance R_1 is the maximum given by nR

$$R_1 = nR$$

iii) When n resistors are connected in parallel effective resistance R_2 is minimum given by $\frac{R}{n}$

iv) The ratio of maximum to minimum resistance is

$$\frac{R_1}{R_2} = \frac{nR}{\frac{R}{n}} = n^2$$

35
v) Equivalent resistance

$$R = \frac{2 \times 1}{2+1} + 3 = \frac{2}{3} + 3 = \frac{11}{3}$$

(i) Equivalent Resistance

$$R = \frac{2 \times 3}{2+3} = \frac{6}{5} \Omega$$

(ii) Equivalent Resistance

$$R = \frac{1 \times 2 \times 3}{1+2+3} = \frac{6}{6} \Omega$$

(iii) Equivalent Resistance

$$R = \frac{1 \times 2 \times 3}{1+2+3} = \frac{6}{6} \Omega$$

$$(iv) R = \frac{2 \times 4}{2+4} = \frac{8}{6} = \frac{4}{3} \Omega$$

(v) Longest resistance of 4 connected in series

$$\frac{4 \times 4}{3} = \frac{16}{3} \Omega$$

$$(vi) Long - 3R + R + R + R + R = 5R$$

$$R = 2 + \frac{R}{R+1}$$

$$R^2 - 2R - 2 = 0$$

$$R = \frac{2 \pm \sqrt{4+8}}{2} = \frac{2 \pm \sqrt{12}}{2} = 1 \pm \sqrt{3}$$

$$R = (1 + \sqrt{3}) = 2.73 \Omega$$

$$r = 0.5 \Omega$$

$$\text{Total resistance} = 2.73 + 0.5 = 3.23 \Omega$$

$V = 12V$

current drawn from source
is given by $\frac{12}{3.23} = 3.72A$

323

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

$$\frac{l_1 R}{l_2 X} = \frac{l_1}{l_2}$$

$$X = \frac{l_1}{l_2} \times R$$

$$= \frac{68.5}{58.3} \times 10 = 11.74 \Omega$$

X is 11.75Ω

324

The relation connecting resistance and emf is

$$x = \frac{(l_1 - l_2) R}{l_2}$$

$$= \frac{763 - 64.8}{64.8} \times 9.5 = 1.68 \Omega$$