

Electric Current

(1.1) $\mathcal{E} = 12V$

$r = 0.4 \Omega$

∴ For maximum current, $R = 0$;

$$\Rightarrow I_{max} = \frac{\mathcal{E}}{r+R} = \frac{12}{0.4+0} = \frac{12}{0.4} = 30A$$

(1.2) $\mathcal{E} = 10V$

$r = 3 \Omega$

$I = 0.5A$

$R = ?$

$$\therefore I = \frac{\mathcal{E}}{r+R} \Rightarrow 0.5 = \frac{10}{3+R}$$

$$\Rightarrow 10 = 1.5 + 0.5R \Rightarrow 8.5 = 0.5R$$

$$\Rightarrow R = \frac{8.5}{0.5} = 17 \Omega$$

(3.3) $R_1 = 1 \Omega$

$R_3 = 3 \Omega$

$R_2 = 2 \Omega$

(a) ∴ $R_{eq} = R_1 + R_2 + R_3 = 1 + 2 + 3 = 6 \Omega$

(b) $\frac{\mathcal{E}}{r+R} = I \Rightarrow I = \frac{12}{6} = 2A$

$V_1 = IR_1 = 2 \times 1 = 2V$

$V_2 = IR_2 = 2 \times 2 = 4V$

$V_3 = IR_3 = 2 \times 3 = 6V$

(3.4) $R_1 = 2 \Omega$

$R_3 = 5 \Omega$

$R_2 = 4 \Omega$

$$(a) \frac{1}{R_{eq}} = \frac{1}{2} + \frac{1}{4} + \frac{1}{5} \Rightarrow \frac{1}{R_{eq}} = \frac{10+4+5}{20}$$

$$\Rightarrow R_{eq} = \frac{20}{19}$$

$$(b) \frac{\mathcal{E}}{R+R} = I \Rightarrow I = \frac{20}{20/19} \Rightarrow I = 19$$

$$\Rightarrow V_{net} = IR = 19 \times \frac{20}{19} = \underline{20V}$$

$$I_1 = \frac{V}{R_1} = \frac{20}{2} = \underline{10A}$$

$$I_2 = \frac{V}{R_2} = \frac{20}{4} = \underline{5A}$$

$$I_3 = \frac{V}{R_3} = \frac{20}{5} = \underline{4A}$$

(3.5) $T_1 = 27^\circ$ $T_2 = ?$
 $R_1 = 100$ $R_2 = 117$
 $\alpha = 1.70 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}$

$$\Rightarrow \alpha = \frac{R_2 - R_1}{R_1(T_2 - T_1)} \Rightarrow 1.70 \times 10^{-4} = \frac{(117 - 100)}{100(T_2 - 27)}$$

$$\Rightarrow \frac{1.70 \times 10^{-2}}{100} = \frac{17}{T_2 - 27}$$

$$\Rightarrow T_2 - 27 = 100 \Rightarrow T_2 = 1027^\circ\text{C}$$

(3.6) $A = 6 \times 10^{-7}$ $L = 15\text{m}$
 $R = 5\Omega$

$$P = \frac{R \times A}{L} = \frac{6 \times 10^{-7} \times 5}{153} = 2 \times 10^{-7} \text{ } \Omega\text{m}$$

3.7 $R_1 = 2.1$
 $T_1 = 27.5$

$R_2 = 2.7$
 $T_2 = 100$

$$\alpha = \frac{(R_2 - R_1)}{R_1 (T_2 - T_1)} = \frac{(2.7 - 2.1)}{2.1 (100 - 27.5)}$$

$$= \frac{0.6}{2.1 \times 72.5} = 0.0039 \text{ } ^\circ\text{C}^{-1}$$

(3.8) $\alpha = 1.7 \times 10^{-4}$

$R_1 = \frac{230}{3.2} = 71.87$

$R_2 = \frac{230}{2.8} = 82.14$

$T_1 = 27^\circ\text{C}$

$T_2 = ?$

$$\alpha = \frac{R_2 - R_1}{R_1 (T_2 - T_1)} \Rightarrow 1.7 \times 10^{-4} = \frac{(82.14 - 71.87)}{71.87 (T_2 - 27)}$$

$\Rightarrow T_2 = 27 = 840$

$\Rightarrow T_2 = 867$

(3.9) $\frac{10}{5} \neq \frac{5}{10}$. The bridge is not balanced, hence current will flow through the path BD

Loop ABDA

$$\Rightarrow 10I_1 + 5I_g - 5I_2 = 0$$

Loop BCBDB

$$\Rightarrow 5(I_1 - I_g) + 10(I_2 + I_g) + 5I_g = 0 \Rightarrow 5I_1 - 20I_g - 10I_2 = 0$$

Loop ADCA

$$\Rightarrow 5I_2 + 10(I_g + I_2) + 10(I_1 + I_2) = 10$$

$$\Rightarrow 10I_1 + 25I_2 + 10I_g = 10$$

$$-5I_1 + 5I_2 = 5I_g \Rightarrow I_g = -I_1 + I_2$$

$$\Rightarrow 5I_1 - 20I_g - 10I_2 = 0$$

$$\Rightarrow I_1 - 4(-I_1 + I_2) - 2I_2 = 0$$

$$\Rightarrow 9I_1 - 6I_2 = 0 \Rightarrow 3I_1 - 2I_2 = 0 \quad \text{--- (i)}$$

$$10I_1 + 25I_2 + 10I_g = 10$$

$$\Rightarrow 2I_1 + 5I_2 + 2I_g = 2$$

$$\Rightarrow 2I_1 + 5I_2 + 2(-I_1 + I_2) = 2$$

$$\Rightarrow -2I_1 + 7I_2 = 2 \quad \text{--- (ii)}$$

$$\begin{aligned} -2I_1 + 7I_2 &= 6 & \Rightarrow & -6I_1 + 21I_2 = 6 \\ 3I_1 - 2I_2 &= 0 & \Rightarrow & -6I_1 - 4I_2 = 0 \\ & & & \hline & & & 17I_2 = 6 \Rightarrow I_2 = \frac{6}{17} \end{aligned}$$

$$\begin{aligned} 3I_1 - 2I_2 &= 0 \Rightarrow 3I_1 = 2I_2 \\ & \Rightarrow 3I_1 = 2 \times \frac{6}{17} \Rightarrow I_1 = \frac{4}{17} \end{aligned}$$

$$I_g = -2I_1 + I_2 = \frac{-2 \times 4}{17} + \frac{6}{17} = \left(\frac{-2}{17} \right) \text{ A}$$

In branch AB = $\left(\frac{4}{17} \right)$

" " BC = $\frac{4}{17} - \left(\frac{-2}{17} \right) = \left(\frac{6}{17} \right)$

" " DD = $\left(\frac{-2}{17} \right)$

" " AD = $\left(\frac{6}{17} \right)$

" " BD = $\frac{6 - 2}{17} = \left(\frac{4}{17} \right)$

(B-10)

(a) $l_1 = 39.5 \text{ cm}$

$x = ?$

$y = 12.5$

\therefore for balance condition

$$\frac{x}{y} = \frac{100 - l_1}{l_1} \Rightarrow \frac{x}{12.5} = \frac{60.5}{39.5}$$

$$\Rightarrow x = \frac{60.5 \times 12.5}{39.5} = 8.16 \Omega$$

Thick copper strip are taken here to minimize the resistance.

(4) If x & y are interchanged, balance point will be l_2

$$\frac{y}{x} = \frac{100 - l_2}{l_2}$$

$$\Rightarrow \frac{12.5}{8.16} = \frac{l_2}{100 - l_2} \Rightarrow l_2 = 60.5$$

(5) If galvanometre & battery cell are interchanged, the galvanometre will show no deflection, hence no current will flow through it.

3

(3.11) $E = 8V$ $V = 120V$
 $R = 15.5$ $r = 0.5$

$$V_{\text{net}} = V - E = 120 - 8 = 112V$$

$$\therefore I = \frac{V_{\text{net}}}{R + r} = \frac{112}{15.5 + 0.5} = \frac{112}{16} = 7A$$

$$\text{Voltage across } R = 7 \times 15.5 = 108.5$$

$$\begin{aligned} \therefore \text{Terminal voltage} &= \text{Total voltage} - \text{Voltage drop} \\ &= 120 - 108.5 \\ &= 11.5V \end{aligned}$$

(3.12) $E_1 = 1.25V$ $l = 35$
 $E_2 = ?$ $l_2 = 63$

$$\begin{aligned} \therefore \frac{E_1}{E_2} &= \frac{l_1}{l_2} \Rightarrow \frac{1.25}{E_2} = \frac{35}{63} \Rightarrow E_2 = \frac{1.25 \times 63}{35} \\ &= 2.25V \end{aligned}$$

$$(B-13) \quad n = 8.5 \times 10^{28}$$

$$A = 2 \times 10^{-6}$$

$$I = 3A$$

$$\therefore \cancel{V_d} = \cancel{I} = neAv_d \Rightarrow v_d = \frac{I}{neA}$$

$$\Rightarrow \underline{v_d} = \frac{3A}{8.5 \times 10^{28} \times 1.6 \times 10^{-19} \times 2 \times 10^{-6}}$$

$$\therefore \text{total time take} = \frac{\text{drift velocity}}{\text{length}}$$

$$= \frac{3}{3} = 3 \times 8.5 \times 1.6 \times 2 \times 10^3$$

$$8.5 \times 1.6 \times 2 \times 10^3$$

$$= 27 \times 10^3 = 2.7 \times 10^4 \text{ s}$$

$$(B-14) \quad \sigma = 10^{-9} \text{ C/m}^2$$

$$I = 1800A$$

$$n = 6.37 \times 10^6$$

$$\therefore A = 4\pi n^2$$

$$= 4 \times 3.14 \times (6.37 \times 10^6)^2$$

$$= 5.09 \times 10^{14}$$

$$q = \sigma A$$

$$= 10^{-9} \times 5 \times 10^{14} = 5 \times 10^5$$

$$I = \frac{q}{t} = \frac{5 \times 10^5}{1800} = 282.77 \text{ s}$$

315 (a) no. of secondary cells (n) = 6

Emf of each cell = 2.0

$$r = 0.015$$

$$R = 8.5$$

$$\therefore I = \frac{n\varepsilon}{nr + R} = \frac{6 \times 2}{6 \times 0.015 + 8.5} = \frac{12}{8.59} = 1.39$$

$$\therefore \text{Terminal voltage} = IR = 1.39 \times 8.5 = 11.87 \text{ A}$$

(b) For maximum current; $I_{\text{max}} = \frac{\varepsilon}{r}$

$$\Rightarrow I_{\text{max}} = \frac{1.0}{380} = \frac{10}{23800} = 0.01 = 0.005 \text{ A}$$

The cell can't be used to drive a motor as it requires very large amount of current.

B-16) $\rho_{\text{Al}} = 2.63 \times 10^{-8} \Omega \text{m}$

$$(A)_d = 2.7$$

$$\rho_{\text{Cu}} = 1.72 \times 10^{-8} \Omega \text{m}$$

$$(A)_d = 8.9$$

$$R_1 = \frac{\rho L_1}{A_1}$$

$$R_2 = \frac{\rho L_2}{A_2}$$

$$R_1 = R_2 \Rightarrow \frac{\rho L_1}{A_1} = \frac{\rho L_2}{A_2}$$

$$\Rightarrow \frac{\rho_1}{A_1} = \frac{\rho_2}{A_2} \Rightarrow \frac{A_1}{A_2} = \frac{\rho_2}{\rho_1} = \frac{2.63 \times 10^{-8}}{1.72 \times 10^{-8}} \Rightarrow$$

$$\Rightarrow \frac{A_1}{A_2} = \frac{2.63}{1.72}$$

$$m_1 = \text{Volume} \times \text{density} = A_1 L_1 \times d_1 = A_1 L_2 d_2$$

$$m_2 = A_2 L_2 d_2$$

$$\Rightarrow \frac{m_1}{m_2} = \frac{A_1 l_1 d_1}{A_2 l_2 d_2}$$

$$\Rightarrow \frac{m_1}{m_2} = \frac{A_1 d_1}{A_2 d_2} = \frac{2.63}{1.72} \times \frac{2.7}{8.9} = 0.46$$

$$\therefore m_1 < m_2$$

\therefore Al is lighter than Cu. Thus aluminium is preferred over copper.

3.18

(a) When a steady current flows in a metallic conductor of non-uniform cross section; $I = \text{constant}$. Current density, electric field, & drift speed are inv proportional to the area of cross-section. Thus they are not constant.

(b) No; Ohm's law is not applicable for all conducting material. Vacuum diode semiconductor is non-ohmic conductor, Ohm's law is not valid for it.

(c) Acc to Ohm's law $\Rightarrow V = IR \Rightarrow V \propto I$
 R is internal resistance $\Rightarrow I = \frac{V}{R}$

If V is low, R should be very low, so that I will be high.

(d) In order to prevent the current from exceeding the safety limit, a high tension must be applied to have a very large internal resistance. If the int resistance is small, then the current drawn can exceed the safety limit in short circuit.
 case of

3-20

$$(i) (R_{eq})_{max} = nR$$

$$(R_{eq})_{min} = \frac{R}{n}$$

Ratio of max. to min. = $\frac{nR}{R/n} = n^2$

(i) $R = \frac{2 \times 1}{2+1} + 3 = \frac{2}{3} + 3 = \frac{2+9}{3} = \frac{11}{3}$

2Ω & 1Ω are in parallel & 3Ω in series.

(ii) $R = \frac{2 \times 3}{2+3} + 1 = \frac{6}{5} + 1 = \frac{11}{5}$

2Ω & 3Ω are in parallel & 1Ω in series.

(iii) $R_{eq} = 1+2+3 = 6\Omega$
 $\therefore 1\Omega, 2\Omega, 3\Omega$ are in series.

(iv) $\frac{1}{R_{eq}} = \frac{1}{1} + \frac{1}{2} + \frac{1}{3} \Rightarrow \frac{6+3+2}{6} = \frac{11}{6} \Rightarrow R_{eq} = \frac{6}{11}$

$\therefore 1, 2, 3\Omega$ are in parallel.

(v) (i) $R_{eq} = \frac{(1+1)(2+2)}{(1+1+2+2)} \Rightarrow R_{eq} =$

$\Rightarrow R_{eq} = \frac{2 \times 4}{8} = \frac{4}{3}$ (For 1 det)

For 4 det $R_{eq} = \frac{4 \times 4}{3} = \frac{16}{3}$

(4) All the resistors are in series.

$$R_{eq} = 5R = 5R$$

(3.21) $R_1 = 1 \Omega$

$$R_{eq} = R'$$

Network is infinite. Thus eqⁿ will be

$$\Rightarrow R' = 2 + \frac{R'}{R'+1}$$

$$\Rightarrow (R')^2 - 2R' - 2 = 0 \Rightarrow R' = \frac{2 + \sqrt{4+8}}{2} = \frac{2 + \sqrt{12}}{2}$$

$$\Rightarrow R = 1 + \sqrt{3} = 1 + 1.73 = 2.73$$

$$\mathcal{E} = 12V$$

$$r = 0.5$$

$$\therefore I = \frac{\mathcal{E}}{R+r} = \frac{12}{2.73+0.5} = \frac{12}{3.23} = 3.72A$$

(3.22) $R = 10 \Omega$

$$L_1 = 58.3$$

$$E_1 = IR$$

$$X = ?$$

$$L_2 = 68.5$$

$$E_2 = IX$$

$$\frac{E_1}{E_2} = \frac{L_1}{L_2} \Rightarrow \frac{10}{X} = \frac{58.3}{68.5} \Rightarrow X = \frac{68.5 \times 10}{58.3}$$

$$\Rightarrow X = 11.749 \Omega$$

If we failed to find the ~~poter~~ balance point with the given cell of emf \mathcal{E} . Then the potential of 12Ω & X could be reduced by putting a resistance in series in it.