

Current Electricity

3.1) $\text{emf} = 12\text{V}$ $r = 0.4\ \Omega$ $I_{\text{max}} = \frac{\mathcal{E}}{r} = \frac{12}{0.4} = \boxed{30\text{A}}$ Ans

Current draw from the battery will be max when ext $R = 0$.

3.2) $\text{emf} = 10\text{V}$ $r = 3\ \Omega$ $I = 0.5\text{A}$

$$I = \frac{\mathcal{E}}{R+r} \Rightarrow R+r = \frac{\mathcal{E}}{I} \Rightarrow R = \frac{10}{0.5} - 3 = \boxed{17\ \Omega}$$

Terminal Voltage = $V = IR = \frac{5}{10} \times 17 = 8.5\text{V}$

3.3) $R_1 = 1\ \Omega$ $R_2 = 2\ \Omega$ $R_3 = 3\ \Omega$

i) $R_S = R_1 + R_2 + R_3 = \boxed{6\ \Omega}$

ii) $\text{emf}(\mathcal{E}) = 12\text{V}$ $V_1 = IR_1 = 2 \times 1 = \boxed{2\text{V}}$

current = $\frac{V}{R_{\text{eq}}} = \frac{12}{6} = 2\text{A}$ $V_2 = 2 \times 2 = \boxed{4\text{V}}$
 $V_3 = 2 \times 3 = \boxed{6\text{V}}$

3.4) i) $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{2} + \frac{1}{4} + \frac{1}{5} = \frac{10+5+4}{20} = \frac{19}{20}$

$R_p = \frac{20}{19}\ \Omega$

ii) $\text{emf} = 20\text{V}$ $I_1 = \frac{\mathcal{E}}{R_1} = \frac{20}{2} = 10\text{A}$ $I_2 = \frac{20}{4} = 5\text{A}$ $I_3 = \frac{20}{5} = 4\text{A}$

Total current = $I_1 + I_2 + I_3 = 10 + 5 + 4 = \boxed{19\text{A}}$

3.5) $R_1 = 100\ \Omega$ $R_2 = 117\ \Omega$ $t_1 = 27^\circ\text{C}$ $\alpha = 1.7 \times 10^{-4}\ \text{C}^{-1}$

$$\alpha = \frac{R_2 - R_1}{R_1(t_2 - t_1)} \quad t_2 - t_1 = \frac{R_2 - R_1}{R_1 \alpha} = \frac{17 \times 10}{100 \times 1.7 \times 10^{-4}} = 10^3$$

$t_2 = 1000 + 27 = \boxed{1027^\circ\text{C}}$

3.6) $l = 15\text{m}$ $A = 6 \times 10^{-7}\text{m}^2$ $R = 5\ \Omega$


$$\rho = \frac{RA}{l} = \frac{5 \times 6 \times 10^{-7}}{15} = \boxed{2 \times 10^{-7}\ \Omega\text{m}}$$

3.7 $R_1 = 2.1 \Omega$ $t_1 = 27.5^\circ\text{C}$ $\alpha = \frac{R_2 - R_1}{R_1(t_2 - t_1)} = 0.5$
 $R_2 = 2.7 \Omega$ $t_2 = 100^\circ\text{C}$
 $= \frac{0}{2(72.5)} = 0.00394^\circ\text{C}^{-1}$
Ans

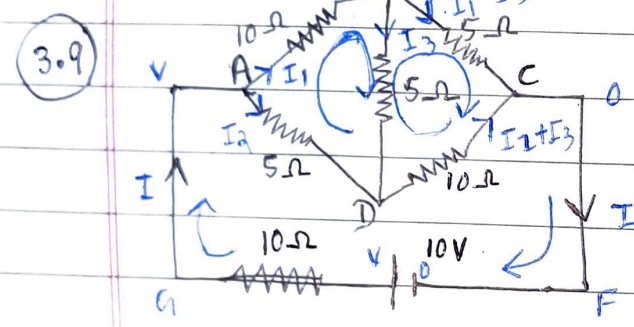3.8 $V = 230\text{V}$ $I_1 = 3.2\text{A}$ $I_2 = 2.8\text{A}$ $\alpha = 1.70 \times 10^{-4}^\circ\text{C}^{-1}$
 $V = I_1 R_1$ $V = I_2 R_2$ $t_1 = 27^\circ\text{C}$
 $R_1 = \frac{2300}{3.2} = 71.875 \Omega$ $R_2 = \frac{V}{I_2} = \frac{2300}{2.8} = 82.143 \Omega$

$\alpha = \frac{R_2 - R_1}{R_1(t_2 - t_1)}$ $t_2 - t_1 = \frac{R_2 - R_1}{R_1 \alpha} = \frac{10.268 \times 10^4}{7.70875 \times 1.7}$
 $= 840.35^\circ\text{C}$

$\therefore t_2 = 840.35 + 27 = 867.35^\circ\text{C}$ Ans



In Loop ABEDA
 $10 I_1 + 5 I_3 - 5 I_2 = 0$
In Loop BCDB
 $5(I_1 - I_3) - 10(I_2 + I_3) - 5 I_3 = 0$
In ADCFGA


$5 I_2 + 10(I_2 + I_3) + 10(I_1 + I_2) = 10$
 $5 I_2 + 10(I_2 + I_3) + 10 I = 10$
 $5 I_2 + 10(I_2 + I_3) + 10(I_1 + I_2) = 10$
 $10 I_1 - 5 I_2 + 5 I_3 = 0 \quad \text{--- (i)}$
 $5 I_1 - 10 I_2 - 20 I_3 = 0 \quad \text{--- (ii)}$
 $10 I_1 + 25 I_2 + 10 I_3 = 10 \quad \text{--- (iii)}$

$I_1 = \frac{4}{17} \text{A}$ $I_2 = \frac{6}{17} \text{A}$
 $I_3 = -\frac{2}{17} \text{A}$

$I_{AB} = I_1 = \frac{4}{17} \text{A}$ $I_{BC} = I_1 - I_3 = \frac{6}{17} \text{A}$
 $I_{DC} = \frac{4}{17} \text{A}$ $I_{AD} = \frac{6}{17} \text{A}$ $I_{BD} = -\frac{2}{17} \text{A}$

Total current = $\frac{10}{17} \text{A}$

Q.10

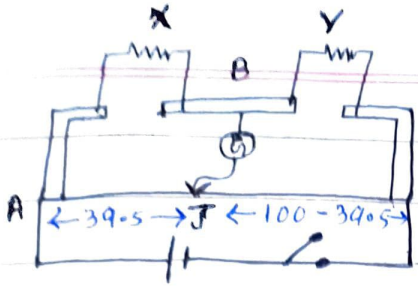

i) $l = 39.5 \text{ cm}$ $R_Y = 12.5 \Omega$

$R_X = ?$

$$\frac{R_X}{39.5} = \frac{12.5}{(100-39.5)} \quad R_X = \frac{12.5 \times 39.5}{60.5}$$

Connections are made by thick copper strips to minimise the resistance of connection.

$= 8.16 \Omega$ Ans

ii) $R = Y = 12.5 \Omega$ $S = X = 8.16 \Omega$ $l = ?$

$$\frac{12.5}{l} = \frac{8.16}{100-l} \Rightarrow 1250 - 12.5l = 8.16l$$

$$\Rightarrow 12.5l + 8.16l = 1250$$

$$\Rightarrow l = \frac{1250}{20.66} = 60.5 \Omega$$
 Ans

iii) Then the conditions of the balanced bridge still remains satisfied and so again the galvanometer will not show any current.

11) $\text{emf}(\mathcal{E}) = 8 \text{ V}$ $r = 0.5 \Omega$ $V = \mathcal{E} + I r$ $R = 15.5 \Omega$

$$\mathcal{E}'_{\text{net}} = 120 - 0.8 = 119 \text{ V}$$

$$I = \frac{\mathcal{E}'}{R+r} = \frac{112}{15.5+0.5} = \frac{112}{16} = 7 \text{ A}$$

$$V = \mathcal{E} + I r = 8 + 7 \times \frac{5}{10} = 8 + 3.5 = 11.5 \text{ V}$$
 Ans

12) $\text{emf}_1 = 1.25 \text{ V}$ $l_1 = 35 \text{ cm}$ $l_2 = 63 \text{ cm}$ $\text{emf}_2 = ?$

As $\frac{\mathcal{E}_2}{\mathcal{E}_1} = \frac{l_2}{l_1}$ $\mathcal{E}_2 = \frac{l_2}{l_1} \times \mathcal{E}_1 = \frac{63}{35} \times \frac{1.25}{4} = 2.25 \text{ V}$ Ans

13) $\rho = 8.5 \times 10^{-28} \text{ m}^{-3}$ $l = 3 \text{ m}$ $a = 2 \times 10^{-6} \text{ m}^2$

$I = 3 \text{ A}$

$I = v_d n e A$

$$v_d = \frac{I}{e n A} = \frac{3 \times 10^{-28} \times 10^{19}}{1.6 \times 8.5 \times 2 \times 10^{-6}}$$

$$t = \frac{l}{v_d} = \frac{3 \times 10^4}{1.1} = 2.73 \times 10^4 \text{ s} = \frac{3}{16 \times 85 \times 2 \times 10} = 1.1 \times 10^{-4} \text{ ms}^{-1}$$

$\approx 7.57 \text{ hr}$

$V = 400 \text{ kV}$ $I = 1800 \text{ A}$

(14)

$\sigma = 10^{-9} \text{ cm}^{-2}$

$R = 6.37 \times 10^6 \text{ m}$

Total charge

$q = \text{Surface area} \times \sigma = 4\pi R^2 \sigma$
 $= 4 \times 3.14 \times (6.37 \times 10^6)^2 \times 10^{-9}$
 $= 509.65 \times 10^3 \text{ C}$

$t = \frac{q}{I} = \frac{509 \times 10^3}{1800} = \boxed{283 \text{ sec}}$ Ans

(15) a)

emf = 2V $n = 6$

$r = 0.015 \Omega$ $R = 8.5 \Omega$ Series

$I = \frac{nE}{R + rn} = \frac{6 \times 2}{8.5 + 6 \times 0.015} = \frac{12}{8.59} \approx \boxed{1.4 \text{ A}}$


$V = 1.4 \times 8.5 = \boxed{11.9}$

b) emf = 1.9V $r = 380 \Omega$

$I = \frac{1.9}{380} = \frac{19}{3800} = \boxed{0.005 \text{ A}}$

cannot derive the stretching of car as it near 100A.

(16)

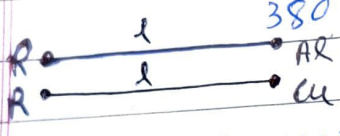

$\rho_{Al} = 2.63 \times 10^{-8} \Omega \text{ m}$

$\rho_{Cu} = 1.72 \times 10^{-8} \Omega \text{ m}$

$R_{D Al} = 2.7$

$R_{D Cu} = 8.9$

mass = Vol x density = $Al \times d$


$\frac{m_{Cu}}{m_{Al}} = \frac{\rho_{Cu} d_{Cu}}{\rho_{Al} d_{Al}} = \frac{1.72 \times 10^{-8} \times 8.9}{2.63 \times 10^{-8} \times 2.7} = 2.2$

$R = \frac{\rho l}{A}$ $\frac{\rho l}{R} \quad d = \frac{\rho l d}{R}$

Cu wire is 2.2 times heavier than Al
So Al is lighter and do not sag down.

(17)

Temp coefficient of resistivity of manganin is negligibly small.

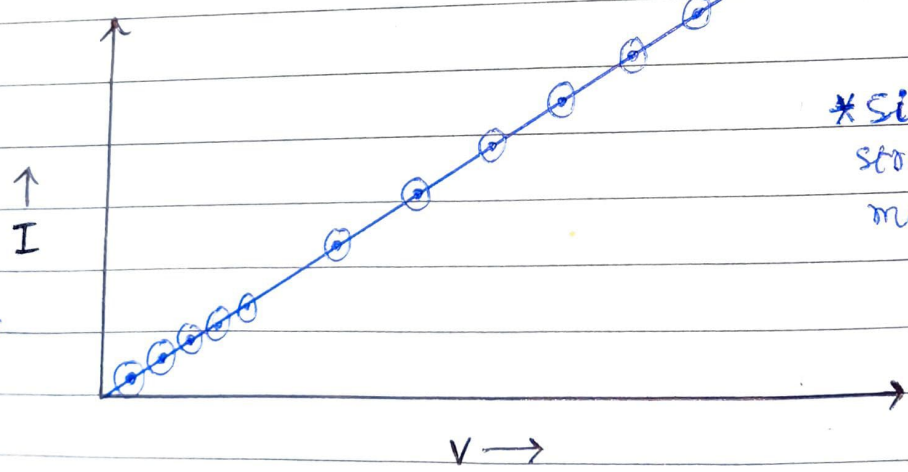

* Since V-I graph is straight line so manganin is an ohmic resistor.

(18) a)

Only current is constant. Other quantity vary inversely with area of cross section.

b)


NO, Non-ohmic conductors like, semiconductor diode, thyristor, vacuum diode

c) $I_{max} = \frac{\epsilon}{r}$ $I \propto \frac{1}{r}$ So, I_{max} is large if r is small


d) If the internal resistance is not very high, then the current will exceed the safety limit in case the circuit is short-circuited accidentally.

- 19) a) greater d) 10^{22}
 b) lower
 c) nearly independent of

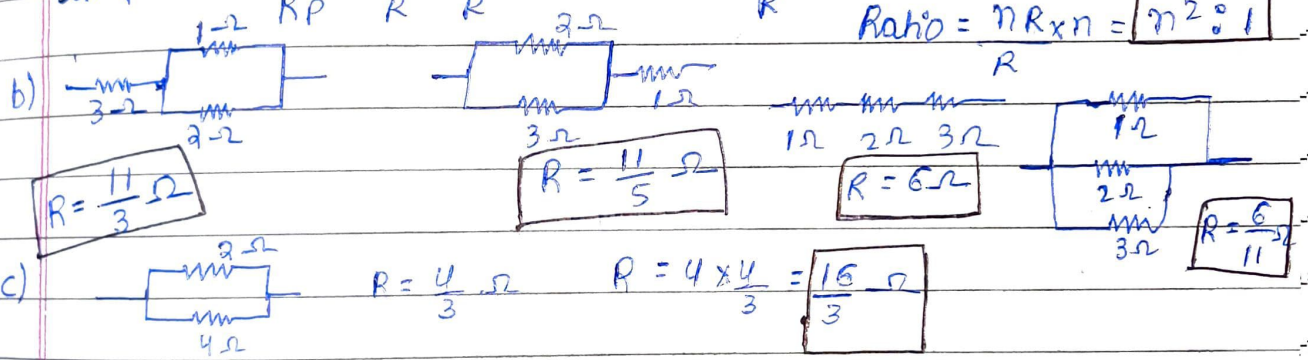20) For max effective resistance all the n resistors must be connected in series $R_s = nR$
 For minimum effective resistance all n resistors must be connected in parallel $\frac{1}{R_p} = \frac{1}{R} + \frac{1}{R} + \dots + \frac{1}{R} = \frac{n}{R}$ $R_p = R/n$
 Ratio = $nR \times n = n^2 : 1$



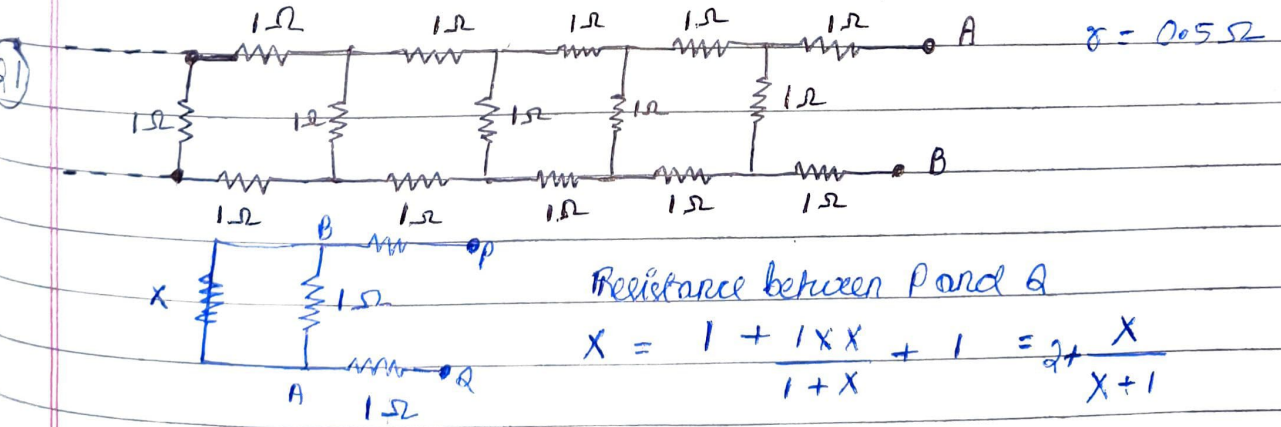a) Equivalent Resistance R
 $E_{eq} = 5R$



$I = \frac{\epsilon}{R + r}$
 $= 12$
 $2.732 + 0.5 = 3.232$ $I = \frac{12}{3.232} = 3.713 A$ Ans

$X^2 + X = 2X + 2 + X$
 $X^2 - 2X - 2 = 0$
 $X = 1 \pm \sqrt{3}$ $X = 1 + \sqrt{3}$
 $X = 2.732 \Omega$

- 22) a) $\mathcal{E}_1 = 1.02V$ $V = 2V$ $r = 0.4\Omega$ $l_1 = 67.3cm$
 $\mathcal{E}_2 = \mathcal{E}$ $\frac{\mathcal{E}}{1.02} = \frac{82.3}{67.3}$ $l_2 = 82.3cm$
 $\mathcal{E} = \frac{82.3}{67.3} \times 102 = \boxed{1.25V}$ Ans
- b) Protects the galvanometer for positions far away from the balance point, by decreasing current through it.
- c) No balance point is not affected, as no current flows through the standard cell at the balance point.
- d) Yes, it changes the potential gradient and affects the balance point.
- e) No, if $\mathcal{E}_0 > \text{emf}$ there will be no balance point on the wire AB.
- f) Unsuitable, because the balance point will be very close to the end A and the % error measured is very large.
 Modified by putting R in series so that V drop is slightly greater than the emf measured.

23

$R = 10\Omega$ $l_1 = 58.3cm$ \times $l_2 = 68.5cm$

$$\frac{\mathcal{E}_2}{\mathcal{E}_1} = \frac{l_2}{l_1} \cdot \frac{x}{R} = \frac{l_2}{l_1} \quad x = \frac{l_2}{l_1} \times R = \frac{68.5}{58.3} \times 10 = \boxed{11.75\Omega}$$

We should reduce current in the outside circuit suitably by putting a series resistor.

24

$r = ?$ $V = 1.5V$ $l_1 = 76.3cm$ $l_2 = 64.8$
 $R = 9.5\Omega$

$$r = R \left(\frac{l_1 - l_2}{l_2} \right) = \left(\frac{76.3 - 64.8}{64.8} \right) \times \frac{9.5}{10}$$

$$= \frac{9.5 \times 11.5}{64.8}$$

$$\approx \boxed{1.75\Omega}$$