

10/7/21

## Chapter - 3

## NCERT EXERCISES



1)  $\mathcal{E} = 12\text{V}$

$r = 0.4\Omega$

The current drawn from the battery will be maximum when the external resistance in the circuit is zero.

$R = 0$

$$\therefore I_{\text{max}} = \frac{\mathcal{E}}{r} = \frac{12}{0.4} = 30\text{A}$$

2)  $T = 0$

$R + r$

$$R + r = \frac{\mathcal{E}}{I}$$

$$R = \frac{\mathcal{E}}{I} - r = \frac{10}{0.5} - 3 = 17\Omega$$

$\therefore$  terminal voltage

$$V = IR = 0.5 \times 17 = 8.5\text{V}$$

3)  $R_5 = R_1 + R_2 + R_3 = 6\Omega$

ii) Current in the circuit  $\Rightarrow I = \frac{\mathcal{E}}{R} = \frac{12}{6} = 2\text{A}$

$\therefore$  potential drops across different resistors are

$$V_1 = IR_1 = 2 \times 1 = 2\text{V}$$

$$V_2 = IR_2 = 2 \times 2 = 4\text{V}$$

$$V_3 = IR_3 = 2 \times 3 = 6\text{V}$$

$$4. i) \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$= \frac{1}{2} + \frac{1}{4} + \frac{1}{5} = \frac{19}{20}$$

$$\therefore R_p = \frac{20}{19} \Omega.$$

ii) Currents drawn through diff. resistors are

$$I_1 = \frac{E}{R_1} = \frac{20}{2} = 10 \text{ A}$$

$$I_2 = \frac{E}{R_2} = \frac{20}{4} = 5 \text{ A}$$

$$I_3 = \frac{E}{R_3} = \frac{20}{5} = 4 \text{ A}$$

Total amount drawn from the battery:

$$I = I_1 + I_2 + I_3 = 10 + 5 + 4 = 19 \text{ A}$$

5) Here,  $R_1 = 100 \Omega$   
 $R_2 = 117 \Omega$   
 $t_1 = 27^\circ \text{C}$   
 $\alpha = 1.70 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}$

$$\text{As } \alpha = \frac{R_2 - R_1}{R_1 (t_2 - t_1)}$$

$$\therefore t_2 - t_1 = \frac{R_2 - R_1}{R_1 \alpha} = \frac{117 - 100}{100 \times 1.70 \times 10^{-4}} = 1000$$

$$\therefore t_2 = 1000 + t_1 = 1000 + 27 = 1027^\circ\text{C}$$

⑥ Resistor

6)  $l = 15 \text{ m}$   
 $A = 6.0 \times 10^{-7} \text{ m}^2$   
 $R = 5.0 \Omega$

Resistivity  $\rho = \frac{RA}{l} = \frac{5.0 \times 6.0 \times 10^{-7}}{15}$   
 $= 2.0 \times 10^{-7} \Omega \text{ m}$

7) Here,  $R_1 = 2.1 \Omega$   
 $t_1 = 27.5^\circ\text{C}$   
 $R_2 = 2.7 \Omega$   
 $t_2 = 100^\circ\text{C}$

temp. coefficient of resistivity of silver

$$\alpha = \frac{R_2 - R_1}{R_1(t_2 - t_1)} = \frac{2.7 - 2.1}{2.1(100 - 27.5)}$$

$$= \frac{0.6}{2.1 \times 72.5}$$

$$= 0.00394^\circ\text{C}^{-1}$$

$$\begin{aligned}
 8) \text{ Here, } & V = 230 \text{ V} \\
 & I_1 = 3.2 \text{ A} \\
 & I_2 = 2.8 \text{ A} \\
 & \alpha = 1.70 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}
 \end{aligned}$$

Resistance at room temp

$$R_1 = \frac{V}{I_1} = \frac{230}{3.2} = 71.875 \Omega$$

Resistance at steady temp.

$$R_2 = \frac{V}{I_2} = \frac{230}{2.8} = 82.143 \Omega$$

$$\text{Now, } \alpha = \frac{R_2 - R_1}{R_1 (t_2 - t_1)}$$

$$\therefore t_2 - t_1 = \frac{R_2 - R_1}{R_1 \alpha}$$

$$= \frac{82.143 - 71.875}{71.875 \times 1.70 \times 10^{-4}} = \frac{10.268 \times 10^4}{71.875 \times 1.7}$$

$$= 840.35^\circ\text{C}$$

$\therefore$  ~~Q10~~ Steady temp. of element.

$$\begin{aligned}
 t_2 &= 840.35 + 27 \\
 &= 867.35^\circ\text{C}
 \end{aligned}$$

9) let  $I_1, I_2, I_3$  be the currents as shown in the below figure we apply kirchoff's second rule to different rules.

for loop ABDA,

$$10I_2 + 5I_3 - 5I_2 = 0$$

for loop BCDB,

$$5(I_2 - I_3) - 10(I_2 + I_3) - 5I_3 = 0$$

for loop ~~ADCPDA~~ ADCPDA,

$$5I_2 + 10(I_2 + I_3) + 10(I_1 + I_2) = 10$$

①

$$10I_1 - 5I_2 + 5I_3 = 0 \quad \text{--- (1)}$$

$$5I_1 - 10I_2 - 20I_3 = 0 \quad \text{--- (2)}$$

$$10I_1 + 25I_2 + 10I_3 = 10 \quad \text{--- (3)}$$

solving equations (1), (2) & (3), we get

$$I_1 = \frac{4}{17} \text{ A}, \quad I_2 = \frac{6}{17} \text{ A}, \quad I_3 = \frac{-2}{17} \text{ A}$$

currents in different branches are

$$I_{AB} = I_1 = \frac{4}{17} \text{ A}, \quad I_{BC} = I_1 - I_3 = \frac{6}{17} \text{ A}$$

$$I_{OC} = I_2 + I_3 = \frac{4}{17} \text{ A}, \quad I_{AD} = I_2 = \frac{6}{17} \text{ A}$$

$$I_{BD} = I_3 = \frac{-2}{17} \text{ A}$$

Total current,

$$I = I_1 + I_2 = \frac{10}{17} \text{ A}$$

11) When the storage battery of 8.0 V is charged with a d.c supply of 120 V, the net e.m.f in the circuit will be

$$e' = 120 - 8.0 = 112 \text{ V.}$$

Current in the circuit during charging

$$I = \frac{e'}{R + r} = \frac{112}{15.5 + 0.5} = 7 \text{ A}$$

The terminal voltage of battery during charging  
 $V = \mathcal{E} + Ir = 8 + 7 \times 0.5 = 11.5 \text{ V.}$

12) Here,  $\mathcal{E}_1 = 1.25 \text{ V}$   
 $l_1 = 35.0 \text{ cm}$   
 $l_2 = 63.0 \text{ cm}$   
 $\mathcal{E}_2 = ?$

$$\mathcal{E}_1 = \frac{A_2}{A_1} = \frac{l_2}{l_1}$$

$$\therefore \mathcal{E}_2 = \frac{l_2}{l_1} \times \mathcal{E}_1 = \frac{63}{35} \times 1.25 = 2.25 \text{ V.}$$

13) Drift speed,

$$v_A = \frac{I}{enA}$$

$$= \frac{3}{1.6 \times 10^{-19} \times 8.5 \times 10^{28} \times 2 \times 10^{-6}} \text{ m/s}$$

$$= \frac{3}{16 \times 33 \times 2 \times 10} \text{ m/s} = 1.1 \times 10^{-4} \text{ m/s}$$

Required time

$$t = \frac{II}{4A}$$

$$= \frac{3}{1.1 \times 10^{-4}} \text{ s} = 2.73 \times 10^4 \text{ s} \approx 7.57 \text{ h}$$