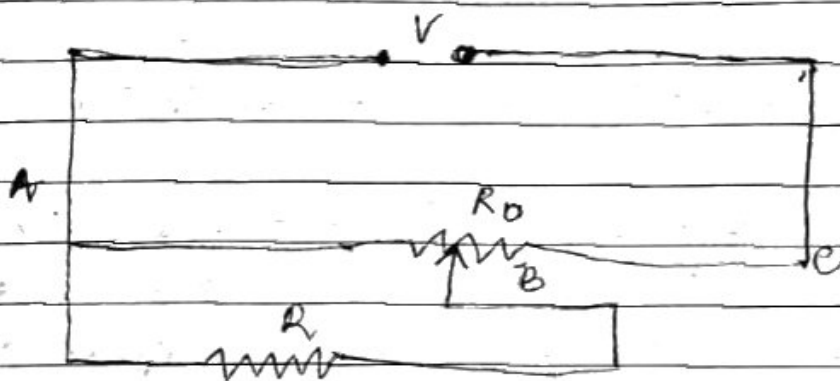


## Ch - Current Electricity

Question:

A resistance  $R$  draws current from a potentiometer of resistance  $R_0$  as shown. Derive an expression for the voltage across  $R$  when the sliding contact is in the middle of the potentiometer wire. (NCERT)



Ans

When the sliding contact is in middle, a resistance of  $R_0/2$  is connected in series with a parallel combination of  $R$  and  $R_0/2$ .

Hence, net resistance is ~~given~~ given by:

$$R_{eq} = \frac{R_0}{2} + \frac{R_0}{2} \parallel R$$

Current flowing through the circuit is given by

$$I = \frac{V}{R_{eq}}$$

Potential across  $R$  is given by:

$$V_R = I \left( \frac{R_0}{2} \parallel R \right) \quad V_R = \frac{V}{R_{eq}} \left( \frac{R_0}{2} \parallel R \right)$$

$$\text{Solving } V_R = \frac{R}{4R + R_0} V$$

Page \_\_\_\_\_

Q Two students  $x$  and  $y$  perform an experiment on potentiometer separately using the circuit given below, keeping other parameters unchanged, how will the position of the null point be affected, if

ans

(a) By increasing resistance  $R$  the current through  $AB$  decreases, so potential gradient decreases. Hence a greater length of wire would be needed for balancing the same potential difference. So the null point would shift towards  $B$ .

ans

(b) By decreasing resistance  $S$ , the current through  $AB$  remains the same, potential gradient does not change. As  $K_2$  is open so there is no effect of  $S$  on null point.

Q3

a) (i) long wire is used so that potential gradient can be observed easily and can be measured.

(ii) wire having uniform area is taken so that potential gradient value may not change drastically while doing the experiment.


(iii) emf of driver cell should be greater because as the circuit starts the potential is dropped across the resistor and more emf is needed to drive current in the circuit.

Q2 b)

Ans

As we know that Potential gradient,  $k = \frac{V}{L}$

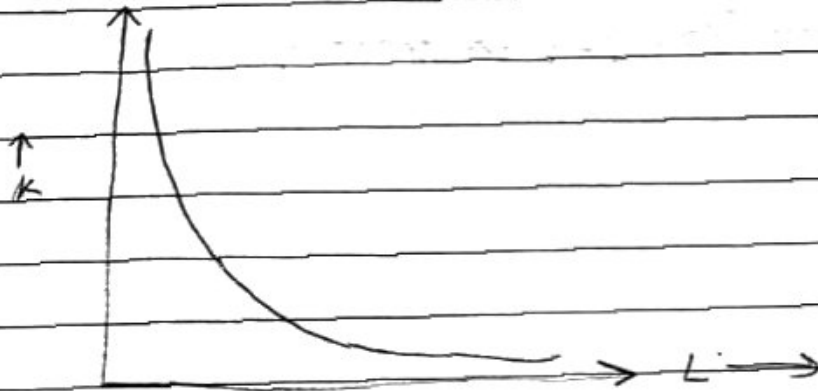Now as the length increases, potential gradient will start decreasing.



Q

a) The purpose of high resistance  $R_2$  is to reduce the current through the galvanometer. When jockey is far from balance point, this saves the galvanometer and the cell from being damaged.

b) When resistance  $R_1$  is decreased, the potential gradient of potentiometer wire increases, so balance point (J) shifts to longer length of wire.

c) (i) The balance point is not obtained because maximum emf across potentiometer wire is  $< V$ .

(ii) When key (K) is closed the terminal difference of cell is zero, so balance point cannot be between A and B. (Since  $V \cdot k \cdot l = 0$  for  $V = 0$ )

Q  
(i)  $R_1$  is decreased

ans: Decreases

(The potential gradient would increase)

(ii)  $R_2$  is increased

ans: Increases

(The terminal p.d across the cell would increase)