

NCPRT Exercise

Current Electricity

3.1 Here $E = 12V$, $r = 0.4$

The current drawn from the battery will be maximum when the external resistance in the circuit is zero i.e., $R = 0$

$$\therefore I_{\text{max}} = \frac{E}{r} = \frac{12}{0.4} = 30A$$

3.2 As $I = \frac{E}{R+r}$

$$R+r = \frac{E}{I}$$

$$R = \frac{E}{I} - r = \frac{12}{0.5} - 0.4 = 23.2$$

Terminal voltage,

$$V = IR = 0.5 \times 17 = 8.5V$$

3.3 a) $R_{\text{eq}} = R_1 + R_2 + R_3 = 6\Omega$

b) Current in the circuit, $I = \frac{E}{R} = \frac{12}{6} = 2A$

\therefore Potential drops across different resistors are

$$V_1 = IR_1 = 2 \times 1 = 2V; V_2 = IR_2 = 2 \times 2 = 4V; V_3 = IR_3 = 2 \times 3 = 6V$$

3.4 a) $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{2} + \frac{1}{4} + \frac{1}{5} = \frac{19}{20}$

$$R_p = \frac{20}{19}$$

b. current drawn through different resistors are :-

$$I_1 = \frac{E}{R_1} = \frac{20}{2} = 10A, I_2 = \frac{E}{R_2} = \frac{20}{4} = 5A$$

$$\frac{E}{R_3} = \frac{20}{5} = 4A$$

Total current drawn from the battery,

$$I = I_1 + I_2 + I_3 = 10 + 5 + 4 = 19A$$

3.5 Here $R_1 = 100\Omega$, $R_2 = 117\Omega$, $t_1 = 27^\circ C$
 $\alpha = 1.70 \times 10^{-4} \text{ } ^\circ C^{-1}$

$$\text{as } \alpha = \frac{R_2 - R_1}{R_1(t_2 - t_1)}$$

$$\therefore t_2 - t_1 = \frac{R_2 - R_1}{R_1 \alpha} = \frac{117 - 100}{100 \times 1.70 \times 10^{-4}} = 1000$$

$$\therefore t_2 = 1000 + t_1 = 1000 + 27 = 1027^\circ C$$

3.6 Here $l = 15m$, $A = 6.0 \times 10^{-7} m^2$, $R = 50\Omega$
 Resistivity, $\rho = \frac{RA}{l} = \frac{50 \times 6.0 \times 10^{-7}}{15} = 2.0 \times 10^{-7} m$

3.7 Here $R_1 = 2.0\Omega$, $t_1 = 27.5^\circ C$, $R_2 = 2.7\Omega$, $t_2 = 100^\circ C$

Temperature coefficient or resistivity of silver

$$\alpha = \frac{R_2 - R_1}{R_1(t_2 - t_1)} = \frac{2.7 - 2.0}{2.0(100 - 27.5)} = \frac{0.6}{2.1 \times 72.5} = 0.00394 \text{ } ^\circ C^{-1}$$

3.8

Here $V = 230V$, $I_1 = 3.2A$, $I_2 = 22.8A$, $\alpha = 1.70 \times 10^{-4} \text{ } ^\circ\text{C}^{-1}$

Resistance at room temperature;

$$R_1 = \frac{V}{I_1} = \frac{230}{3.2} = 71.875 \Omega$$

Resistance at steady temperature,

$$R_2 = \frac{V}{I_2} = \frac{230}{2.8} = 82.143 \Omega$$

Now, $\alpha = \frac{R_2 - R_1}{R_1(t_2 - t_1)}$

$$\therefore t_2 - t_1 = \frac{R_2 - R_1}{R_1 \alpha} = \frac{82.143 - 71.875}{71.875 \times 1.70 \times 10^{-4}} = 840.35^\circ\text{C}$$
$$t_2 = 840.37 + 27 = 867.35^\circ\text{C}$$

3.9) I = current flowing through the outer circuit

I_1 = current flowing through branch AB

I_2 = current flowing through branch AD

I_3 = current flowing through branch BD

$I_2 + I_3$ = current flowing through branch CD.

$I_1 = I_3$ = current flowing through branch BC

For loop ABDA,

$$10I_1 + 5I_3 - 5I_2 = 0$$

For loop BCDB,

$$5(I_1 - I_3) - 10(I_2 + I_3) - 5I_3 = 0$$

For loop ABCFGA,

$$5I_2 + 10(I_2 + I_3) + 10(I_1 + I_2) = 10$$

$$10I_1 - 5I_2 + 5I_3 = 0 \quad (1)$$

$$5I_1 - 10I_2 - 20I_3 = 0 \quad (2)$$

$$10I_1 + 25I_2 + 10I_3 = 0 \quad (3)$$

Solving equations (1), (2) and (3) we get
 $I_1 = \frac{4}{17} A$, $I_2 = \frac{6}{17} A$, $I_3 = -\frac{2}{17} A$

Current in different branches are:-

$$I_{AB} = I_1 = \frac{4}{17} A, I_{BC} = I_1 - I_3 = \frac{6}{17} A$$

$$I_{DC} = I_2 + I_3 = \frac{4}{17} A; I_{AD} = I_2 = \frac{6}{17} A,$$

$$I_{BD} = I_3 = -\frac{2}{17} A$$

Total current.

$$I = I_1 + I_2 = \frac{10}{17} A$$

3.10. a) Here $l = 35.9 \text{ cm}$, $R = x = 7$, $s = 4.12.5 \Omega$

$$\text{As } s = \frac{100 - l}{x} R \therefore 12.5 = \frac{100 - 39.5}{39.5} \times R$$

$$R = \frac{12.5 \times 39.5}{60.5} = 8.16 \Omega$$

Connections are made by thick copper strips to minimise the resistance of connections which are not accounted for in the above formula.

(b) when x and y are interchanged,

$$R = y = 12.5 \Omega, s = x = 8.16 \Omega, l = ?$$

$$\text{As } s = \frac{100 - l}{x} R \therefore 8.16 = \frac{100 - l}{l} \times 12.5$$

$$\Rightarrow 8.16 \times l = 1250 - 12.5l$$

$$\Rightarrow l = \frac{1250}{20.66} = 60.5 \text{ cm from end A.}$$

(c) when the galvanometer and cell are interchanged at the balance point, the conditions of the balance bridge are still satisfied and so

again the galvanometer will not show any current.

3.11

When the storage battery of 8.0 V is charged with a dc supply of 120 V, the net emf in the circuit will be

$$E' = 120 - 8.0 = 112 \text{ V}$$

current in the circuit during charging,

$$I = \frac{E'}{R+r} = \frac{112}{15.5+0.5} = 7 \text{ A}$$

The terminal voltage of the battery during charging,

$$V = E + Ir = 8.0 \times 7 \times 0.5 = 11.5 \text{ V}$$

The series resistor limits the current drawn from the external source. In its absence, the current will be very dangerously high.

3.12

Here $E_1 = 12.5 \text{ V}$, $l_1 = 35.0 \text{ cm}$, $l_2 = 63.0 \text{ cm}$

$$E_2 = l_2 \times E_1 = \frac{63 \times 1.25}{35} = 2.025 \text{ V}$$

~~$$F_s \cdot l_2 \propto E_1 = \frac{63 \times 1.25}{35}$$~~

3.13 Here $n = 8.5 \times 10^{28} \text{ m}^{-3}$, $l = 3 \text{ cm}$, $A = 2.0 \times 10^{-6} \text{ m}^2$
 $\rightarrow e = 1.6 \times 10^{-19} \text{ C}$, $I = 3.0 \text{ A}$

drift speed,

$$v_d = \frac{I}{enA} = \frac{3}{1.6 \times 10^{-19} \times 8.5 \times 10^{28} \times 2 \times 10^{-6}} \text{ m/s}$$

$$= \frac{3}{16 \times 8.5 \times 2 \times 10} \text{ m/s} = 1.01 \times 10^{-4} \text{ m/s}$$

Required Time :-

$$t = \frac{1}{\text{Vol}} \times 3 = \frac{1}{1.1 \times 10^{-4}} \times 2.073 \times 10^4 \text{ s} = 2.073 \times 10^4 \text{ s} = 2.073 \text{ h}$$

3.14 Surface charge density, $\sigma = 10^{-9} \text{ cm}^{-2}$
 Radius of the earth, $R = 6.37 \times 10^6 \text{ m}$
 Current, $I = 1800 \text{ A}$

Total charge of the globe,

$$q = \frac{4\pi R^2 \sigma}{3}$$

$$= 4.314 \times (6.37 \times 10^6)^2 \times 10^{-9}$$

$$= 509.65 \times 10^3 \text{ C}$$

Required time,

$$t = \frac{q}{I} = \frac{509.65 \times 10^3}{1800} = 283.138 \approx 283.1$$

3.15 a) Here $E = 2 \text{ V}$, $r_1 = 0.015 \Omega$, $R = 8.5 \Omega$, $r_2 = 6 \Omega$
 When the cells are joined in series, the current is

$$I = \frac{nE}{R + r_{\text{total}}} = \frac{6 \times 2}{8.5 \times 6 + 0.015} = \frac{12}{51} \text{ A} \approx 1.4 \text{ A}$$

$$\text{Terminal voltage, } V = IR = 1.4 \times 8.5 = 11.9 \text{ V}$$

b) Here $E = 1.9 \text{ V}$, $r_1 = 380 \Omega$

$$I_{\text{max}} = \frac{E}{r} = \frac{1.9}{380} = 0.005 \text{ A}$$

This secondary cell cannot relieve the starting motor of a car because that requires a large current of about 100 A for a few seconds.

3.016


$$\text{mass} = \text{volume} \times \text{density} = Al d$$
$$\Rightarrow \frac{fl}{R} \cdot ld = \frac{fdl^2}{R}$$

As the two wires are of equal length and have same resistance, their mass ratio will be

$$\frac{\text{Mass}_{\text{Cu}}}{\text{Mass}_{\text{Al}}} = \frac{I_{\text{cu}} L_{\text{cu}}}{I_{\text{Al}} L_{\text{Al}}} = \frac{1.72 \times 10^{-8} \times 8.9}{2.63 \times 10^{-8} \times 2.7} = 2.1558 \approx 2.2$$

that is copper wire is 2.2 times heavier than aluminium wire. Since aluminium is lighter, it is preferred for long suspension of cables. otherwise heavy cable may sag down due to its own weight.

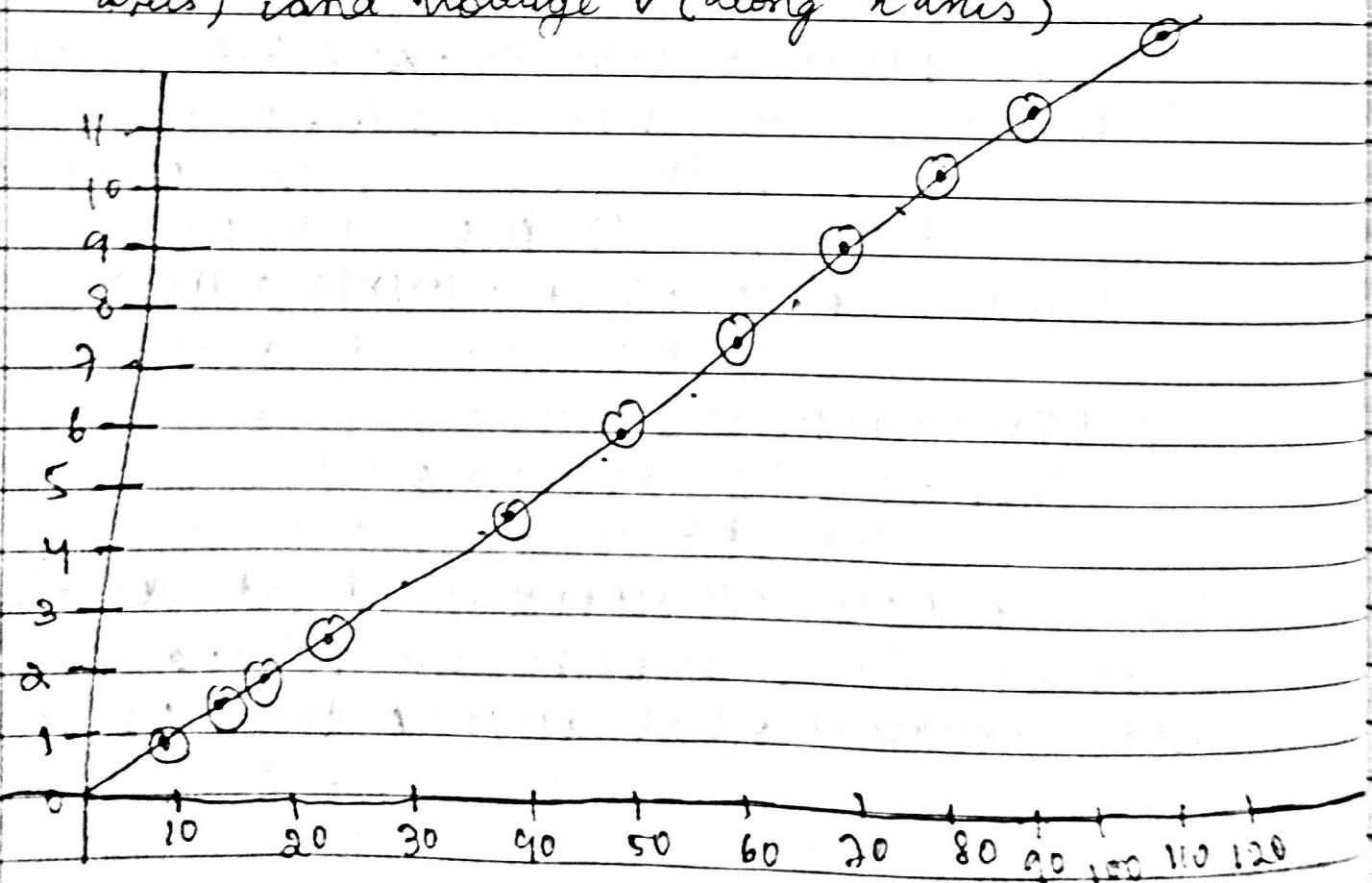3.017 we plot a graph between current I (along y axis) and voltage v (along x axis)



Since the V-I graph is almost a straight line therefore, manganin resistor is an ohmic resistor over given ranges of voltage and current. As the current increases from 0 to 8A, the temperature coefficient of resistance resistivity of mega-manganin alloy is negligibly small.

3.18

- a) Only current is constant because it is given to be steady. Other quantities: current density, electric field and drift speed vary inversely with area of cross-section.
- b) No, Ohm's law is not universally applicable for all conducting elements. Examples of non-ohmic elements are vacuum diode, diode, semiconductor diode, thyristor, gas, discharge tube, electrolytic solution, etc.
- c) The maximum current that can be drawn from a voltage supply is given by

$$I_{\max} = \frac{E}{r}$$

Clearly, I_{\max} will be large if r is small.

- d) If the internal resistance is not very large then the current will exceed the safety limits of case the circuit is short circuited accidentally.

3.19

- (a) greater
- (b) lower
- (c) is nearly independent of
- (d) 10^{22}

3.20

(a) For maximum effective resistance, all the n resistors must be connected in series.

\therefore Maximum effective resistance, $R_s = nR$

For minimum effective resistance, all the n resistors must be connected in parallel.

It is given by

$$\frac{1}{R_p} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \dots \text{ n terms} = \frac{n}{R}$$

\therefore Minimum effective resistance, $R_p = \frac{R}{n}$

$$\frac{R_s}{R_p} = \frac{nR}{R/n} = \frac{n^2}{1} = n^2 \Omega$$

(b) Here $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$

(i) When parallel combination of 1Ω and 2Ω resistor is connected in series with 3Ω resistor the equivalent resistance is

$$R + R_p + R_3 = \frac{R_1 \parallel R_2}{R_1 + R_2} + R_3 = \frac{1 \times 2}{1+2} + 3 = \frac{2}{3} + 3 = \frac{11}{2}\Omega$$

(ii) When parallel combination of 2Ω and 3Ω resistors is connected in series 1Ω resistor the equivalent resistance is !

$$R = \frac{R_2 R_3}{R_2 + R_3} + R_1 = \frac{2 \times 3 + 1}{2 + 3} + \frac{6}{5} = 1 + \frac{11}{5} = 2\Omega$$

(iii) When the three resistances are connected in series, the equivalent resistance is

$$R_1 + R_2 + R_3 = 1 + 2 + 3 = 6\Omega$$

(iv) When the three resistances are connected in parallel, the equivalent resistance is

~~$$R_1 + R_2 + R_3 = 1 + 2 + 3 = 6\Omega$$~~

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{1} + \frac{1}{2} + \frac{1}{3} = \frac{11}{6}$$

$$R = \frac{6}{11}\Omega$$

Ques. On figure (a) :-

$$\frac{1}{R} = \frac{1}{2} + \frac{1}{4} = \frac{2+1}{4} = \frac{3}{4}$$

$$R = \frac{4}{3}$$

$$\therefore \text{Resistance of the total network} = 4 \times \frac{4}{3} = \frac{16}{3}\Omega$$

On figure (b) :-

$$R = 5\Omega$$


Ques.

Let the equivalent resistance of the infinite network be n . The network consists of infinite units of 3 resistors of $1\Omega, 1\Omega, 1\Omega$.

Resistance between A and B :-

~~Method~~
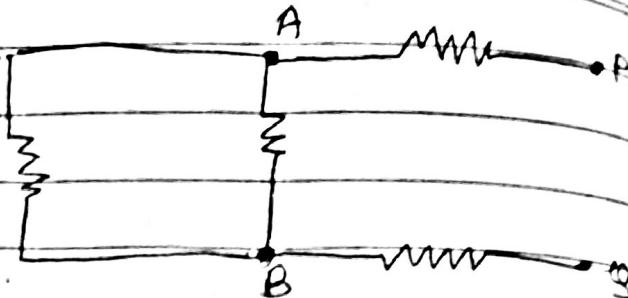
$$= \frac{n \times 1}{n+1} - \frac{x}{n+1}$$



$$\text{Resistance between } P \text{ and } Q = \frac{1+x}{n+1} + 1 = 2 + \frac{n}{n+1}$$

$$x = 2 + \frac{n}{1+n}$$

$$x^2 = 2$$

$$x^2 - 2x - 2 = 0$$

$$x = 1 \pm \sqrt{3}$$

As the value of resistance cannot be negative, so

$$n = 1 + \sqrt{3} = 2.732 \Omega$$

$$\text{Q. } I = \frac{E}{x+r} = \frac{12}{2.732 + 0.5} = 3.713 A$$

3.22

$$\text{a) } E_1 = 1.002 V, l_1 = 67.3 \text{ cm } f = 9, E_2 = E = ? \\ l_2 = 82.3$$

$$\frac{E_2}{E_1} = \frac{l_2}{l_1} \Rightarrow E = \frac{82.3}{67.3} \times 1.002 = 1.25 V$$

- (b) High resistance of $600 k \Omega$ protects the galvanometer for positions far away from the balance point, by decreasing current.

- (c) No, balance point is not affected by high resistance because no current flows through the standard cell at the balance point.
- (d) No, the arrangement will not work. If
- (a) The point is not affected by the presence of high resistance.
 - (b) The method would not work if the driver cell of the potentiometer had an emf of 1.0 V instead of 2.0 V. This is because of the driver cell of the potentiometer is less than the emf of the other cell, then there should be no balance point on the wire.

3.23 Here $L_1 = 76.3 \text{ cm}$, $L_2 = 64.8 \text{ cm}$, $R = 9.5 \Omega$

The formula for the internal resistance of a cell by the potentiometer method is

$$r = R \left(\frac{L_1 - L_2}{L_2} \right) = 9.5 \left(\frac{76.3 - 64.8}{64.8} \right) = \frac{9.5 \times 11.5}{64.8} = 1.7 \Omega$$