

### Home Assignment:

1. While the slide is in the middle of the potentiometer only half of its resistance ( $R_0/2$ ) will be between the points A and B. Hence, the total resistance between A and B, say  $R_1$ , will be given by the following expression:

$$\frac{1}{R_1} = \frac{1}{R} + \frac{1}{(R_0/2)}$$

$$R_1 = \frac{R_0 R}{R_0 + 2R}$$

The total resistance between A and C will be sum of resistance between A and B and B and C, i.e.,  $R_1 + R_0/2$

∴ The current flowing through the potentiometer will be,

$$I = \frac{V}{R_1 + R_0/2} = \frac{2V}{2R_1 + R_0}$$

The voltage  $V_1$  taken from the potentiometer will be the product of current  $I$  and resistance  $R_1$ ,

$$V_1 = IR_1 = \left( \frac{2V}{2R_1 + R_0} \right) \times R_1$$

Substituting for  $R_1$ , we have a

$$V_1 = \frac{2V}{2 \left( \frac{R_0 \times R}{R_0 + 2R} \right) + R_0} \times \frac{R_0 \times R}{R_0 + 2R}$$

$$V_1 = \frac{2VR}{2R + R_0 + 2R} \quad \text{OR} \quad V_1 = \frac{2VR}{4R + R_0}$$

i) By increasing resistance  $R$ , the current through  $AB$  decreases, so potential gradient decreases. Hence, a greater length of wire would be needed for balancing the same potential difference. So, the null point would shift towards  $B$ .

ii) By decreasing resistance  $S$ , the current through  $AB$  remains the same, potential gradient does not change. As  $K_2$  is open so there is no effect of  $S$  on null point.

3a) Principle of potentiometer: The potential drop across the length of a steady current carrying wire of uniform cross-section is proportional to the length of the wire.


i) We use a long wire to have a lower value of potential gradient (i.e., a lower 'least count') or greater sensitivity of the potentiometer.



i) The area of cross-section has to be uniform to get a 'uniform wire' as per the principle of the potentiometer.

iii) The emf of the driving cell has to be greater than the emf of the primary cells as otherwise no balance point would be obtained.

b) Potential gradient  $K = V/L$

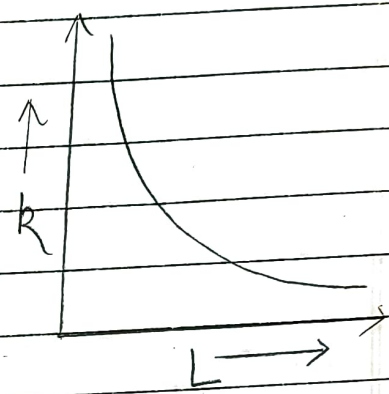

4a) The purpose of high resistance  $R_2$  is to reduce the current through the galvanometer. When jockey is far from the balance point, this saves the galvanometer and the cell (of emf  $\mathcal{E}$ ) from being damaged.

b) When resistance  $R_1$  is decreased, the potential gradient of potentiometer wire increases, so balance point (J) shifts to longer length of wire.

c) The balance point is not obtained because maximum emf across potentiometer wire is  $2V$

(2) When key (K) is closed, the terminal potential difference of cell is zero, so balance point cannot be between A and B. (Since  $V = RL \Rightarrow l = 0$  for  $V = 0$ )

5 i) Decreases as the potential gradient would increase.

ii) Increases as the terminal p. d. across the cell would increase.